

# Revised Version

R1


ENE610

9/26/07

## CHAPTER 8
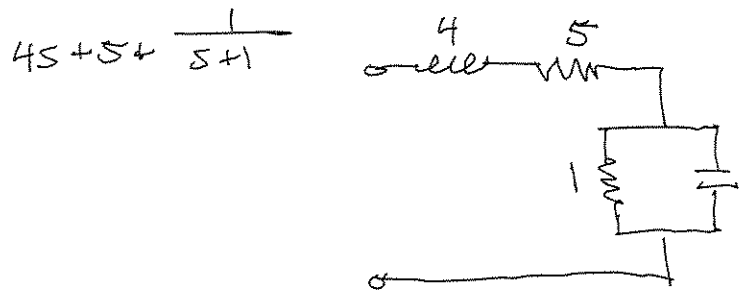
### SYNTHESIS OF PASSIVE & ACTIVE NETWORKS

$$\text{EX. } z(s) = \frac{4s^2 + 9s + 6}{s+1} = \frac{4s(s+1) + 5(s+1) + 1}{s+1}$$



$$z(s) = s-1 \leftarrow \text{NOT REAL}$$

### POSITIVE REAL FUNCTIONS

A RATIONAL FUNCTION  $z(s) = \frac{N(s)}{D(s)}$  A POSITIVE REAL

- iff
- a)  $z(s)$  HAS NO POLES IN THE RHP OF THE COMPLEX PLANE
  - b) THE POLES OF  $z(s)$  ON  $(j\omega)$  AXIS SHOULD BE SIMPLE  
WITH REAL & POSITIVE RESIDUES MUST BE ORDER 1 OR LOWER
  - c)  $\text{Re}\{z(j\omega)\} \geq 0$  FOR ALL  $\omega$  ( $0 \leq \omega < \infty$ )

IF  $Z(s) = \frac{N(s)}{D(s)}$  IS POSITIVE REAL THEN THE FOLLOWING ARE TRUE:


- 1)  $N(s) \neq D(s)$
- 2) ALL THE ZEROS AND POLES OF  $Z(s)$  ARE IN THE LHP  $s$ -PLANE
- 3)  $Z(s) \neq Z^*(s)$  ARE SIMPLE (ON  $j\omega$ ) w/ RFP RESIDUES
- 4)  $N(s) \neq D(s)$  DIFFER ONLY  $\perp$  DEGREE
- 5) NO MULTIPLE POLES OR ZEROS AT THE ORIGIN

EX.  $Z(s) = \frac{1}{s^2+1} \Rightarrow$  CONDITION 4 VIOLATED

- FOSTER METHOD  $\rightarrow$  1<sup>ST</sup> <sup>FORM</sup> ORDER, 2<sup>ND</sup> ORDER (IMPEDANCE) <sup>FORM</sup>
- CAUERS METHOD  $\rightarrow$  1<sup>ST</sup> ORDER, 2<sup>ND</sup> ORDER (ADMITTANCE) <sup>FORM</sup>


ONCE A FUNCTION IS PR  $\neq$  REACTANCE THEN:
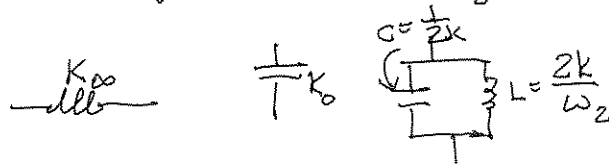
$$Z(s) = K_{\infty}s + \frac{K_0}{s} + \frac{2K_2s}{s^2+\omega_2^2} + \frac{2K_4s}{s^2+\omega_4^2} + \dots + \frac{2K_ms}{s^2+\omega_m^2}$$




Note: Corrections Made Here

R<sub>3</sub>

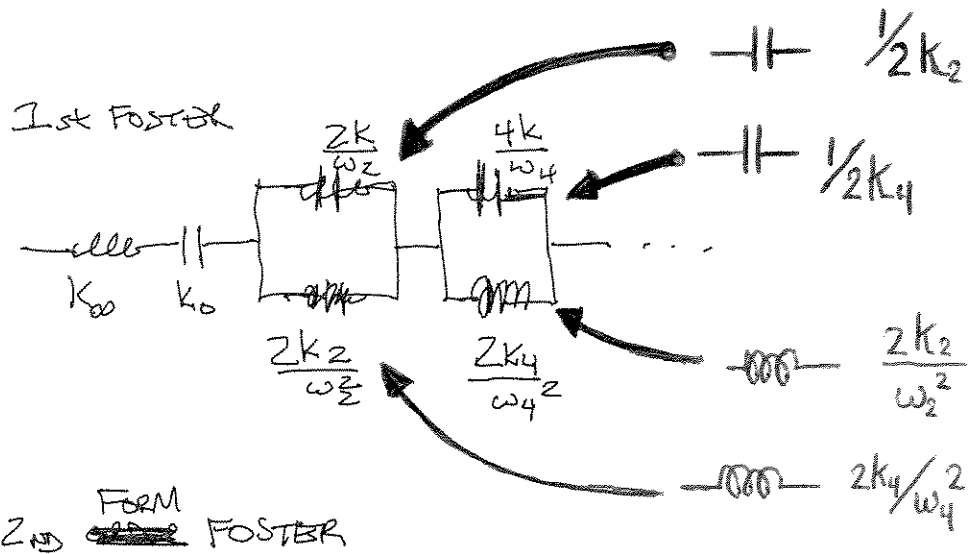


\* in L-C tanks, L & C should be in series
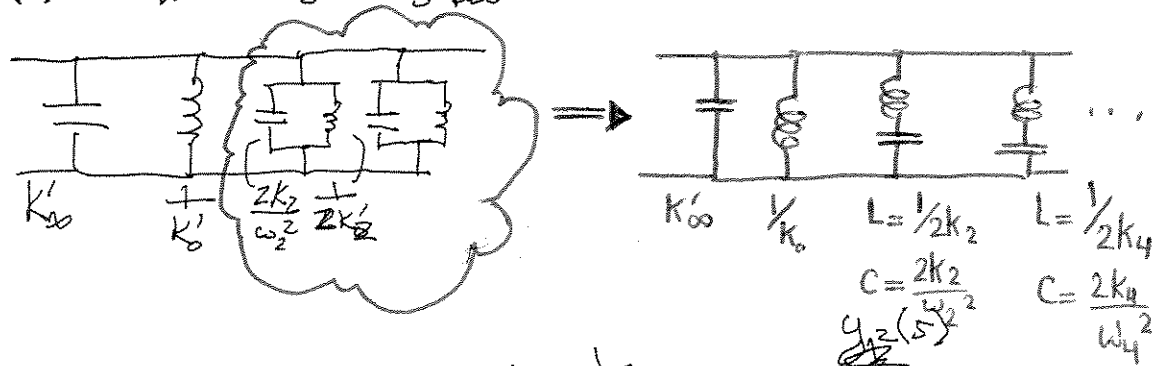
$$Y(s) = K_{\infty} s + \frac{K'_0}{s} + \frac{2K'_2}{s^2 + \omega_2^2} + \dots$$



$$Z(s) = L_1 s + Z_1(s) \quad Y_1 = \frac{1}{Z_1} = C_2 s + \dots$$

$$Z_2 = \frac{1}{Y_2} = L_3 s + Z_3(s)$$

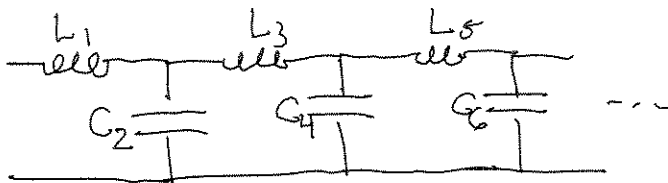

PROBLEM 8.4 IN TEXT BOOK

~~1<sup>st</sup>~~ FORM CAUER

$$\begin{aligned}
 & \cancel{Z(s) = L_1 s} \\
 Z_1(s) &= L_1 s + \frac{1}{C_2 s + \frac{1}{L_3 s + \frac{1}{C_4 s + \dots}}}
 \end{aligned}$$

2<sup>nd</sup> FORM

$$Z(s) = \frac{1}{C_1 s} + \frac{1}{\frac{1}{L_2 s} + \frac{1}{\frac{1}{C_3 s} + \frac{1}{L_4 s + \dots}}}$$

EXAMPLE FOR CAUER'S METHOD:

$$Z(s) = \frac{Z_1(s^2+1)(s^2+5)}{s s (s^2+3)(s^2+7)} \Rightarrow L_1 = 0$$

$$y_1 = \frac{1}{Z_1(s)} = \frac{1}{Z(s)} = \frac{5}{Z_1} s + \underbrace{\frac{5}{Z_1} \left( \frac{4s^3 + 16s}{s^4 + 6s^2 + 5} \right)}_{y_2}$$

R5

$$Z_2 = \frac{1}{y_2} = \frac{21}{5} \cdot \frac{1}{4} s + \frac{21}{5} \underbrace{\frac{2s^2+5}{4s^3+16s}}_{z_1(s)}$$

$$y_3 = \frac{1}{Z_3} = \frac{10}{21} s + \frac{5}{21} \frac{6s}{2s^2+5}$$

$$L_5 = \frac{21}{15}$$

$$Z_3 = \frac{42s^2+105}{20s^3+80s} \rightarrow y_3 = \frac{1}{Z_3} = \frac{20s^3+80s}{42s^2+105}$$

~~Handwritten scribbles~~


2nd Form  $C=1$

$$Z(s) = \frac{105 + 126s^2 + 21s^4}{105s + 50s^3 + 5s^5} = \frac{1}{s} + \frac{76s^2 + 16s^2}{105s + 50s^3 + 5s^5}$$


$$\frac{105s + 50s^3 + 5s^5}{76s^2 + 16s^4} = \frac{1}{\left(\frac{76}{105}\right)s} + \frac{\left(\frac{50}{19}\right)s^3 + 5s^2}{76s^2 + 16s^4}$$

$$L_2 = \frac{76}{105}$$

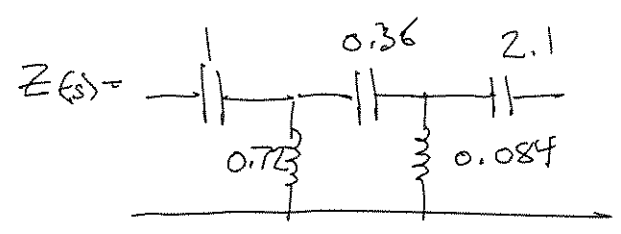- $C_3 = 0.36$
- $L_4 = 0.084$
- $C_5 = 2.1$



RICHARDS' FUNCTION

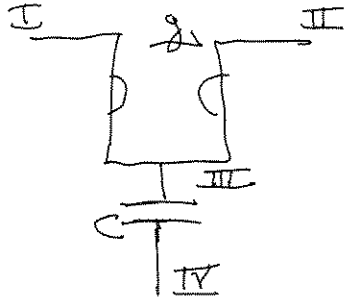

$$Y_{\text{PART}} = \begin{bmatrix} \frac{g^2}{sC} & g - \frac{g^2}{sC} \\ -g - \frac{g^2}{sC} & \frac{g^2}{sC} \end{bmatrix}$$

$$Y_L(s) = \frac{Y_{11} \cdot Y_{22} - \Delta y}{y_{11} - y_{12}} = g^2 \frac{\left(\frac{1}{sC} y_{11} - 1\right)}{\frac{g^2}{sC} - y_{11}}$$

$$Z_L(s) = \frac{1}{Y_L(s)} = \frac{g^2 Z_{IN}(s) - sC}{g^2 - g^2 sC Z_{IN}(s)}$$

$$\frac{\frac{1}{C} Z_{IN}(s) - s \left(\frac{1}{g^2}\right)}{\frac{1}{C} - s Z_{IN}(s)}$$

$$R(s) = \frac{KZ(s) - sZ(k)}{KZ(k) - sZ(s)}$$

$$K = \frac{1}{C}$$

$$Z(k) = \frac{1}{g^2}$$