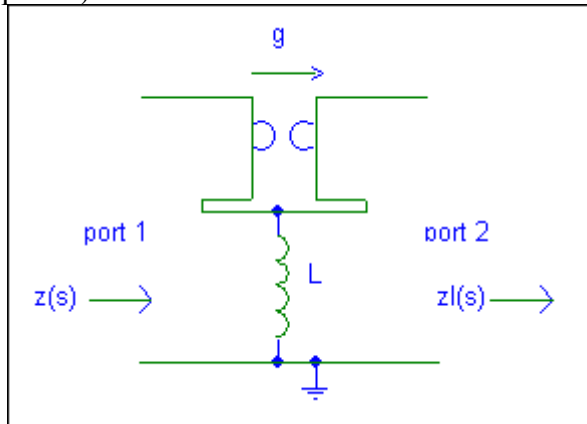


EENE 610
 Homework Problems for Grading, Set 3 (150 points)
 Due at class M 10/01/07
 Richards' functions and lossless synthesis

1.(100 points)



- a) Find the load impedance, $z_l(s)$, versus the input impedance, $z(s)=z_{in}(s)$, and the circuit parameters g and L .
- b) Find a Richards' type function, $z_r(s)$, in terms of k and $z(s)$ for the above circuit, relate to $z_l(s)$ and give g and L in terms of k and $z(k)$.
- c) Show that $k=1$ is a zero of the even part and choose $k=1$ to synthesize the following two impedances as cascades using the above circuit
 - c1) $z(s)=[s(s^2+5)/(s^2+3)]$
 - c2) $z(s)=(s^2+3)/[s(s^2+5)]$
- d) Repeat c1) using $k=2$ and again for $k=-1$
- e) Discuss the meaning of the results of this problem – consider passivity and minimality of the circuits and the differences in circuits for z and y .

2. (50 points)

- a) Find the zeros of the even part of the following functions
 - a1) $f(s)=(s+3)/(s+5)$
 - a2) $f(s)=(s+5)/(s+3)$
 - a3) $f(s)=s(s+3)/(s+5)$
 - a4) $f(s)=(s^2+s+1)/(s^2+2s+1)$
 - a5) $f(s)=(s^2-2s+1)/(s^2+2s+1)$
- b) Synthesize the admittance $y(s)=(s+3)/(s+5)$ using k as a zero of the even part and the Richards' type function of problem 1 above.