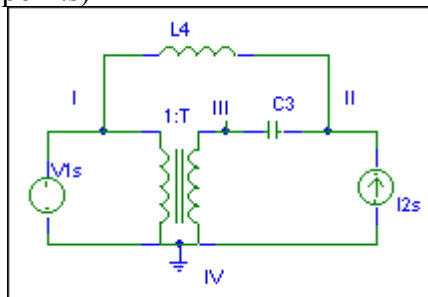


ENEE 610
 Homework Problems for Grading, Set 4 (200 points)
 Due at class W 10/10/07
 Semi-state & state equations, lossless synthesis and complex Richards' functions

1. (100 points)



- a) Draw the graph for the circuit numbering the nodes as shown, I to IV, and the branches by the element numbers (using 5 & 6 for the transformer). Orient the branches with arrows pointing down or to the right and choose the tree as branches 1 to 3.
 - b) Set up the semi-state equations choosing $u=[v_1s \ i_2s]^T$ and y as the voltage at node II with respect to ground.
 - c) Reduce the semi-state equations to state variable form.
 - d) Give the transfer function matrix, $T(s)$ for $Y(s)=T(s)U(s)$.
 - e) Determine if the entries of $T(s)$ are positive real for positive element values, C_3 , L_4 and T (the turns ratio).
2. (50 points)
 Synthesize $z(s)=[s(s^2+5)/(s^2+3)]$ by the Foster and Cauer circuits.

3. (50 points)

Show that the Richards' type function $y_R(s)=y(k)[ky(k)-sy(s)]/[ky(s)-sy(k)]$ is "positive" when $y(s)$ is positive real and $k=k_r+jk_i$ is a complex zero of the even part of $y(s)$ with $k_r=\text{Re}(k)>0$. Here "positive" is the "last" one of the defining three positive real conditions and means $\text{Re}(y_R(s))\geq 0$ for those $s=\sigma+j\omega$ for which $\sigma=\text{Re}(s)>0$. $\text{Re}(\cdot)$ means taking the real part; also $j=\sqrt{-1}$.