

ENEE 610
HW IV

Solutions for problem 1 & 2
Problem 3 solution is incomplete.

Problem 1

Part a) and b) are trivial. Let me know if you need the graph.

(c) Reducing Semi-State equations to Steady-State Form:

$$\begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \\ \dot{x}_5 \\ \dot{x}_6 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \\ C & 0 \\ 0 & -L \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} x_3 \\ x_4 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 0 & +1 \\ 0 & 0 & sC_3 & 0 & 0 & +1 \\ -1 & -1 & 0 & -sL_4 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & -T \\ -T & 1 & 1 & 0 & 0 & 0 \end{bmatrix} \underline{x}$$

$$+ \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 s \\ v_2 s \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} C & 0 \\ 0 & -L \end{bmatrix} \begin{bmatrix} \dot{x}_3 \\ \dot{x}_4 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & -1 \\ -1 & 1 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \\ x_5 \\ x_6 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \underline{u}$$

$$\begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & -1 \\ 0 & 0 & 0 & 0 & 1 & T \\ -T & -1 & -1 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \\ x_5 \\ x_6 \end{bmatrix} + \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \underline{u}$$

interchange columns 5 & 6 with 3 & 4

$$\Rightarrow \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 0 & 1 \\ 0 & 0 & 1 & T & 0 & 0 \\ -T & -1 & 0 & 0 & -1 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \\ x_5 \\ x_6 \end{bmatrix} + \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \underline{u}$$

$$\begin{bmatrix} x_1 \\ x_2 \\ x_5 \\ x_6 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ -1 & 0 \\ 0 & -T \\ 0 & 0 \end{bmatrix} \begin{bmatrix} x_3 \\ x_4 \end{bmatrix} + \begin{bmatrix} 1 & 0 \\ T & 0 \\ 0 & -T \\ 0 & 1 \end{bmatrix} \underline{u}$$

$$\begin{bmatrix} C_3 & 0 \\ 0 & -L_4 \end{bmatrix} \begin{bmatrix} \dot{x}_3 \\ \dot{x}_4 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & -1 \\ -1 & 1 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \\ x_5 \\ x_6 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \underline{u}$$

$$\Rightarrow \begin{bmatrix} C_3 & 0 \\ 0 & -L_4 \end{bmatrix} \begin{bmatrix} \dot{x}_3 \\ \dot{x}_4 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & -1 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_5 \\ x_6 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} x_3 \\ x_4 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \underline{u}$$

$$= \begin{bmatrix} 0 & 0 & 0 & -1 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 & 0 \\ -1 & 0 \\ 0 & -T \\ 0 & 0 \end{bmatrix} \begin{bmatrix} x_3 \\ x_4 \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 & -1 \\ -1 & 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ T & 0 \\ 0 & -T \\ 0 & 1 \end{bmatrix} \underline{u}$$

$$= \begin{bmatrix} 0 & -1 \\ -1 & 0 \end{bmatrix} \begin{bmatrix} x_3 \\ x_4 \end{bmatrix} + \begin{bmatrix} 0 & -1 \\ T-1 & 0 \end{bmatrix} \underline{u}$$

Assume $C_3, L_4 \neq 0 \Rightarrow$

$$\begin{bmatrix} C_3 & 0 \\ 0 & -L_4 \end{bmatrix}^{-1} = \frac{1}{-L_4 C_3} \begin{bmatrix} -L_4 & 0 \\ 0 & C_3 \end{bmatrix} = \begin{bmatrix} 1/C_3 & 0 \\ 0 & -1/L_4 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} \dot{x}_3 \\ \dot{x}_4 \end{bmatrix} = \begin{bmatrix} 1/C_3 & 0 \\ 0 & -1/L_4 \end{bmatrix} \begin{bmatrix} 0 & -1 \\ -1 & 0 \end{bmatrix} \begin{bmatrix} x_3 \\ x_4 \end{bmatrix} + \begin{bmatrix} 1/C_3 & 0 \\ 0 & -1/L_4 \end{bmatrix} \begin{bmatrix} 0 & -1 \\ T-1 & 0 \end{bmatrix} \underline{u}$$

$$\Rightarrow \begin{bmatrix} \dot{x}_3 \\ \dot{x}_4 \end{bmatrix} = \begin{bmatrix} 0 & 1/C_3 \\ -1/L_4 & 0 \end{bmatrix} \begin{bmatrix} x_3 \\ x_4 \end{bmatrix} + \begin{bmatrix} 0 & -1/C_3 \\ -1/L_4(T-1) & 0 \end{bmatrix} \underline{u}$$

$$\Rightarrow \left. \begin{array}{l} \dot{x} = Ax + Bu \\ y = Cx + Du \end{array} \right\}$$

← state - equations

$$y = v_2 \Rightarrow v_2 = v_1 - v_4$$

$$v_4 = r_4 s L_4 \quad ; \quad r_4 = x_4$$

$$\Rightarrow y = \begin{bmatrix} 0 & -sL_4 \end{bmatrix} \begin{bmatrix} x_3 \\ x_4 \end{bmatrix} + \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 s \\ r_2 s \end{bmatrix}$$

d) from lecture notes we have

$$T(s) = C(sI - A)^{-1}B + D$$

where

$$D = [1 \ 0]$$

$$C = [0 \ -sL_4]$$

$$A = \begin{bmatrix} 0 & 1/C_3 \\ -1/L_4 & 0 \end{bmatrix} ; \quad B = \begin{bmatrix} 0 & -1/C_3 \\ (T+1)/L_4 & 0 \end{bmatrix}$$

$$\Rightarrow T = \left[\begin{array}{c} T_1 \\ T_2 \end{array} \right] = \left[\begin{array}{c} \frac{s^2 C_3 L_4 + 1(1-T)}{(s^2 C_3 L_4 + 1)C_3} + 1 \\ \frac{-sL_4}{s^2 C_3 L_4 + 1} \end{array} \right]$$

e) For 1st entry poles are $\pm 1/\sqrt{-L_4 C_3} = \pm \frac{1}{j\sqrt{C_3 L_4}}$

We have the same poles for the second entry of $T(s)$ as well.

Since the poles are not in the RHP \Rightarrow 1st Condition is satisfied

Also the poles are simple, which are the order of \leq or lower.

For the 3rd Condition we need $\text{Re}\{\text{each entry}\} \gg 0 \quad \forall \omega \leq \infty$

for 1st entry.

$$\text{Real}\{T_1\} = \frac{1}{2} \left\{ T_1(s) + T_1^*(s) \right\} = \frac{1}{2} \left\{ \frac{(0+j\omega)^2 C_3 L_4 + (1-T)}{s^2 C_3 (L_4+1)C_3} + 2 + \frac{(0-j\omega)^2 C_3 L_4 + (1-T)}{s^2 C_3 (L_4+1)C_3} \right\}$$

No poles in RHP $\Rightarrow s \rightarrow j\omega$

$$= \frac{1}{2} \left\{ \frac{-\omega^2(C_3 L_4 + (1-T))(-\omega^2)}{s^2 C_3 (L_4 + 1)} + \frac{-\omega^2 C_3 L_4 (1-T)(-\omega^2)}{s^2 C_3 (L_4 + 1)} + 2(\omega^2) C_3 (L_4 + 1) \right\}$$

$$= \frac{1}{2} \left\{ \frac{2\omega^2 C_3 L_4 + 2\omega^4 (1-T) + 2\omega^2 C_3 (L_4 + 1)}{s^2 C_3 (L_4 + 1)} \right\}$$

\Rightarrow The numerator of the above is positive for $0 \leq \omega < \infty$

\Rightarrow 1st entry of $T(s)$ is Positive Real

for 2nd entry we have.

$$\operatorname{Re}\{T_2(s)\} = \frac{1}{2} \{T_2(s) + T_2^*(s)\} = \frac{1}{2} \left\{ \frac{-(\sigma + j\omega)L_4}{s^2 C_3 (L_4 + 1)} + \frac{-(\sigma - j\omega)L_4}{s^{*2} C_3 (L_4 + 1)} \right\}$$

$$= \frac{1}{2} \frac{L_4 (\sigma + j\omega)(\sigma - j\omega)^2 + (-\sigma + j\omega)(\sigma + j\omega)^2 L_4}{s^2 \cdot s^{*2} C_3 (L_4 + 1) L_4}$$

$$= \frac{1}{2} \frac{-(\sigma + j\omega)(\sigma^2 - 2j\omega\sigma - \omega^2) + (-\sigma + j\omega)(\sigma^2 + 2j\omega\sigma - \omega^2)}{s^2 \cdot s^{*2} C_3 (L_4 + 1) L_4}$$

$$= \frac{1}{2} \frac{(\sigma^3 - 2\sigma^2 j\omega + \sigma\omega^2 - j\omega^3 - \sigma\omega^2 + j\omega^3 - \sigma^3 - 2j\sigma^2\omega - \sigma\omega^2 + j\omega^3 - \sigma\omega^2 + j\omega^3 - 2\sigma\omega^2 - j\omega^3)(L_4)}{s^2 \cdot s^{*2} C_3 (L_4 + 1) L_4}$$

$$= \frac{1}{2} \left(\frac{(-2\sigma^3 - 3\sigma\omega^2)L_4}{(\cdot)} \right) \Rightarrow \text{This is negative for all } 0 \leq \omega < \infty$$

\Rightarrow Second Term in $T(s)$ is not real Positive


Problem 2

Problem 2)

$$Z(s) = s(s^2 + 5) / (s^2 + 3)$$


1st Foster Method: $Z(s) = \frac{s^2 + 5s}{s^2 + 3} = s + \frac{2s}{s^2 + 3}$

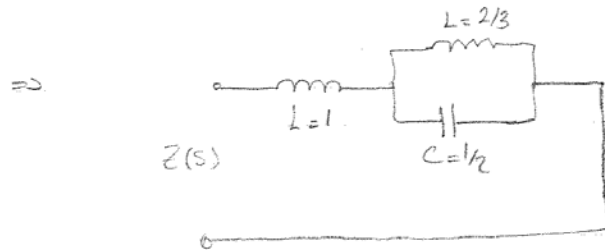So we have $K_{\infty} = 1$, $2K_2 = 2$, $\omega_2^2 = 3$



So for 2nd Foster Method:
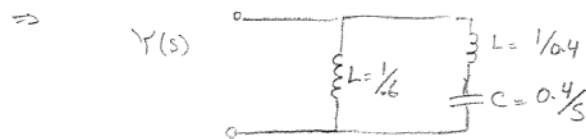
$$Y(s) = \frac{1}{Z(s)} = \frac{s^2 + 3}{s(s^2 + 5)} = \frac{.6}{s} + \frac{.4s}{s^2 + 5}$$



For Cover Method:


1st Cover Method:

$$\text{we have } Z(s) = \frac{s(s^2+5)}{s^2+3} = s + \frac{2s}{s^2+3}$$

$$\text{so } \frac{2s}{s^2+3} = Z_1 \quad \& \quad L_1 = 1$$

$$\Rightarrow s_0, \quad Y_1(s) = \frac{1}{Z_1} = \frac{s^2+3}{2s} = \frac{1}{2}s + \frac{3}{2s} \Rightarrow C = \frac{1}{2}$$
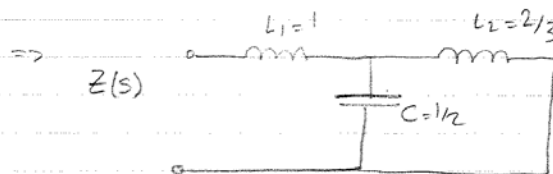
$$\text{and } Z_2 = \frac{1}{Y_2} = \frac{2s}{3} \Rightarrow L_2 = \frac{2}{3}$$



For 2nd Cover Method:


$$Z(s) = \frac{s(s^2+5)}{s^2+3} \Rightarrow Y(s) = \frac{s^2+3}{s^2+5s}$$

$$\Rightarrow Y(s) = \frac{3}{5s} + \frac{(2/5)s^2}{s^2+5s} \Rightarrow L = 3/5$$

$$\text{So } Z = \frac{s^2+5s}{2/5s^2} = \frac{25s}{2s} + \frac{s}{(2/5)} \Rightarrow C = 25/2$$

$$\Rightarrow Y = \frac{2/5}{s} \Rightarrow L_2 = 2/5$$

1. The circuit is a parallel combination of a capacitor and a series combination of a capacitor and an inductor.

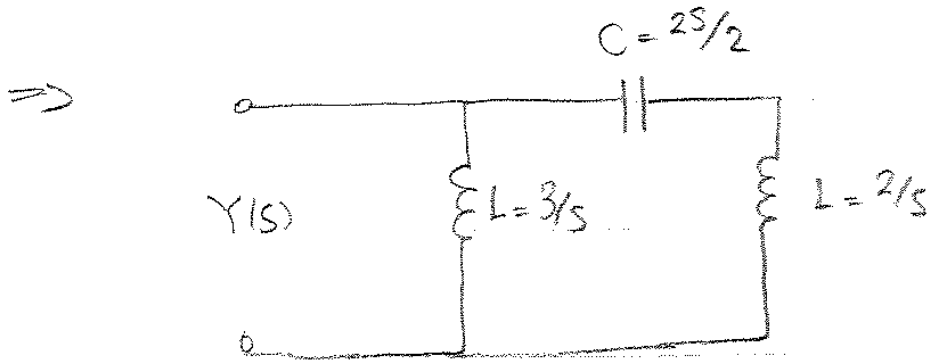

Problem 3

Suggestion: I will start by writing the real part of the ratio as the ratio of the real-parts PLUS the ratio of the imaginary parts. Then decompose each term into its REAL and IMAG. I am not sure if this leads to the solution!