

303 Fall 2008 – Midterm Exam Makeup – Take Home

Due in class Tuesday 11/18/08;

Open book open notes; all work your own which your signature guarantees

Maximum points:

- a) 10 if greater than 65 was obtained on the midterm
- b) 70 maximum for the total of midterm + midterm-makeup if less than 66 was obtained on the midterm

1. (up to 25 points) A given transistor circuit has the (normalized) transfer function
 $[V_o(s)/V_i(s)] = T(s) = 5(s^2 - 4s + 3)/(s^2 + 4s + 3)$
 - a) Give the zeroes and poles of $T(s)$ and plot them in the s -plane
 - b) If, for $-\infty < t < +\infty$, $v_i(t) = 0.03e^{j2t}$ give $v_o(t)$.
 - c) Using the result of b) give $v_o(t)$ when $v_i(t) = 0.03\sin(2t)$.
2. (up to 25 points) The following is an equivalent circuit for a source follower as a 2-port for which the 2×2 admittance matrix $Y(s)$ is desired.
 - a) Find $Y(s)$.
 - b) From $Y(s)$ give the input resistance $V_1(s)/I_1(s)$ under open circuit load conditions, that is, when $I_2 = 0$. Repeat to find, also when $I_2 = 0$, the transfer function $T(s) = V_2(s)/V_1(s)$.

