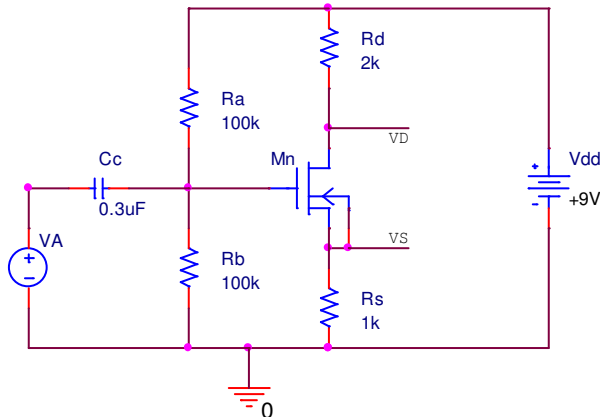


For these problems the transistors should again be those of the 4007 package.

1. The following circuit is Figure 1 of Lab 6 where it is assumed that  $C_c$  is large enough to be considered infinite.



- a) Find the Q point and with it the  $g_m$  and  $g_o$  of  $M_n$ . Ignoring all parasitic capacitors, draw the small signal equivalent circuit and find the small signal gains  $v_d/v_a$  and  $v_s/v_a$ .
  - b) Place a 0.3uF capacitor,  $C_s$ , in parallel with  $R_s$  and assume that it is the only effective capacitor in the circuit. Find the resulting small signal gains (as functions of complex frequency  $s$ ) and give their poles and zeros, comparing those in  $v_d/v_a$  with those of  $v_s/v_a$ .
2. In the above circuit replace the NMOS transistor by a PMOS,  $M_p$ , (with its bulk connected to its source) and interchange the resistors  $R_s$  and  $R_d$  (so they will still be tied to the source and drain); also relabel so that  $V_D$  is at the drain and  $V_S$  at the source).
    - a) Draw the new schematic.
    - b) Repeat Problem 1a) above for the new schematic. Compare with the results of Problem 1a).
    - c) Repeat Problem 1b) above for the new schematic (placing  $C_s$  again across the source resistor  $R_s$ ).