
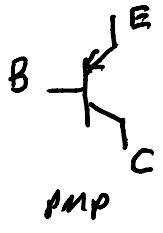


BJT = bipolar junction transistor

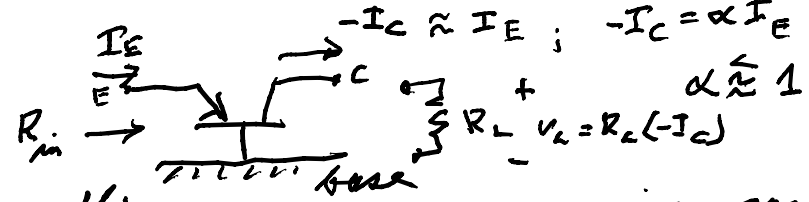

transistor = transfer resistor




$-I_C \approx I_E$; $-I_C = \alpha I_E$
 $\alpha \approx 1$
 $v_o = R_L (-I_C)$




(small) large gives power gain

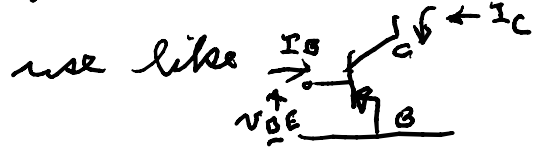KCL, $0 = I_E + I_C + I_B \Rightarrow I_B = \text{small}$





gives much bigger power out

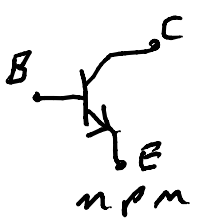

exponential

CMOS = complementary metal oxide silicon

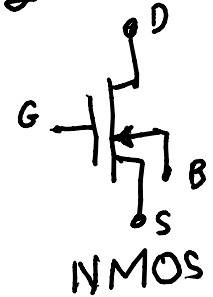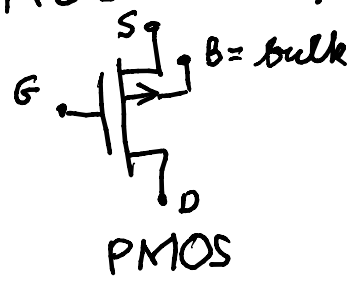

M in spice device

polynomial