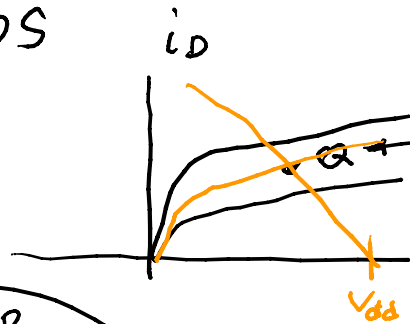



Biasing of MOS

EE 303 Th 09/18/08

NMOS





choose V_{DS} chosen fixed
 $V_{GS}|_Q = \frac{R_b}{R_a + R_b} V_{DD}$
 $I_Q = \frac{1}{1 + (\frac{R_a}{R_b})} \cdot V_{DD}$

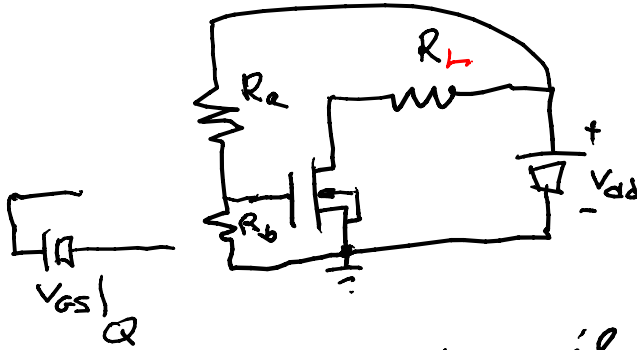

to avoid loading a signal source choose R_a parallel R_b to be large

$$R_{11} = \frac{R_a R_b}{R_a + R_b} = \frac{R_a}{1 + (R_a/R_b)} \Rightarrow \text{choose } R_a \text{ very large}$$

large

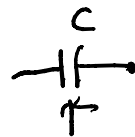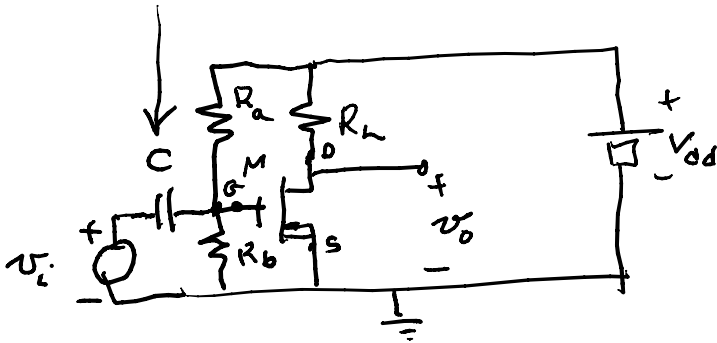

$$Z_c = \frac{1}{sC} \Rightarrow Z_c(j\omega) = \frac{-j}{\omega C}$$


at a fixed ω ; $|Z_c| = \frac{1}{\omega C}$ is small if C is large


at bias $\omega = 0$ (at DC)

$$\text{so } |Z_c(0)| = \infty$$

interested in $\frac{V_o}{V_i}(s)$

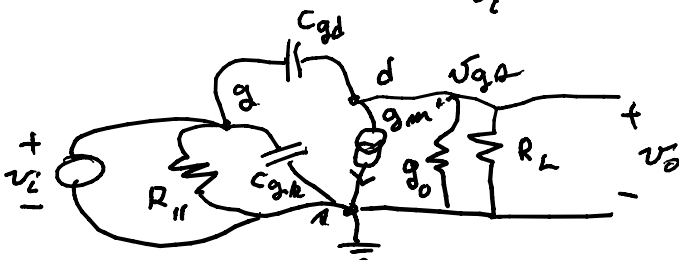here battery \Rightarrow short
 Capacitor \Rightarrow open short
 M \rightarrow small signal equivalent



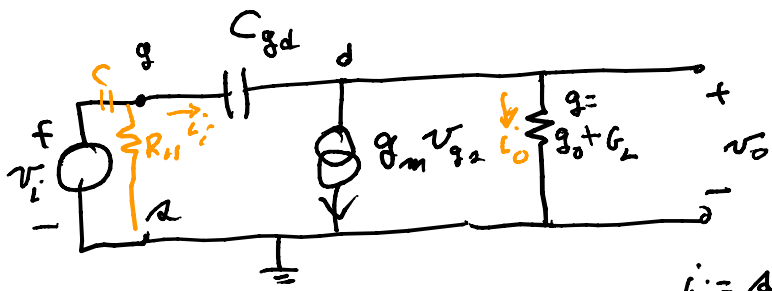

$$i_o = g v_o$$

$$i_o = i_i - g_m v_{gs}$$

$$= i_i - g_m v_i$$



$$i_i = s C_{gd} \cdot [v_i - v_o]$$

$$g v_o = i_o = i_i - g_m v_i$$

$$= s C_{gd} (v_i - v_o) - g_m v_i \Rightarrow \frac{v_o}{v_i}$$

$$g v_o + s C_{gd} v_o = (s C_{gd} - g_m) v_i \Rightarrow \frac{v_o}{v_i} = \frac{(s C_{gd} - g_m)}{(g_o + G_L) + s C_{gd}}$$
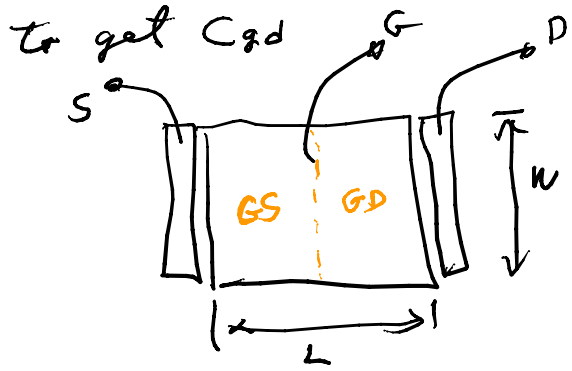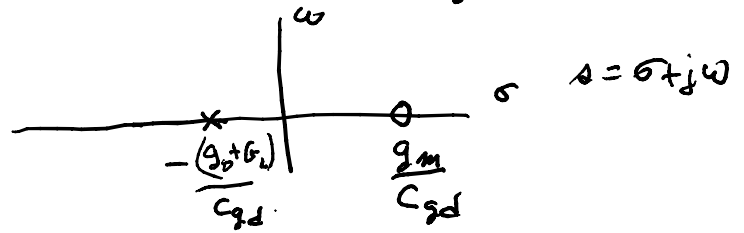
$$\frac{v_o}{v_i} = \frac{s - \frac{g_m}{C_{gd}}}{s + \frac{g_o + G_L}{C_{gd}}}$$





$$C_{\text{capacitance}} = \frac{\epsilon A}{d} = \epsilon_{\text{SiO}_2} \frac{W L}{2} \cdot \frac{1}{t_{\text{ox}}}$$


thickness

Note $e^{st} = e^{\sigma t + j\omega t} = e^{\sigma t} \cdot e^{j\omega t} = e^{\sigma t} (\cos(\omega t) + j\sin(\omega t))$


Current sources:

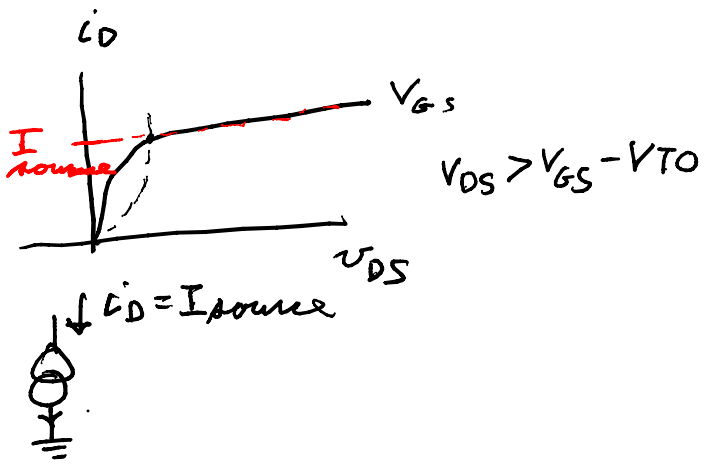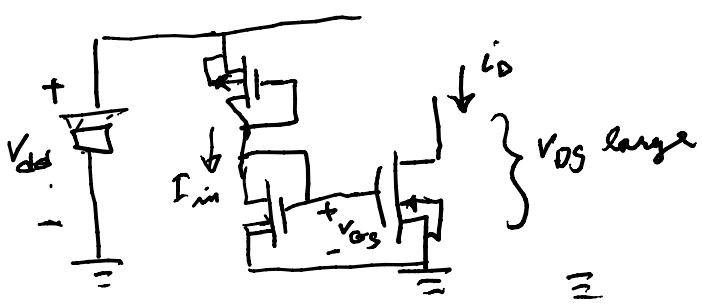

Differential pair

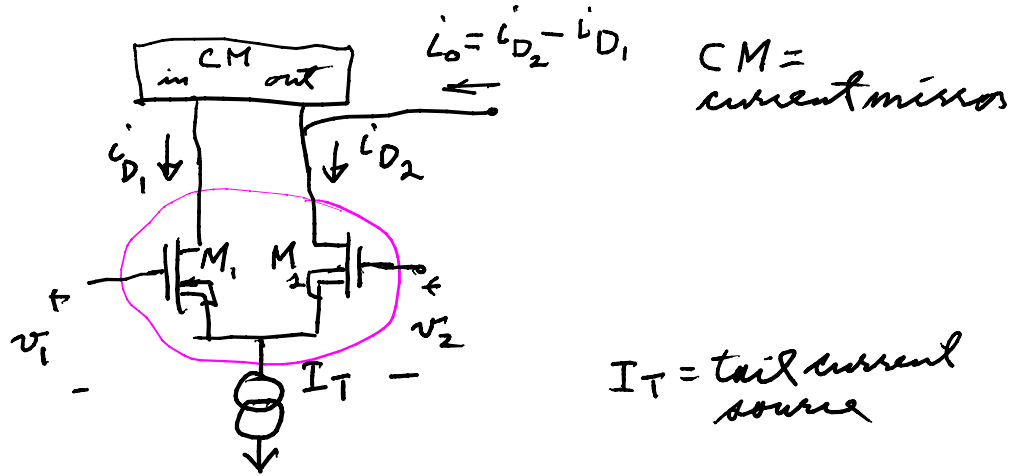
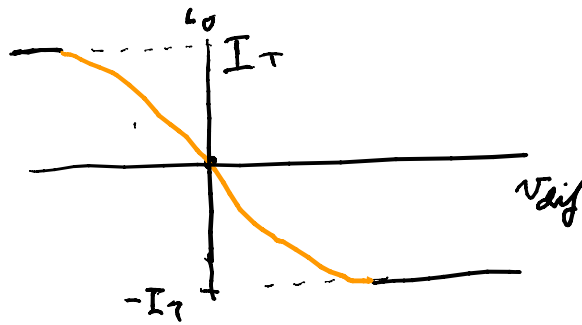
$$I_T = i_{D1} + i_{D2} \quad ; \quad v_{dif} = v_1 - v_2$$



how to make the current mirrors

