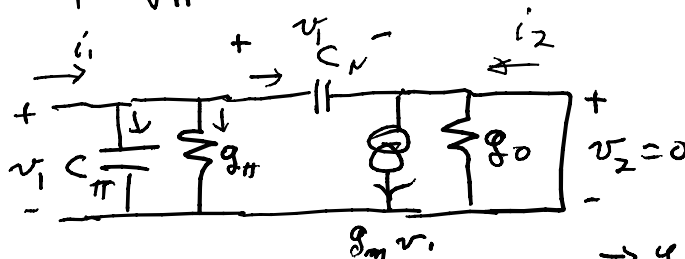


To get the Y matrix:  
appendix b

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = Y \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$


$$i_1 = y_{11} v_1 + y_{12} v_2 \Rightarrow y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}$$



$$i_1 = i_{Cp} + i_{gn} + i_{Cp} = sCp v_1 + gn v_1 + sCp v_1$$

$$\Rightarrow y_{11} = gn + s(Cp + Cp)$$

$$y_{12} = \frac{i_1}{v_2} \Big|_{v_1=0}$$

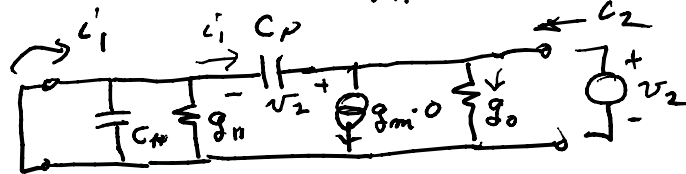


$$i_1 = -sCp \cdot v_2 \text{ as } i_{Cp} = i_{gn} = 0 \text{ since shorted}$$

$$y_{12} = -sCp$$

$$i_2 = go \cdot v_2 + sCp v_2$$

$$y_{22} = \frac{i_2}{v_2} \Big|_{v_1=0} = go + sCp$$

$$y_{21} = \frac{i_2}{v_1} \Big|_{v_2=0}$$

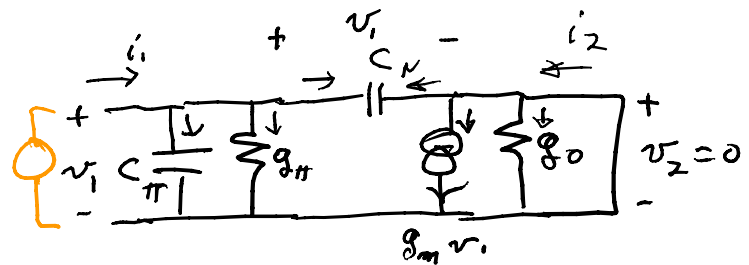


$$i_2 = -sCp v_1 + gm v_1$$

$$y_{21} = gm - sCp$$


~~$$i_2 = y_{21} v_1 + y_{22} v_2$$~~
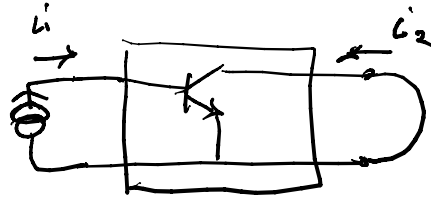
$$Y = \begin{bmatrix} gn + s(Cp + Cp) & -sCp \\ gm - sCp & go + sCp \end{bmatrix}$$



$$\left. \frac{i_2}{i_1} \right|_{v_2=0} = \left. \frac{i_2/v_1}{i_1/v_1} \right|_{v_2=0} = \frac{g_{21}}{g_{11}}$$
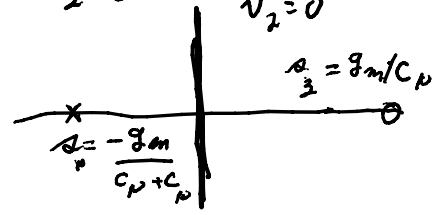
$$\frac{i_2}{i_1} = \frac{g_{21}}{g_{11}} = \frac{g_m - sC_p}{g_{\pi} + s(C_p + C_{\pi})} \approx \beta(s)$$



$$s = j\omega; \quad \beta(j\omega) = \frac{g_m - jC_p\omega}{g_{\pi} + j\omega(C_p + C_{\pi})}$$

$$|\beta(j\omega)| = \frac{\sqrt{g_m^2 + (C_p\omega)^2}}{\sqrt{g_{\pi}^2 + \omega^2(C_p + C_{\pi})^2}}$$

for normal use  
 $C_p\omega \ll g_m$

$$g_m = \frac{|I_c|}{V_T}$$



$$g_{\pi} = \frac{|I_c|}{\beta_0 V_T} = \frac{g_m}{\beta_0}$$

$$\approx \frac{\sqrt{(g_m/g_{\pi})^2}}{\sqrt{1 + \omega^2(C_p + C_{\pi})^2/g_{\pi}^2}} = \frac{\beta_0}{\sqrt{1 + \omega^2(C_p + C_{\pi})^2/g_{\pi}^2}}$$


look for the frequency  $\omega_T$  for which  $\left| \frac{i_2}{i_1}(j\omega_T) \right| = 1$   
means the transistor becomes ineffective:

$$1 \approx \frac{\beta_0 \cdot g_{\pi}}{\omega(C_p + C_{\pi})} \Rightarrow \omega_T = \frac{\beta_0 \cdot g_{\pi}}{C_p + C_{\pi}} = \frac{g_m}{C_p + C_{\pi}}$$

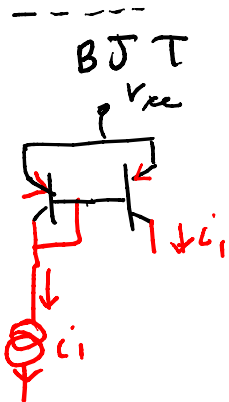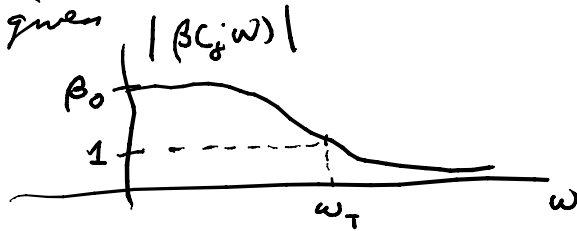on data sheets  $f_T = \frac{\omega_T}{2\pi}$  is given



BJT differential pair

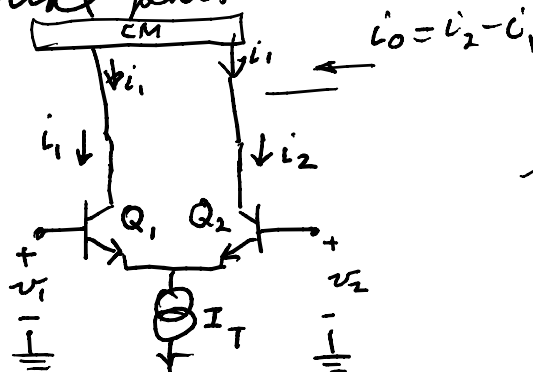

bias in the forward active region

$$-i_{E_1} - i_{E_2} = I_T, \quad i_1 = -\alpha i_{E_1}, \quad i_2 = -\alpha i_{E_2}$$

$$\frac{I_T}{\alpha} = i_1 + i_2; \quad i_1 = \alpha I_{ES} e^{v_{BE_1}/V_T}$$

$$i_2 = \alpha I_{ES} e^{v_{BE_2}/V_T}$$

$$i_2 - i_1 = i_{out} = \alpha I_{ES} (e^{v_{BE_2}/V_T} - e^{v_{BE_1}/V_T})$$

$$= \alpha I_{ES} e^{v_{BE_2}/V_T} (1 - e^{(v_{BE_1} - v_{BE_2})/V_T})$$

$$\alpha I_T = \alpha I_{ES} (e^{v_{BE_2}/V_T} + e^{v_{BE_1}/V_T}) = \alpha I_{ES} e^{v_{BE_2}/V_T} (1 + e^{\frac{v_{BE_1} - v_{BE_2}}{V_T}})$$

$$v_d = v_{BE_1} - v_{BE_2} \Rightarrow \frac{i_{out}}{I_T} = \frac{1 - e^{v_d/2V_T}}{1 + e^{v_d/2V_T}} = \frac{e^{v_d/2V_T} (e^{-v_d/2V_T} - e^{v_d/2V_T})}{e^{v_d/2V_T} (e^{-v_d/2V_T} + e^{v_d/2V_T})}$$

$$i_{out} = -I_T \cdot \tanh(v_d/2V_T)$$

