

#1.  $v_o = R i_{D_{Q1}} - R i_{D_{Q2}} = R (i_{D_{Q1}} - i_{D_{Q2}}) = R (-\alpha I_T \tanh(v_o / (2V_T)))$   
 (from class notes  
 or p.707 from  $\alpha((7.72) - (7.73))$ )  
 $\therefore v_o = -\alpha R I_T \tanh\left(\frac{v_o}{2V_T}\right)$

#2.  $M_1$  is in saturation;  $V_{GS} = V_{DS} = V_1 = 3V$

$\therefore I_{D1} = \frac{K P_n W}{2 L} (V_{GS} - V_{Tn})^2 (1 + \lambda V_{DS})$   
 $= \frac{20.54 \times 10^{-6}}{2} \cdot \frac{144}{8} (3 - 1.3)^2 (1 + 15 \times 10^{-3} \times 3) = 184.986 \times 10^{-6} (1.7)(1.045)$   
 $= 0.329 \text{ mA}$

as  $v_R = V_{CC} - V_1 = 6 - 3 = 3 = R \cdot I_{D1} \Rightarrow R = 3 / 0.329 \times 10^{-3}$

a)  $\Rightarrow R = 9.12 \text{ k}\Omega$

b) as  $M_2 = M_1$ , when  $V_{out} = V_1$ ,  $I_{out} = I_{D1} = 0.329 \text{ mA}$   
 When  $V_{out} = 4 = V_{DS} M_2 \Rightarrow I_{out} = I_{D1} \times \left[ \frac{1 + \lambda V_{out}}{1 + \lambda V_1} \right] = I_{D1} \times \left( \frac{1 + 0.060}{1 + 0.045} \right)$

$\therefore I_{out} |_{V_{out}=3} = 0.329 \text{ mA} = I_{D1} (1.014)$

$I_{out} |_{V_{out}=4} = 0.334 \text{ mA}$

#3.  $s^2 + 2s + 3 = 0 \Rightarrow p_{1,2} = -1 \pm \frac{1}{2} \sqrt{4 - 4 \times 3} = -1 \pm j\sqrt{2} = \text{poles}$

$s^2 - 2s + 3 = 0 \Rightarrow z_{1,2} = +1 \pm j\sqrt{2} = \text{zeros}$

a)  $v_o(t) = T(s) v_i(t) = \frac{5(-2 - 2s + 3)}{(s - 2 + 2s + 3)} e^{j2t}$   
 $= 5 \left( \frac{1 - j4}{1 + j4} \right) e^{j2t} = 5 e^{j(2t - 2 \arctan(4/1))}$   
 $2 \times 76^\circ = 2.66 \text{ rad}$


b)  $= 5 e^{j(2t - 2.66)}$  as  $\left| \frac{1 - j4}{1 + j4} \right| = 1$  (this is all-pass)

as  $e^{j2t} = \cos(2t) + j \sin(2t) \Rightarrow \cos(2t) = \frac{e^{j2t} + e^{-j2t}}{2}$

By linearity & real coefficients of  $T(s)$

$v_o(t) = \frac{5}{2} e^{j(2t - 2.66)} + \frac{5}{2} e^{-j(2t - 2.66)}$

c)  $= 5 \cos(2t - 2.66)$

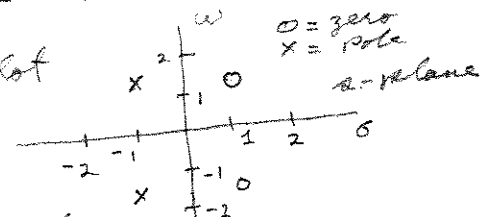

4.  $v_o = R_s i_{R_s}$  where by KCL:  $i_{R_s} = g_m v_{gs} + i_{R_g} + i_{C_g}$

$$= g_m v_{gs} + G_g v_{gs} + \alpha C_g v_{gs}$$

$$= (g_m + G_g + \alpha C_g) v_{gs}$$

2 by KVL:  $v_{gs} = v_i - v_o$  where  $G_g = \frac{1}{R_g}$

$\therefore v_o = R_s (g_m + G_g + \alpha C_g) [v_i - v_o]$


$$\Rightarrow (1 + R_s [g_m + G_g + \alpha C_g]) v_o = R_s (g_m + G_g + \alpha C_g) v_i$$

$$\Rightarrow \frac{v_o}{v_i} = \frac{R_s (C_g \alpha + [g_m + G_g])}{R_s (C_g \alpha + [g_m + G_g + G_s])} \quad \text{where } G_s = \frac{1}{R_s}$$

Pole:  $p = - [g_m + G_g + G_s] / C_g$

zero:  $z = - [g_m + G_g] / C_g$

here  $|z| < |p| \Rightarrow$

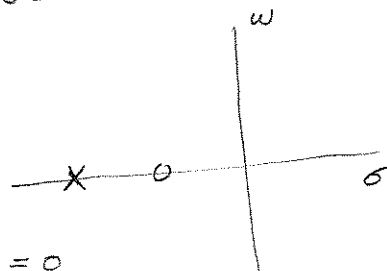

The low frequency gain is for  $\alpha = 0$

$$\frac{v_o(0)}{v_i} = \frac{g_m + G_g}{g_m + G_g + G_s} = \frac{g_m + G_g}{g_m + G_g + 1/R_s} = \frac{R_s (g_m + G_g)}{R_s (g_m + G_g) + 1} < 1$$

$$= g_m R_d \left( \frac{1 + G_g/g_m}{1 + R_s (g_m + G_g)} \right) \text{ if } R_s = R_d$$

Here the source follower gain is less than 1 while the grounded source amplifier gain  $g_m R_d$  can be large. In all cases the two gains differ by the factor  $\left( \frac{1 + G_g/g_m}{1 + R_s (g_m + G_g)} \right)$