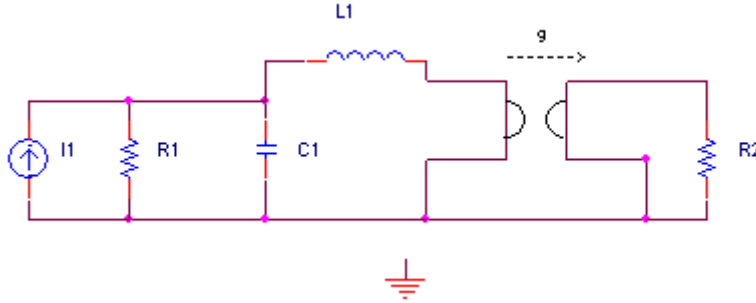


C in 2. corrected to [1 0 0] 10/27/08

1. For the following circuit set up the indefinite admittance matrix (excluding the current source). Then ground the bottom line of the circuit after which eliminate the two right-most (upper) nodes to get the input admittance $Y(s)$ seen by the current source.



2. Consider the state equations

$$\frac{dx}{dt} = \begin{bmatrix} -(2\zeta\omega_0 + \lambda) & 1 & 0 \\ -(2\zeta\omega_0\lambda + \omega_0^2) & 0 & 1 \\ -\lambda\omega_0^2 & 0 & 0 \end{bmatrix} x + \begin{bmatrix} k \\ 2k\xi\rho \\ k\rho^2 \end{bmatrix} u = Ax + Bu$$

$$y = [1 \ 0 \ 0]x = Cx$$

$\zeta, \xi, \lambda, \rho, \omega_0, k$ all real and positive;

$x = x(t)$, a real - valued 3 - vector function

- Find $(sI-A)^{-1}$
- Find the (scalar) transfer function $T(s)=C(sI-A)^{-1}B$ and give its poles and zeros (note that $s+\lambda$ is a denominator factor).
- Assume that $T(s)=V_{out}/V_{in}=Y(s)/U(s)$ and draw an op-amp-RC circuit to realize this.
- Find a transformation P such that $A_p=PAP^{-1}$ is of the form

$$A_p = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -a_0 & -a_1 & -a_2 \end{bmatrix}. \text{ Give the new B and C matrices, } B_p \text{ and } C_p.$$