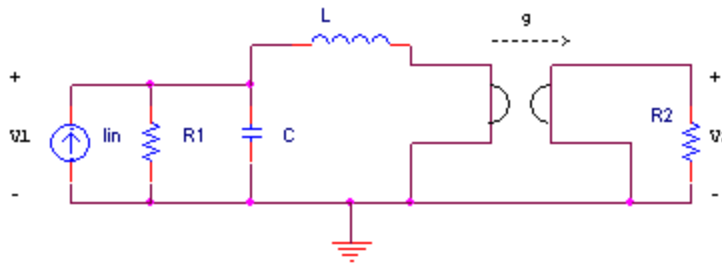


1. For the following circuit the transfer function of interest is $V_2/I_{in}(s)$
 - a. Draw the graph for the circuit with separate (terminal) branches for I_{in} and V_2 .
 - b. Draw the adjoint circuit and give the components which go into the terminal branches assuming that ΔV_2 is desired.
 - c. Give the formula for $\Delta V_2/\Delta R_1$ in terms of voltages and currents in the network and its adjoint.
 - d. Analyze the two networks to evaluate $\Delta V_2/\Delta R_1$ in terms of circuit elements and I_{in} .

e. Give the sensitivity $S_{R_1}^{V_2/I_{in}} = \frac{R_1}{V_2/I_{in}} \frac{d(V_2/I_{in})}{dR_1}$



2. Repeat problem 1 above to find
 - a) $S_C^{V_2/I_{in}} = \frac{C}{V_2/I_{in}} \frac{d(V_2/I_{in})}{dC}$
 - b) $S_{R_1}^{V_1/I_{in}} = \frac{R_1}{V_1/I_{in}} \frac{d(V_1/I_{in})}{dR_1}$
 - c) $S_g^{V_2/I_{in}} = \frac{g}{V_2/I_{in}} \frac{d(V_2/I_{in})}{dg}$