

$$v_b = e^T v_t, \quad i_b = \sigma^T i_r$$

$$b = t + l$$

$$p = 0 = v_b^T i_b = \text{total power from outside the circuit}$$


$$= (e^T v_t)^T i_b = (v_t^T e^T) \cdot i_b = v_t^T \cdot \underbrace{e \cdot i_b}_0 = 0$$

$0 = e i_b$ ;  $e$  is  $t$  rows  
 $b$  columns } =  $t \times b$  matrix  
 $\Downarrow$   
 $\sigma_t \Rightarrow$  KCL for each tree branch

$0$  as  $v_t$  is arbitrary  
 (for the graph with any elements giving it)


$$v_b = [v_1, v_2, v_3, v_4, v_5]^T$$

$$v_t = [v_1, v_2]^T$$

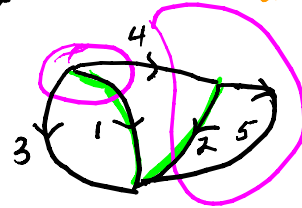

$$\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ 0 & 1 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}; \quad e = \begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ 0 & 1 & 0 & -1 & 1 \end{bmatrix}$$

gyrator  $\Rightarrow$  2-port

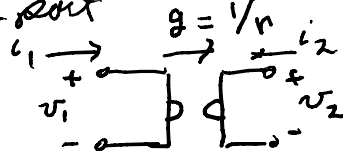

$r =$  gyration resistance

$$z = -z^T = \begin{bmatrix} 0 & -r \\ r & 0 \end{bmatrix}, \quad \begin{bmatrix} 0 & -r \\ r & 0 \end{bmatrix}^T = \begin{bmatrix} 0 & r \\ -r & 0 \end{bmatrix}$$


$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & -r \\ r & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \Rightarrow v = z i$$

$$z^{-1} = y = \frac{1}{r^2} \begin{bmatrix} 0 & r \\ -r & 0 \end{bmatrix} = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix}$$


Telepen introduced  
 @ Philips labs

$$z y = \begin{bmatrix} 0 & -r \\ r & 0 \end{bmatrix} \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} = \begin{bmatrix} -r(-g) = 1 & 0 \\ 0 \cdot r - 0 \cdot g = 0 & r \cdot g = 1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$
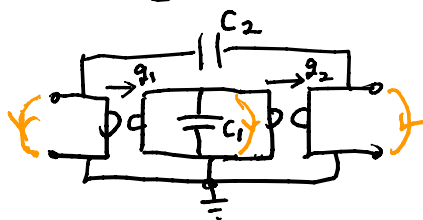
$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Rightarrow \begin{aligned} i_2 &= -g v_1 \\ i_1 &= g v_2 \end{aligned} \Rightarrow \text{VCCS (= OTA)}$$




$$i = g v_j$$

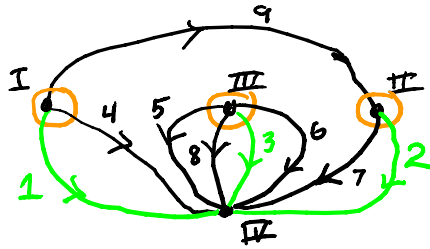

$C$  is  $3 \times 9$   
KCL

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{matrix} 4 & 5 & 6 & 7 & 8 & 9 \\ 1 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 & -1 \\ 0 & 1 & 1 & 0 & 1 & 0 \end{matrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \\ i_7 \\ i_8 \\ i_9 \end{bmatrix} ; v_b = e \cdot v_t$$

$$Y_{b \times b} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \Rightarrow i = Y_{b \times b} \cdot v$$

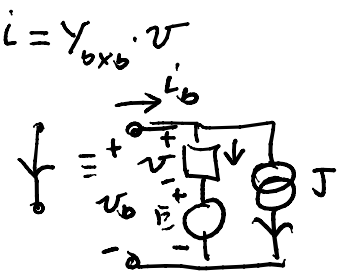

$$\begin{cases} v_b = v + E \\ i_b = i + J \end{cases} \Rightarrow \begin{cases} v = v_b - E \\ i = i_b - J \end{cases}$$

here in this example  $E = 0_9 = 9$ -vector of zeros

$$J = \begin{bmatrix} j_1 \\ j_2 \\ j_3 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$i = Y_{b \times b} v = i_b - J$$

$$= Y_{b \times b} v_b = i_b - J$$

multiply by  $C \Rightarrow$

$$C Y_{b \times b} v_b = C \cdot i_b - C \cdot J = 0_3 - e J = - \begin{bmatrix} j_1 \\ j_2 \\ j_3 \end{bmatrix}$$

$$C Y_{b \times b} e^T v_t = - \begin{bmatrix} j_1 \\ j_2 \\ j_3 \end{bmatrix} \Rightarrow Y_{t \times 3} = C Y_{b \times b} e^T = Y_{nodal}$$

$$v_t = Y_{nodal}^{-1} \cdot i_{intra\ nodes} = Y_{nodal}^{-1} \cdot (-j) ; v_b = e^T v_t$$

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{matrix} 4 & 5 & 6 & 7 & 8 & 9 \\ 1 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 & -1 \\ 0 & 1 & 1 & 0 & 1 & 0 \end{matrix} \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 & g_1 & 0 \\ -g_1 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 & 0 & 0 \\ 0 & g_2 & 0 \\ -g_2 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 0 & 1 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 & 9 \\ 0 & 0 & 0 & 0 & g_1 & 0 & 0 & 0 & AC_2 \\ 0 & 0 & 0 & 0 & 0 & -g_2 & 0 & 0 & -AC_2 \\ 0 & 0 & 0 & -g_1 & 0 & 0 & g_2 & AC_1 & 0 \end{bmatrix} \times \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ \hline 1 & 0 & 0 \\ 0 & 0 & 1 \\ 0 & 0 & 1 \\ 0 & 0 & 1 \\ 0 & 0 & 1 \\ 1 & -1 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} AC_2 & -AC_2 & g_1 \\ -AC_2 & AC_2 & -g_2 \\ \hline -g_1 & g_2 & AC_1 \end{bmatrix} = Y_{ext} \quad \begin{bmatrix} -j_1 \\ -j_2 \\ -j_3 \end{bmatrix} = - \begin{bmatrix} I_{ports} \end{bmatrix}$$

From the 2-port set  $j_3 = 0$ ; eliminates inner node


$$\begin{bmatrix} i_{1, port} \\ i_{2, port} \\ 0 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ \hline Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v_{1t} \\ v_{2t} \\ v_{3t} \end{bmatrix} \Rightarrow \begin{bmatrix} i_{1t} \\ i_{2t} \end{bmatrix}_{port} = Y_{11} \begin{bmatrix} v_{1t} \\ v_{2t} \end{bmatrix}_t + Y_{12} v_{3t}$$

$$\Rightarrow v_{3t} = Y_{22}^{-1} (-Y_{21}) \begin{bmatrix} v_{1t} \\ v_{2t} \end{bmatrix}_t \Rightarrow \begin{bmatrix} i_{1t} \\ i_{2t} \end{bmatrix}_{port} = \begin{bmatrix} Y_{11} - Y_{12} Y_{22}^{-1} Y_{21} \end{bmatrix} \begin{bmatrix} v_{1t} \\ v_{2t} \end{bmatrix}_{port}$$

$$Y_{2port} = Y_{11} - Y_{12} Y_{22}^{-1} Y_{21} \\
 = \begin{bmatrix} AC_2 & -AC_2 \\ -AC_2 & AC_2 \end{bmatrix} - \begin{bmatrix} g_1 \\ -g_2 \end{bmatrix} \frac{1}{AC_1} \begin{bmatrix} -g_1 & g_2 \end{bmatrix}$$

$$= \begin{bmatrix} g_2 & -g_2 \\ -g_2 & g_2 \end{bmatrix} = \begin{bmatrix} -g_1^2/g_2 & +g_1g_2/g_2 \\ g_1g_2/g_2 & -g_2^2/g_2 \end{bmatrix}$$
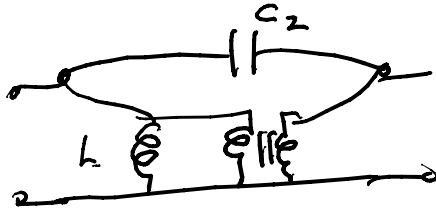
$$= g_2 \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} + \frac{1}{g_2} \begin{bmatrix} g_1^2 & -g_1g_2 \\ -g_1g_2 & g_2^2 \end{bmatrix} = Y_{2 \text{ port}}$$



here

