

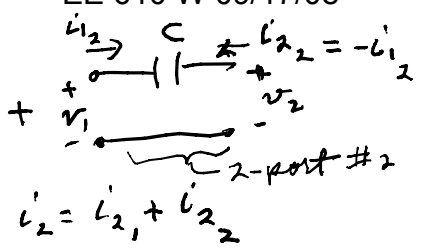


$i = Yv$

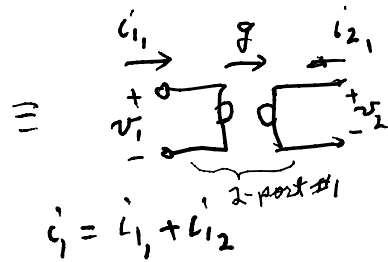

$$i = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = Y \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = Yv = \begin{bmatrix} i_1 + i_2 \\ i_2 + i_2 \end{bmatrix}$$

$$= Y_1 v + Y_2 v = (Y_1 + Y_2)v$$

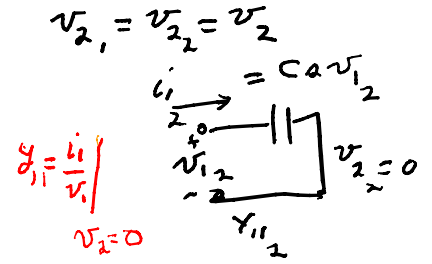


$$Y_1 = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix}; \quad Y_2 = \begin{bmatrix} sC & -sC \\ -sC & sC \end{bmatrix}$$

$y_{12} = i_2 / v_2 \Big|_{v_1=0}$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Rightarrow y_{11} = i_1 / v_1 \Big|_{v_2=0}$$

$$y_{12} = i_1 / v_2 \Big|_{v_1=0} = -sC$$

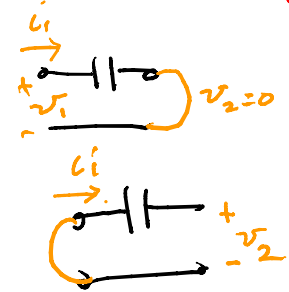

$$\Rightarrow Y = Y_1 + Y_2 = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} + \begin{bmatrix} sC & -sC \\ -sC & sC \end{bmatrix}$$

$$= \begin{bmatrix} sC & g - sC \\ -g - sC & sC \end{bmatrix}$$

$$Z = Y^{-1} = \frac{1}{\det Y} \begin{bmatrix} sC = (1,1) \text{ cofactor} & -g + sC = -(g - sC) \\ g + sC & sC = (2,1) \text{ cofactor} \end{bmatrix}$$

$$\det = (sC)(sC) - (g - sC)(-g - sC) = s^2 C^2 - (-g^2 + s^2 C^2) = +g^2$$

$$Z = \frac{1}{g^2} \begin{bmatrix} sC & -g + sC \\ g + sC & sC \end{bmatrix} \quad \text{as a check } Z \cdot Y = \mathbf{1}_2$$



$$ZY = \frac{1}{g^2} \begin{bmatrix} gC & -g + gC \\ g + gC & gC \end{bmatrix} \begin{bmatrix} gC & g - gC \\ -g - gC & gC \end{bmatrix} = \frac{1}{g^2} \begin{bmatrix} g^2 C^2 + g^2 - g^2 C^2 & g^2 C - g^2 C^2 \\ g^2 C + g^2 C^2 & -g^2 C + g^2 C^2 \\ -g^2 C & -g^2 C^2 \\ g^2 - g^2 C^2 + g^2 C^2 \end{bmatrix}$$

$$= \frac{1}{g^2} \begin{bmatrix} g^2 & 0 \\ 0 & g^2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

$$Z = \begin{bmatrix} gC/g^2 & -1/g + gC/g^2 \\ 1/g + gC/g^2 & gC/g^2 \end{bmatrix}$$

$$= \begin{bmatrix} 0 & -1/g \\ 1/g & 0 \end{bmatrix} + \frac{gC}{g^2} \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$$

$$V = ZI$$

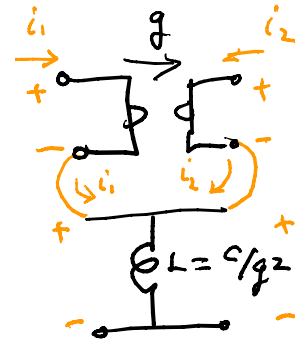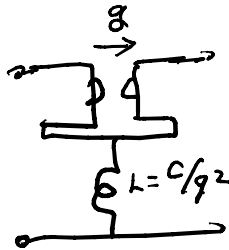


Some things have no admittance or impedance descriptions

Ideal op-amp:

$$v_{in} = v_d = 0; i_+ = i_- = 0$$




$$v_o = \text{arbitrary}, i_o = \text{arbitrary}$$

virtual "ground"

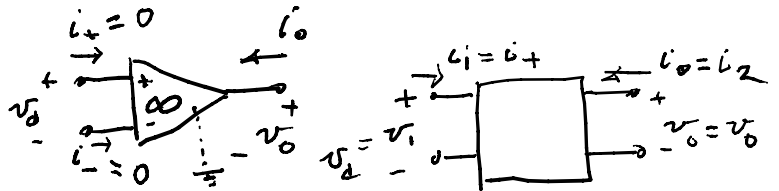

$$\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

ideal op-amp

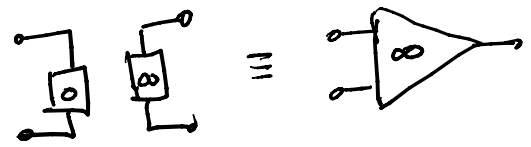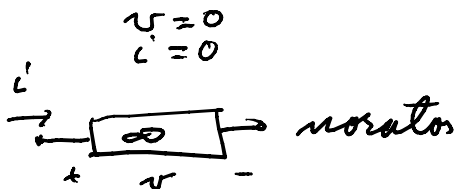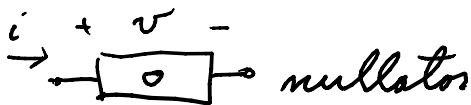

the nullor 2-port

$$[0][i] = [0][v] \Rightarrow \text{norator}$$

$$\begin{bmatrix} 1 \\ 0 \end{bmatrix} [i] = \begin{bmatrix} 0 \\ 1 \end{bmatrix} [v] \Rightarrow \text{nullator}$$

for linear circuit $Av = Bi$ as port descriptions

For Z : $v = Zi$, $Z = A^{-1}B$

Y : $i = Yv$, $Y = B^{-1}A$


no Z or Y

for an ideal op-amp

Back to graph theory: $Av = Bi$

$$i_b = i + i_a = i + j$$

$$v_b = v + v_a = v + e$$

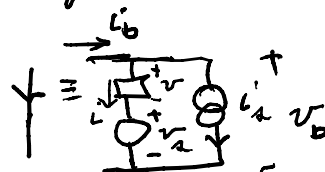

solve for $i, v \Rightarrow Av = A(v_b - v_a) = B(i_b - i_a)$

$$i_b = J^T \cdot i_a$$

$$v_b = e^T \cdot v_a$$

$$Av_b - Bi_b = Av_a - Bi_a$$

$$Ae^T v_a - B J^T i_a = \underbrace{\quad}_{\text{source terms}}$$

$$= [Ae^T - B J^T] \begin{bmatrix} v_a \\ i_a \end{bmatrix} = Au$$

$$x = \begin{bmatrix} v_a \\ i_a \end{bmatrix}$$

$$= [M_a + N]x = Bu$$

$u = \text{input sources}$

$$M_a \cdot x = -N x + Bu \Rightarrow E \frac{dx}{dt} = Ax + Bu$$

$$\begin{matrix} \text{if} \\ E \\ \text{is} \\ A \end{matrix} \quad x = \text{semi-state} = \begin{bmatrix} v_a \\ i_a \end{bmatrix}$$

if output is a linear combination of voltages and currents then it is given by a matrix on x (tree voltages & link currents)

$$y = C \cdot x$$

$y = \text{output}$

or

$$\left. \begin{matrix} E \dot{x} = Ax + Bu \\ y = Cx \end{matrix} \right\}$$

E can be singular

$u = \text{inputs}$

$y = \text{outputs}$

$x = x(t) = \text{semi-state}$

If E is identity

$$\left. \begin{aligned} \dot{x} &= Ax + Bu \\ y &= Cx \end{aligned} \right\} \text{state variable} \\ \text{equations}$$

$+ D\dot{x} + F\ddot{u}$