

$$E \frac{dx}{dt} = Ax + Bu$$

$$y = Cx$$

Let $\hat{x} = Px$, $P = \text{constant nonsingular}$

$$E P^{-1} \frac{dPx}{dt} = A P^{-1} Px + Bu$$

$$y = C P^{-1} Px$$

$P^{-1}P = I_b = b \times b$
identity matrix
 $x = b$ -vector

can premultiply by a constant matrix, nonsingular,

$$(QEP^{-1}) \frac{d\hat{x}}{dt} = QAP^{-1}\hat{x} + QBu$$

P & Q are $b \times b$ nonsingular


$$y = CP^{-1}\hat{x}$$

$\Rightarrow \hat{E} \frac{d\hat{x}}{dt} = \hat{A}\hat{x} + \hat{B}u$ } same input output description
 $y = \hat{C}\hat{x}$ } (normally $Q=P$)

$$T(s) = \hat{C}(s\hat{E} - \hat{A})^{-1}\hat{B} = C(sE - A)^{-1}B$$

this allows many choices for a circuit giving this $T(s)$

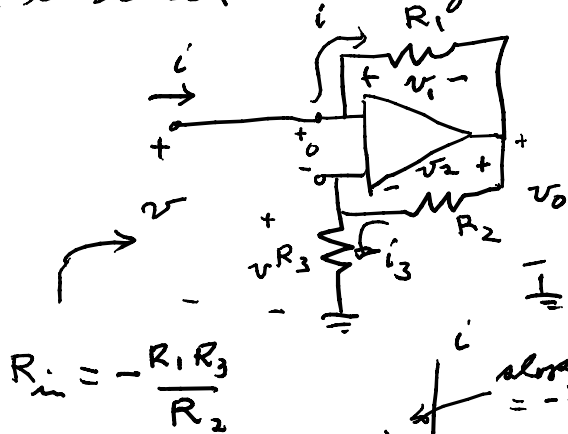a circuit which gives negative resistance




$$v = v_{R3} = R_3 i_3$$





$$v_2 = R_2 i_3 = \frac{R_2}{R_3} v$$

$$v_2 = -v_1 \Rightarrow v_1 = -\frac{R_2}{R_3} v$$


$$v_1 = R_1 i \Rightarrow i = \frac{1}{R_1} v_1 = -\frac{1}{R_1} \cdot \frac{R_2}{R_3} v$$

$$R_{in} = -\frac{R_1 R_3}{R_2}$$

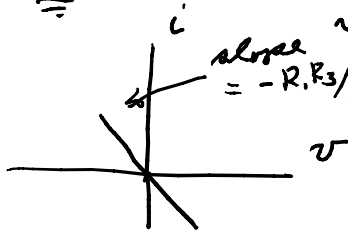


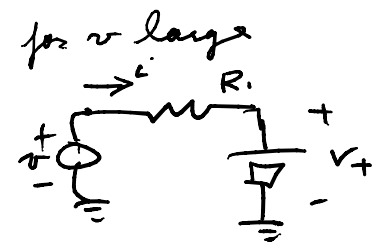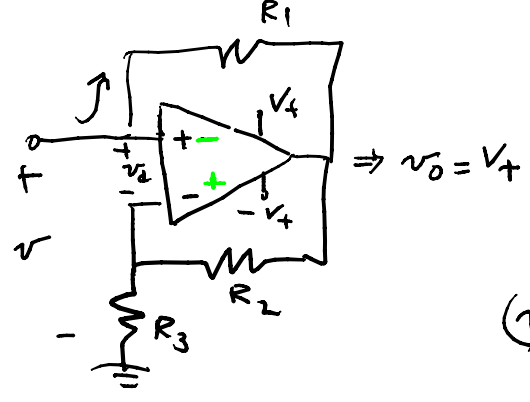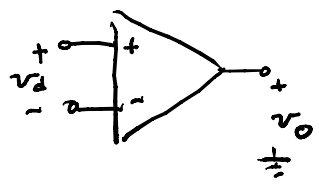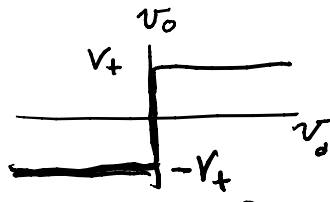

$$\frac{(v - V_+)}{R_1} = i$$

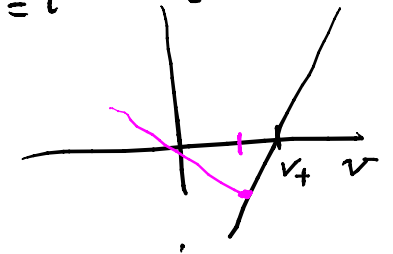

for v very small; $v_o = -V_+$

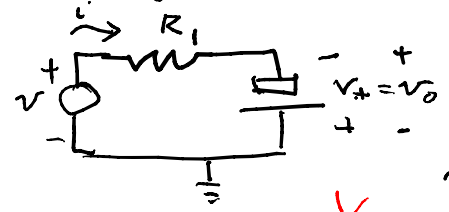


$$\frac{v + V_+}{R_1} = i$$

slope = $1/R_1$

slope = $-\frac{R_1 R_3}{R_2}$

slope = $1/R_1$

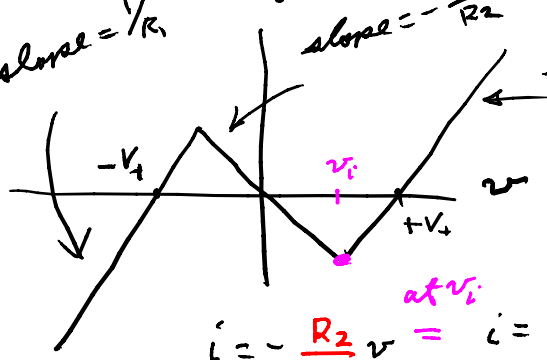


$$i = -\frac{R_2}{R_1 R_3} v = i = \frac{v - V_+}{R_1} \Rightarrow$$

$$-\frac{R_2}{R_3} v_i - v_i = -V_+$$


$$v_i = \frac{1}{1 + \frac{R_2}{R_3}} V_+$$

If we reverse the op-amp inputs we exchange V_+ & $-V_+$

gives

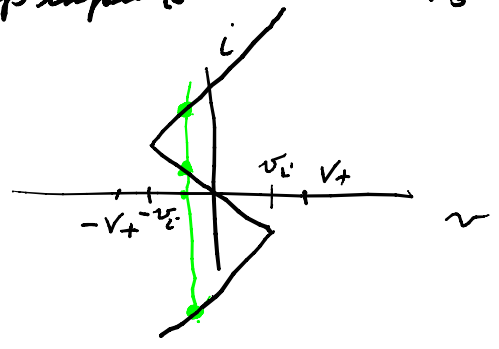

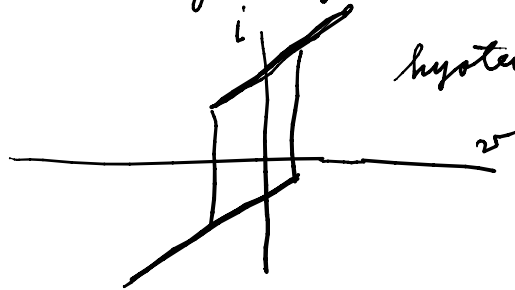which has 3 values for i given v in the range $-v_i \leq v \leq v_i$.



hysteresis type curve

in Spice a DC run
will not converge
since there are 3 values
at $v=0$

chapter 8 \Rightarrow positive-real functions
PR