

Passive Synthesis = Chapter 8

EE 610 M 09/29/08

Given a transfer function to create a circuit,

start with 1-port $y(s)$ or $z(s)$

assume from a passive finite RLC (gyrators & transformers) circuit

then $y(s)$ & $z(s)$ are rational in s

$$y(s) = \frac{N(s)}{D(s)} = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_m s^m + \dots + b_1 s + b_0}$$

has real coefficients, no poles in the RHP, $s = \sigma + j\omega$, $\sigma > 0$

also require by the passiveness that $\operatorname{Re} y(s) \geq 0$ in $\sigma > 0$

Positive-Real function $f(s)$

- 1) $f(s)$ is real for $s = \sigma$ ($s = \text{real}$) with $\sigma > 0$
[means real components
 a_i & b_i all real if rational]
- 2) $f(s)$ is analytic in $s = \sigma > 0$
[means, stable circuit;
no poles in $\sigma > 0$ if rational]
- 3) $\operatorname{Re} f(s) \geq 0$ in $s = \sigma + j\omega$ with $\sigma > 0$
[means $f(s)$ comes from a passive circuit]

Ex:

$$1) f(s) = y(s) = g \Rightarrow g \text{ real for 1)} \\ \operatorname{Re} g = g \geq 0 \text{ for 2) automatic} \\ \text{for 3)}$$

$$2) f(s) = \frac{1}{Ls} = g(s) \quad \int_0^\infty$$

$f(s) = \frac{1}{Ls}$ should be real for s real $> 0 \Rightarrow L = \text{real}$

$f(s) = \frac{1}{Ls}$ has a pole at $s=0$ not in $s > 0$
2) \Rightarrow ok

$$\begin{aligned} \text{Re } f(s) &= \text{Re} \left(\frac{1}{L(\sigma + j\omega)} \right) = \frac{1}{2} \left[\frac{1}{L(\sigma + j\omega)} + \frac{1}{L(\sigma - j\omega)} \right] \\ &= \frac{1}{2} \left[\frac{\sigma - j\omega + \sigma + j\omega}{L(\sigma + j\omega)(\sigma - j\omega)} \right] = \frac{\sigma}{L(\sigma^2 + \omega^2)} \end{aligned}$$

in $s > 0$ for all ω , $-\infty < \omega < \infty$


$\Rightarrow L > 0 \Rightarrow$ shows \int_0^∞ is passive

$$3) f(s) = \frac{s+2}{s+b_0} \quad \& \text{ find } b_0 \text{ such that } f(s) \text{ is PR}$$

condition 1) $b_0 \Rightarrow$ real

condition 2) $s = -b_0$ is the only pole
can't be in $s > 0$

$$\Rightarrow b_0 \geq 0$$

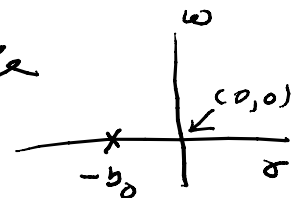


condition 3)


$$\begin{aligned} \text{Re } f(s) &= \frac{1}{2} \left\{ \frac{\sigma + j\omega + 2}{\sigma + j\omega + b_0} + \frac{\sigma - j\omega + 2}{\sigma - j\omega + b_0} \right\} \\ &= \frac{1}{2} \left\{ \frac{(\sigma + 2 + j\omega)(\sigma - j\omega + b_0) + (\sigma + 2 - j\omega)(\sigma + b_0 + j\omega)}{(\sigma + b_0 + j\omega)(\sigma + b_0 - j\omega)} \right\} \\ &= \frac{1}{2} \left\{ \frac{2(\sigma + 2)(\sigma + b_0) + \omega^2}{(\sigma + b_0)^2 + \omega^2} \right\} \geq 0 \quad \text{for all } \sigma > 0 \\ & \quad \& \text{ all } -\infty < \omega < \infty \end{aligned}$$

$g(s) f(s) = \frac{s+2}{s+b_0}$ is PR for $b_0 \geq 0$ & of degree $f(s) = 1$

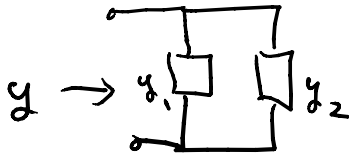
$$= \frac{s}{s+b_0} + \frac{2}{s+b_0} = \frac{1}{1 + \frac{b_0}{s}} + \frac{1}{\frac{s}{2} + \frac{b_0}{2}} = g(s) = g_1 + g_2$$



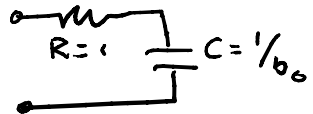
$$y_1 \Rightarrow z_1 = \frac{1}{y_1} = 1 + \frac{b_0}{a} \Rightarrow$$


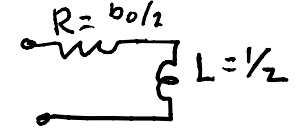
$$y_2 \Rightarrow z_2 = \frac{1}{y_2} = \frac{b_0}{2} + \frac{a}{2} \Rightarrow$$




$$y(a) = \frac{a+2}{a+b_0} \Rightarrow$$

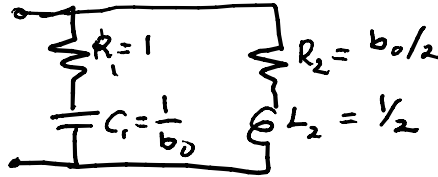

Rewrite $f(a) = \frac{a+2}{a+b_0} = y(a) \quad \frac{1}{a+b_0} \frac{a+2}{a+b_0}$
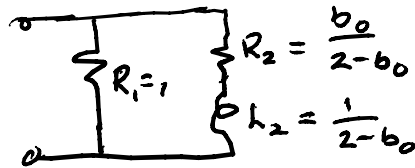
$$= 1 + \frac{2-b_0}{a+b_0} \quad \frac{2-b_0}{2-b_0}$$




this passive only if $0 < b_0 < 2$

$$y(a) = f(a) = \frac{1}{\frac{a+b_0}{a+2}}$$

$$\frac{a+2}{a+b_0} \frac{1}{a+2} \frac{a+2}{b_0-2}$$

$$= \frac{1}{1 + \frac{b_0-2}{a+2}}$$

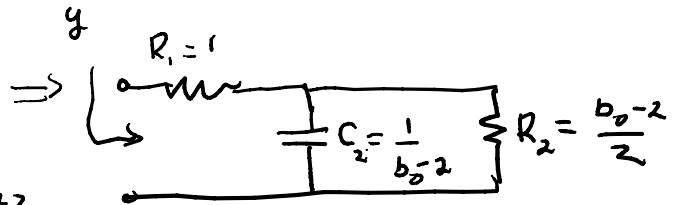$\underbrace{\quad}_{z_1} \quad \underbrace{\quad}_{z_2}$




$$y_2 = \frac{1}{z_2} = \frac{a+2}{b_0-2}$$

valid for $b_0 > 2$

shows can have many solutions to getting a circuit from a transfer function.

circuits without resistance \Rightarrow lossless
 \Rightarrow reactance functions, p. 342

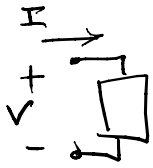$P(j\omega) = 0 =$ ^{average} power input in the sinusoidal steady state for a lossless circuit



$$P(j\omega) = \frac{V^* I + V I^*}{2} \quad \text{at } s = j\omega$$

$$= \frac{V^* y(j\omega) V + V y^*(j\omega) V^*}{2}$$

$$= \frac{1}{2} \left\{ y(j\omega) V^* V + y^*(j\omega) V V^* \right\}$$

$$= \frac{1}{2} (y(j\omega) + y^*(j\omega)) V V^* = 0 \quad \text{when } V \neq 0$$

$$y(j\omega) + y^*(j\omega) = 0$$

$$= y(j\omega) + y(-j\omega) = 0$$

$$= [y(s) + y(-s)] \Big|_{s=j\omega} = 0$$

for almost all ω
(not really for natural frequencies [a finite # of them])

mathematicians show this will hold for all s


$$y(s) + y(-s) = 0 \Rightarrow y(s) = -y(-s)$$

$$\text{or } \text{Ev } y(s) = 0$$

$$\text{Ex: } y(s) = \frac{1}{Ls} \Rightarrow y(s) + y(-s) = \frac{1}{Ls} + \frac{1}{L(-s)} = \frac{1}{Ls} - \frac{1}{Ls} = 0$$

$$\left. \begin{aligned} \text{Ev } y(s) &= \frac{1}{2} [y(s) + y(-s)] \\ \text{Od } y(s) &= \frac{1}{2} [y(s) - y(-s)] \end{aligned} \right\} y(s) = \text{Ev } y(s) + \text{Od } y(s)$$

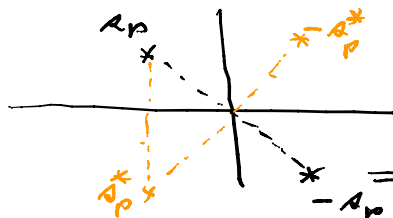
$\Rightarrow y(s) = \text{Od } y(s)$ for a reactance function



\Rightarrow can not be if $y(s)$ is PR

∴ for a reactance function all poles are on the $j\omega$ axis $\frac{k}{(s + j\omega_0)^{m_p}}$

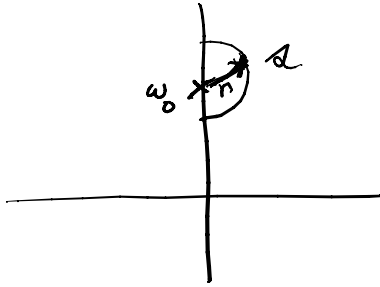but these poles must be simple ($m_p = 1$ & k real) with real positive residue ($k > 0$)



$y(s)$ near the pole

$$\approx \frac{k}{(s - j\omega_0)^{m_0}} \quad \text{for } re^{j\theta}, \quad -\frac{\pi}{2} < \theta < \frac{\pi}{2}$$

Let $\text{Re } y(s) \geq 0; \quad (s - j\omega_0) = re^{j\theta}$

$$\text{Re } y(s) \Big|_{\text{on the semicircle}} = \text{Re} \left(\frac{k}{(re^{j\theta})^{m_0}} \right) = \frac{1}{r} \text{Re} \left(\frac{k}{e^{j\theta m_0}} \right)$$

$$= \frac{1}{r} |k| \text{Re} \left(e^{j(4k - \theta m_0)} \right)$$

$$= \frac{1}{r} |k| \cos(4k - \theta m_0) > 0 \text{ only if}$$

$$\begin{aligned} 4k &= 0 \\ m_0 &= 1 \end{aligned}$$