

Synthesis of PR functions

EE 610 W 10/01/08

PR = rational positive real $F(s)$

$F(s)$ an admittance or an impedance
 $Y(s)$ $Z(s) = 1/Y(s)$

Y or $Z \Rightarrow$ immittance

$$V(s) = Z(s)I(s)$$

$$I(s) = Y(s)V(s)$$

} duals if replace I by V
 & V by I

in the dual replace

$$C_d = L, L_d = C, R_d = R$$

$$\text{then } Y_d(s) = Z(s) = 1/Y(s)$$

know if $F(s)$ is PR then $1/F(s)$ is PR

then $F(1/s)$ is PR

for PR

$$Y(s) = \frac{N(s)}{D(s)} = \frac{a_n s^n + \dots + a_1 s + a_0}{b_m s^m + \dots + b_1 s + b_0}$$


has no poles in RH s -plane; all in $\sigma \leq 0$

no zeros in RH s -plane; all in $\sigma \leq 0$

$$Y(s) = \frac{k_0}{(s - j\omega_0)^{m_0}} + \dots$$

$$k_0 > 0; m_0 = 1$$

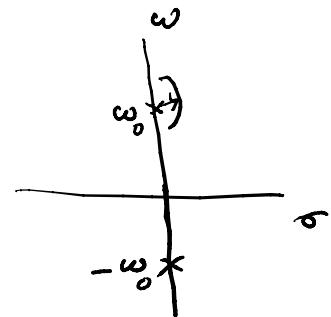as coefficients are real
 any zero of N or D comes
 with a conjugate



$$Y(s) = \frac{k_0}{s - j\omega_0} + \frac{k_0}{s + j\omega_0} + \text{others}$$



$$= \frac{k_0(s + j\omega_0) + k_0(s - j\omega_0)}{(s - j\omega_0)(s + j\omega_0)} + \text{others}$$

terms in a partial fraction expansion

$$= \frac{2k_0 s}{s^2 + \omega_0^2} + Y_1(s) \quad ; \quad \text{set } Y_0(s) = \frac{2k_0 s}{s^2 + \omega_0^2}$$

$$Z_0(s) = \frac{1}{Y_0(s)} = \frac{s}{2k_0} + \frac{\omega_0^2}{2k_0 s}$$
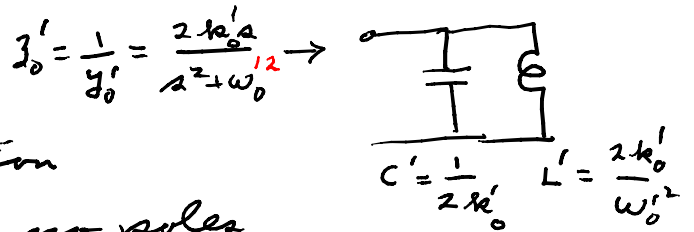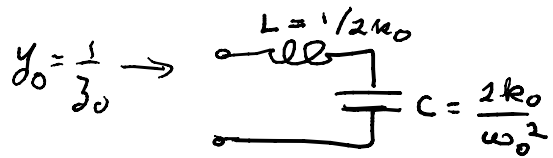
$$y_0 z(a) = \frac{2k_0' a}{a^2 + \omega_0'^2} + z_1(a)$$



For a reactance function

$$y(a) + y(-a) = 0 \Rightarrow \text{no poles of } y(a) \text{ in } \sigma \neq 0 \text{ (none in RHP or LHP) or zeros}$$

$$\frac{1}{z(a)} + \frac{1}{z(-a)} = 0$$

$$\frac{z(a) + z(-a)}{z(a)z(-a)} = 0 \Rightarrow \text{no poles of } z(a) \text{ in } \sigma \neq 0$$

but poles of $z(a) = \frac{1}{y(a)} = \frac{1}{N/D} = \frac{D}{N}$ in $\sigma \neq 0$

\therefore for a reactance function

all poles and zeros are on the $j\omega$ axis & there the poles (and zeros) are simple with a positive residue.

$$y(a) = \frac{\prod_{i=1}^n (a^2 + \omega_{mi}^2)}{\prod_{j=1}^m (a^2 + \omega_{dj}^2)} \times \frac{1}{a} \text{ (or } \times a)$$

Ex: $y(a) = \frac{1}{a} \frac{(a^2 + 3)}{(a^2 + 4)}$

maybe $\hat{y}(a) = \frac{a^2 + 3}{a(a^2 + 2)}$ but not a reactance function:

$$= \frac{k_0}{a} + \frac{k_1}{a - j2} + \frac{k_1^*}{a + j2}$$

$$k_0: \lim_{a \rightarrow 0} a y(a) = k_0 + a \left[\frac{k_1}{a - j2} + \frac{k_1^*}{a + j2} \right] \Big|_{a=0} = k_0 \Rightarrow k_0 = 3/4$$

$$= \lim_{a \rightarrow 0} a \frac{1}{a} \left(\frac{a^2 + 3}{a^2 + 4} \right) = \frac{3}{4}$$

$$k_1: \lim_{a \rightarrow j2} (a - j2) y(a) = \frac{k_0(a - j2)}{a} \Big|_{a=j2} + k_1 + \lim_{a \rightarrow j2} \left(\frac{a - j2}{a + j2} \right) k_1^* = k_1$$

$$(a-j2) \frac{1}{a} \left(\frac{a^2+3}{(a-j2)(a+j2)} \right) \Big|_{a=j2} = \frac{-4+3}{j2(2 \times j2)} = \frac{-1}{-8} = 1/8 = k_1 = k_1^*$$

$$y(a) = \frac{1}{a} \frac{(a^2+3)}{a^2+4} = \frac{3/4}{a} + \frac{1/8}{a-j2} + \frac{1/8}{a+j2} = \frac{3/4}{a} + \frac{2 \cdot \frac{1}{8} a}{a^2+4}$$


as a check

$$\Rightarrow \frac{\frac{3}{4}(a^2+4) + \frac{2}{8}a^2}{a(a^2+4)} = \frac{1 \cdot a^2 + \frac{3 \times 4}{4}}{a(a^2+4)}$$

here

$$y(a) = \frac{3/4}{a} + \frac{1/4 a}{a^2+4}$$
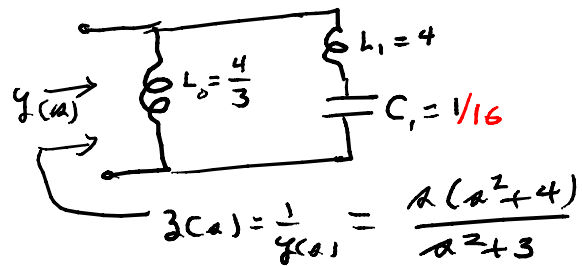
$$\begin{aligned} &= \text{th} \\ & y_1 \rightarrow 3, = \frac{1}{y_1} \\ & = \frac{a^2+4}{\frac{1}{4}a} \\ & = 4a + \frac{1}{16} \end{aligned}$$



Look at $\hat{y} = \frac{1}{a} \cdot \frac{a^2+3}{a^2+2} = \frac{3/2}{a} + \frac{\hat{k}_1}{a-j\sqrt{2}} + \frac{\hat{k}_1^*}{a+j\sqrt{2}}$

$$\hat{k}_1 = (a-j\sqrt{2}) \hat{y} \Big|_{a=j\sqrt{2}} = \hat{k}_1$$

$$= \frac{1}{j\sqrt{2}} \cdot \frac{3-2}{(a+j\sqrt{2})} \Big|_{a=j\sqrt{2}} = \frac{1}{j\sqrt{2} \cdot 2 \cdot j\sqrt{2}} = -1/4$$

i. $\hat{y}(a)$ is not PR

for a reactance function (is PR, $y(a) + y(-a) = 0$)


$$y(a) = \frac{k_0}{a} + k_0 a + \sum_{i=1}^q \frac{k_i a}{a^2 + \omega_i^2} \quad \text{all } k_i \text{ real \& positive}$$

$$y(j\omega) = j \left[-\frac{k_0}{\omega} + k_0 \omega + \sum_{i=1}^q \frac{k_i \omega}{-\omega^2 + \omega_i^2} \right]$$

$$\begin{aligned} \frac{d y(j\omega)/j}{d\omega} &= \frac{k_0}{\omega^2} + k_0 + \sum_{i=1}^q \left\{ \frac{k_i}{-\omega^2 + \omega_i^2} - \frac{k_i \omega (-2\omega)}{(-\omega^2 + \omega_i^2)^2} \right\} \\ &= \frac{k_0}{\omega^2} + k_0 + \sum_{i=1}^q \frac{+1 k_i \omega^2 + k_i \omega_i^2}{(-\omega^2 + \omega_i^2)^2} \quad d(1/x) = -1/x^2 \end{aligned}$$

we see $\frac{dY(j\omega)/j}{d\omega} > 0$ (or ∞ at the poles)

$$Y(j\omega) = G(\omega) + jB(\omega)$$

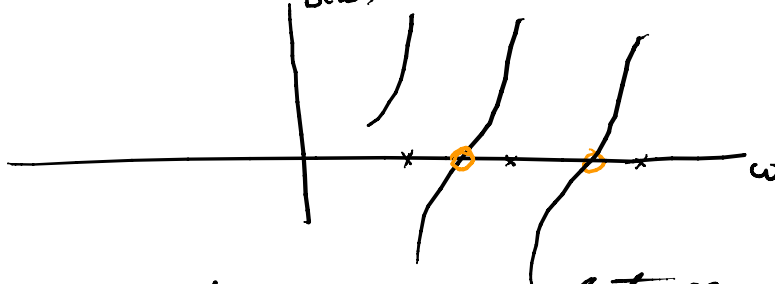

shows that zeros appear between poles of a reactance function \Rightarrow poles & zeros alternate

note $\hat{Y} = \frac{s^2 + 3}{s(s^2 + 2)}$ does not have this property