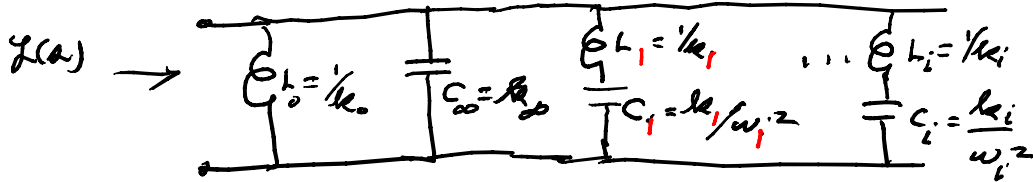


Reactance function synthesis

EE 610 M 10/06/08


$$y(s) = \frac{k_0}{s} + k_{\infty} s + \sum_{i=1}^n \frac{k_i s}{(s^2 + \omega_i^2)}$$

$$y_i = \frac{k_i s}{s^2 + \omega_i^2}; z_i = \frac{s}{k_i} + \frac{\omega_i^2}{s k_i}$$




2nd Foster = partial fraction expansion of $y(s) = y(-s)$ reactance

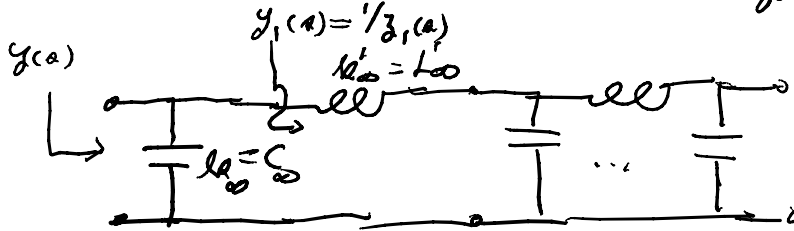uses minimum number of L 's & C 's (reactances)




$$z(s) = \frac{1}{y(s)} = k'_0 s + \frac{k'_0}{s} + \sum_{i=1}^{n'} \frac{k'_i s}{s^2 + \omega_i'^2}$$
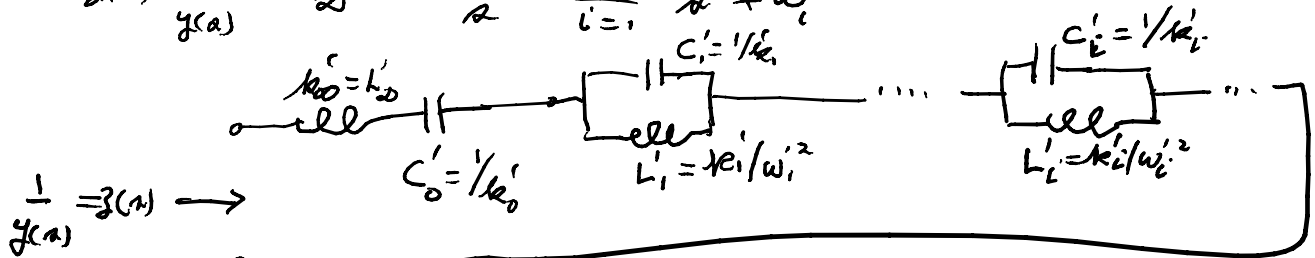
$$\frac{s^2 + \omega_i'^2}{k'_i s} = z'_i$$



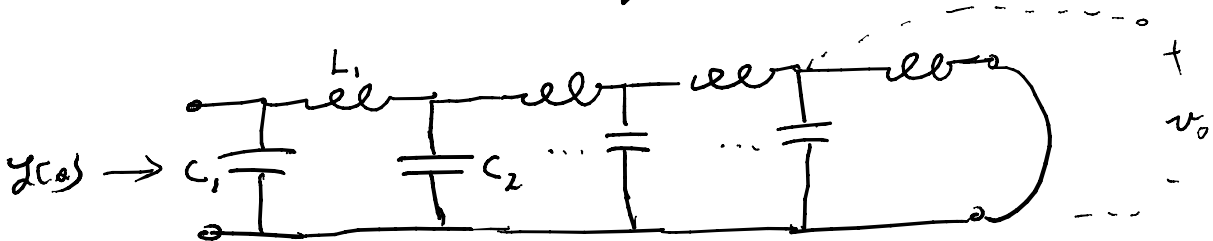1st Foster = partial fraction expansion of $z(s) = 1/y(s)$




Extract poles at infinity of y 's and z 's = 1st Cauer

∞ = zeros of transmission at ∞

useful for low pass

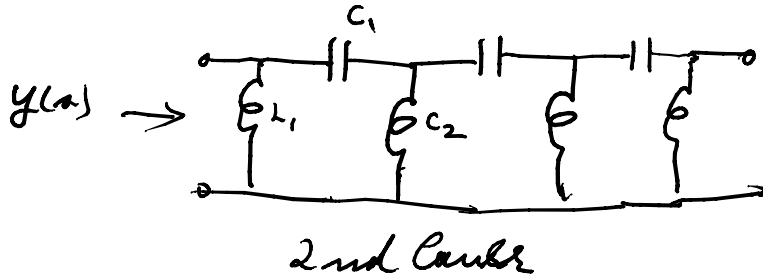also can do at $s=0$: extract poles at $s=0$ of y 's and z 's



From 1st Foster:

$$y(s) = k_{\infty} s + \frac{1}{k_0' s + \frac{1}{k_0'' s + \dots}} \quad \left. \vphantom{y(s)} \right\} \begin{array}{l} \text{Continued fraction} \\ \text{expansion about } \infty \\ (\div \text{ highest powers of } s) \end{array}$$

2nd Foster

$$y(s) = \frac{1}{\frac{1}{k_0'} s} + \frac{1}{\frac{1}{\frac{1}{k_0'} s} + \frac{1}{\frac{1}{k_0'' s} + \dots}} \quad \left. \vphantom{y(s)} \right\} \begin{array}{l} \text{Continued fraction} \\ \text{expansion about } s=0 \\ (\div \text{ lowest powers of } s) \end{array}$$

Ex: $y(s) = \frac{(s^2+1)(s^2+6)}{s(s^2+3)} = \frac{2}{s} + 1 \cdot s + \frac{k_1 s}{s^2+3}; k_1 = 8/3$

$$\left. \frac{(s^2+1)(s^2+6)}{s^2} \right|_{s^2=-3} = \left(\frac{2(s^2+3)}{s^2} + (s^2+3) + k_1 \right) \left. \frac{s^2+3}{s} \right|_{s^2=-3}$$

$\underbrace{\hspace{10em}}_{=0} + k_1$

$$\frac{(-2)(+3)}{-3} = +2 = k_1 \quad \text{with } s^2 = -3$$

$$y(s) = \frac{2}{s} + s + \frac{2s}{s^2+3} \Rightarrow \begin{array}{c} \text{Circuit diagram for 2nd Foster form:} \\ \text{Parallel branches: } L_0 = 1/2, C_0 = 1, L_1 = 1/2 \\ \text{Series branch: } C_1 = 2/3 \end{array}$$


$$z(s) = \frac{1}{y(s)} = \frac{s(s^2+3)}{(s^2+1)(s^2+6)} = \frac{k_1 s}{s^2+1} + \frac{k_2 s}{s^2+6} = \frac{24/5}{s^2+1} + \frac{34/5}{s^2+6}$$

$$k_1 = \left. \frac{s^2+3}{s} \cdot z(s) \right|_{s^2=-1} = \left. \frac{s^2+3}{s^2+6} \right|_{s^2=-1} = \frac{2}{5}$$

$$k_2 = \left. \frac{s^2+6}{s} \cdot z(s) \right|_{s^2=-6} = \frac{-6+3}{-6+1} = \frac{-3}{-5} = 3/5$$

$$y_1 = \frac{s^2+1}{24/5}$$

$$y_2 = \frac{s^2+6}{3/5 s}$$

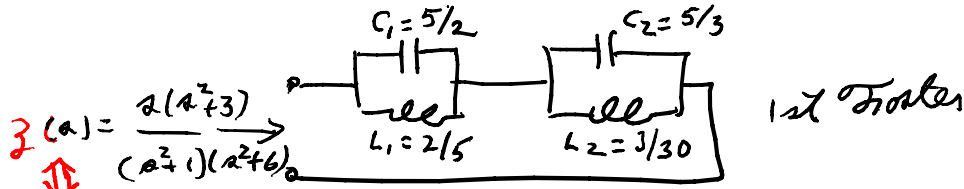

$y(s) = \frac{(s^2+1)(s^2+6)}{s(s^2+3)}$

$y(s) = \frac{s^4 + 7s^2 + 6}{s^3 + 3s}$
 $= N/D$


uses 4 reactive elements
 $\delta[4] = 4 = \delta[3]$
 " degree of a rational function, $\delta \Rightarrow \delta[5]$

1st Case: start with a pole at ∞

$D = s^3 + 3s \quad \left| \begin{array}{l} s \\ s^4 + 7s^2 + 6 = N \\ s^4 + 3s^2 \end{array} \right. \Rightarrow \text{remainder} = \frac{4s^2 + 6}{s^3 + 3s} = \frac{N_1}{D}$

$$y(s) = 2 + \frac{1}{\frac{1}{4}s + \frac{1}{\frac{16}{6}s + \frac{1}{\frac{36}{4}s + 0}}}$$

\downarrow
 $z=0 = \text{short}$

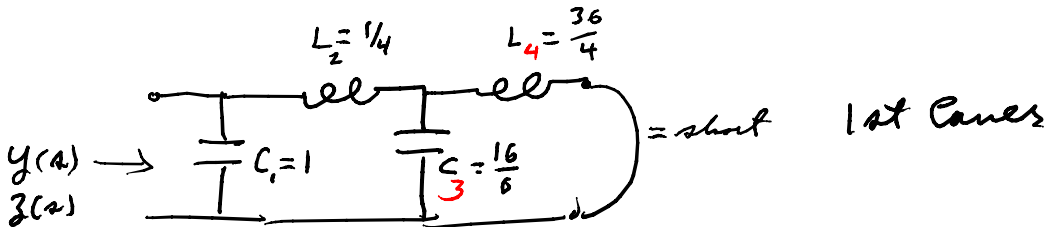

2nd Case $y(s) = \frac{s^4 + 7s^2 + 6}{s^3 + 3s}$; $Z(s)$

$$\frac{6}{3s} \left| \begin{array}{l} 6 + 7s^2 + s^4 \\ 6 + \frac{6}{3}s^2 \end{array} \right. \frac{9}{15s}$$

$$\frac{15}{3}s^2 + s^4 \left| \begin{array}{l} 3s + s^3 \\ 3s \end{array} \right. \frac{15}{3 \times 6s}$$

$$\frac{6}{15}s^3 \left| \begin{array}{l} 15s^2 + s^4 \\ 15s^2 \end{array} \right. \frac{16}{15s}$$

$$\frac{15}{3}s^2 \left| \begin{array}{l} s^4 \\ s^4 \end{array} \right. \frac{16}{15}s^3$$

$$\begin{aligned}
 Y(s) &= \frac{6}{3s} + \frac{1}{s} \\
 &\xrightarrow{2} \frac{2}{s} + \frac{1}{s} \\
 &\xrightarrow{2} \frac{2}{s} + \frac{1}{s} \\
 &\xrightarrow{4} \frac{2}{s} + \frac{1}{s} \\
 &\xrightarrow{3} \frac{16}{15s} + 0
 \end{aligned}$$

