

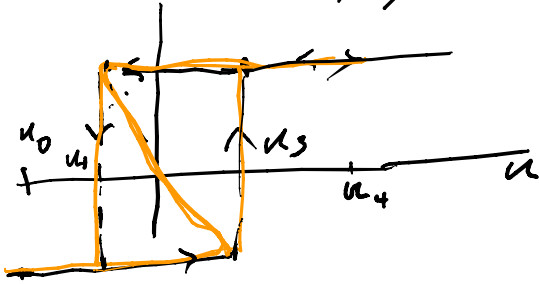
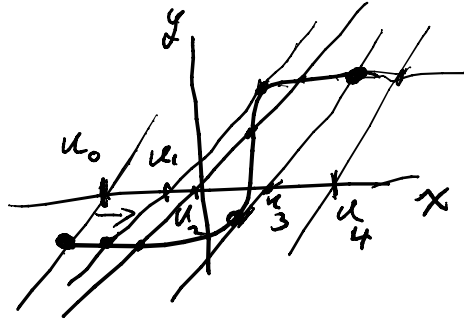


Hysteresis

EE 610
10/27/08

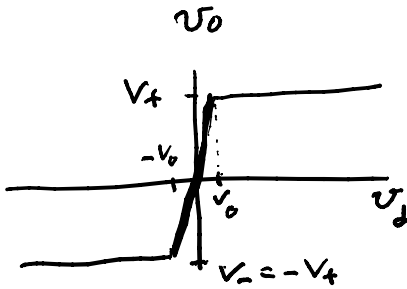

actual circuit for

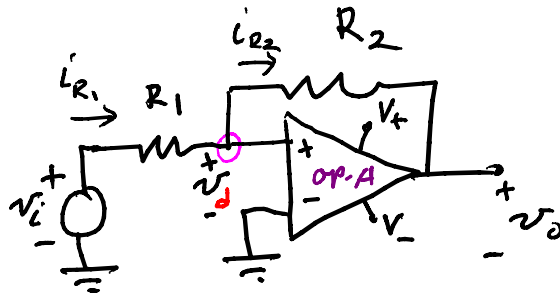

device curve

$i_{R1} = i_{R2}$ as no current into input lead of the op-amp

$$i_{R1} = \frac{1}{R_1} (v_i - v_d) = i_{R2} = \frac{1}{R_2} (v_d - v_o)$$

$$\frac{R_2}{R_1} (v_i - v_d) = v_d - v_o$$

$$v_o = v_d + \frac{R_2}{R_1} v_d - \frac{R_2}{R_1} v_i$$


$$= \left(1 + \frac{R_2}{R_1}\right) v_d - \frac{R_2}{R_1} v_i$$


$$y = \left(1 + \frac{R_2}{R_1}\right) x + x_0$$

$$\frac{dy}{dx} = 1 + \frac{R_2}{R_1}$$

when $v_o = 0$ intersect at
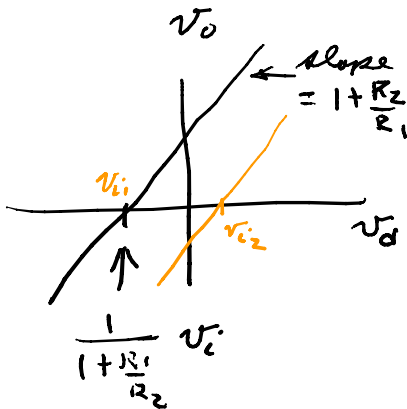
$$v_d = \frac{R_2/R_1}{1 + R_2/R_1}, v_i = \frac{1}{1 + R_1/R_2} v_i$$



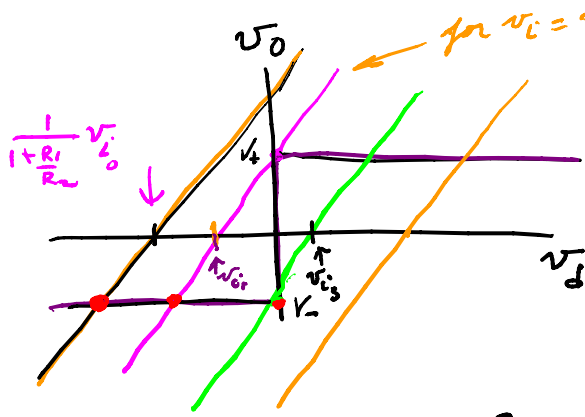

for $v_i = v_{i1}$


$$1) v_o = \left(1 + \frac{R_2}{R_1}\right) v_d - \frac{R_2}{R_1} v_{i1}$$

$$2) v_o = V_+ \text{ for } v_{i1} \text{ intersect}$$

here $v_d = 0$ for v_{i1}


$$V_+ = 0 - \frac{R_2}{R_1} v_{i1} \Rightarrow v_{i1} = -\frac{R_1}{R_2} V_+$$
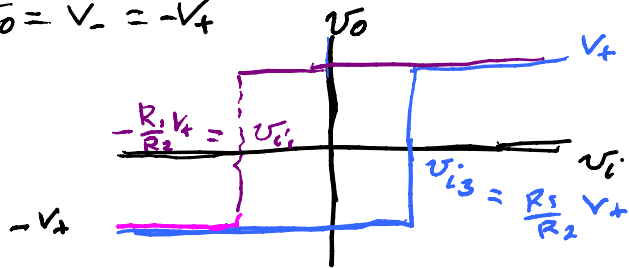
$$\left. \begin{aligned} 1') v_o &= \left(1 + \frac{R_2}{R_1}\right) v_d - \frac{R_2}{R_1} v_{i3} = V_- = -V_+ \text{ \& } v_d = 0 \\ 2') v_o &= V_- = -V_+ \end{aligned} \right\} \begin{aligned} v_{i3} &= -\frac{R_1}{R_2} V_- \\ &= +\frac{R_1}{R_2} V_+ \end{aligned}$$




$$\text{hysteresis width} = v_{i3} - v_{i1} = 2 \frac{R_1}{R_2} V_+$$

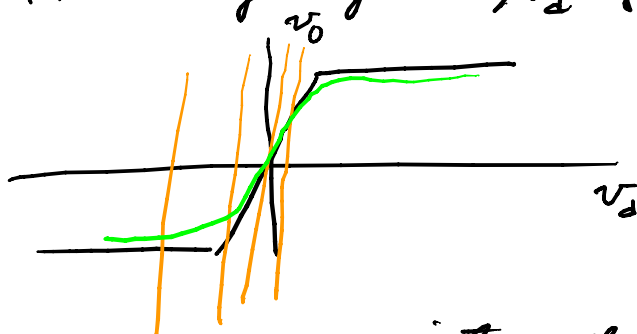
For a more practical one there is a non ∞ slope at the origin for v_o/v_d of the op-amp



To get more than 1 intersect need the slope of the load line, $\left(\frac{1}{1 + \frac{R_2}{R_1}}\right)$, less than the device slope.

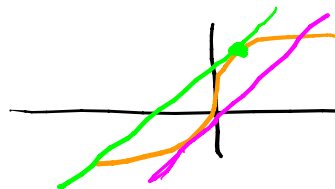We need slope of load line = device slope for a jump point




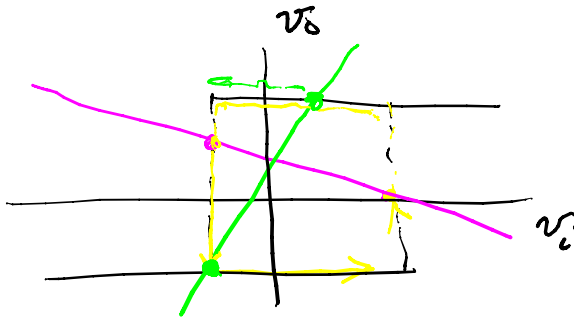


This makes a nice
oscillator — magenta
or memory — green


p.406 = adjoint allows to take the derivative by solving circuit equations

Here will get $Y_{b \times b}^a = Y_{b \times b}^T$ where these b's don't include input & output branches

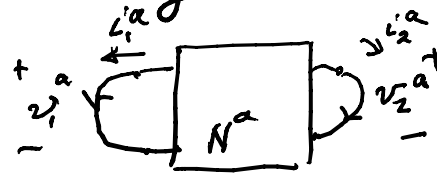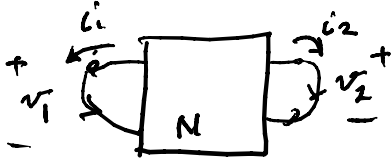N = original network, N^a = adjoint network; same graph


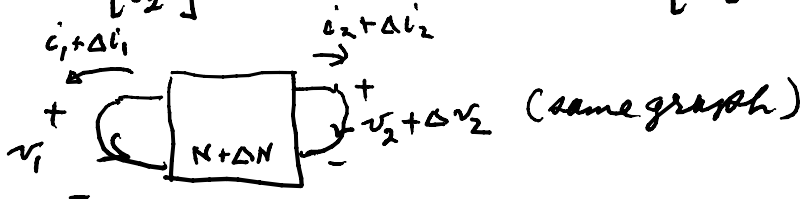
$$1) \begin{bmatrix} v_1 & v_2 \end{bmatrix} \begin{bmatrix} i_1^a \\ i_2^a \end{bmatrix} + v_b^T l_b^a = 0 \quad \begin{bmatrix} v_1^a & v_2^a \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} + v_b^{aT} l_b = 0 \quad (2)$$



$$3) \begin{bmatrix} v_1 & v_2 + \Delta v_2 \end{bmatrix} \begin{bmatrix} i_1^a \\ i_2^a \end{bmatrix} + (v_b + \Delta v_b)^T l_b^a = 0$$

$$4) \begin{bmatrix} v_1^a & v_2^a \end{bmatrix} \begin{bmatrix} i_1 + \Delta i_1 \\ i_2 + \Delta i_2 \end{bmatrix} + v_b^{aT} (i_b + \Delta i_b) = 0$$

if the output is open-circuit v_2 , & input voltage source v_1

$$\Downarrow \\ i_2 = 0 \Rightarrow \Delta i_2 = 0$$

assume have admittance matrices $Y = Y_{b \times b}$, $Y^a = Y_{b \times b}^a$

& have a change in Y , ΔY .

$$1) - 3) : [0 + \Delta v_2 \cdot i_2^a] + v_b^T i_b^a - [v_b + \Delta v_b]^T \cdot i_b^a = 0$$

$$\Rightarrow \Delta v_2 \cdot i_2^a - (\Delta v_b)^T \cdot i_b^a = \Delta v_2 \cdot i_2^a - \Delta v_b^T \cdot Y^a v_b^a = 0 \quad (5)$$

$$2) - 4) : [v_1^a i_1 - v_1^a \Delta i_1 - v_2^a i_2 - v_2^a \Delta i_2] + v_b^T i_b - v_b^T (i_b + \Delta i_b) = 0$$

$$\Rightarrow -v_1^a \Delta i_1 - v_b^{aT} \Delta i_b = 0$$

but $i_b = Y_{b/b} \cdot v_b \Rightarrow \Delta i_b = \Delta Y \cdot v_b + Y \cdot \Delta v_b$

$$-v_1^a \Delta i_1 - v_b^{aT} \Delta Y \cdot v_b - v_b^{aT} Y \cdot \Delta v_b = 0 \quad (6)$$

$$6) - 5) \Rightarrow -v_1^a \Delta i_1 - v_b^{aT} \Delta Y \cdot v_b - v_b^{aT} Y \Delta v_b$$

$$- \Delta v_2 \cdot i_2^a + \Delta v_b^T Y^a v_b^a = 0 \Rightarrow \text{gives } Y^a = Y^T$$

set $v_1^a = 0$
(a short) $\Rightarrow \Delta v_2 \cdot i_2^a = v_b^{aT} \cdot \Delta Y \cdot v_b$

\therefore set $i_2^a = 1 \Rightarrow \Delta v_2 = v_b^{aT} \Delta Y v_b$

