
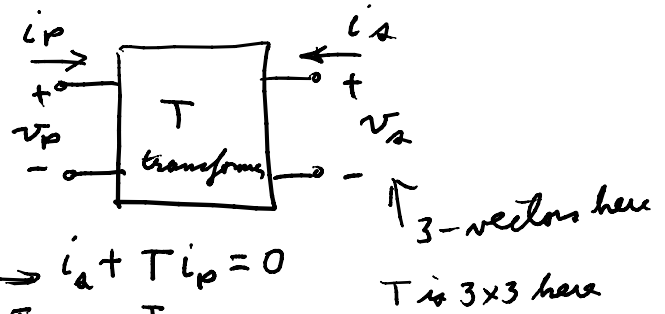

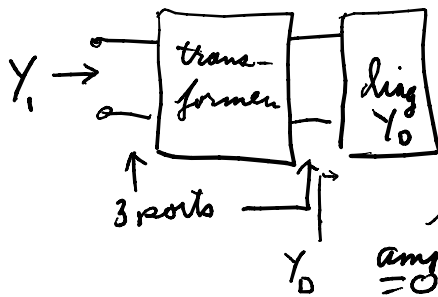
$$Y = \begin{bmatrix} 3/2 & -1/4 & -9/8 \\ -1/4 & 0 & 0 \\ -9/8 & 0 & 5/2 \end{bmatrix} + \begin{bmatrix} 0 & -1/4 & -1/8 \\ 1/4 & 0 & 0 \\ 1/8 & 0 & 0 \end{bmatrix} = Y_1 + Y_2$$




sum of amp turns = 0 $\rightarrow i_2 + T i_p = 0$

power in = power out $\rightarrow v_p^T i_p = v_2^T i_2$

holds for any $\Rightarrow v_p^T = v_2^T T \Rightarrow v_p = T^T v_2$

Y_1 vs Y_0

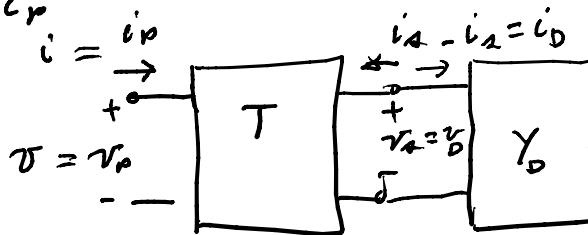

$$i = Y_1 v = Y_1 v_p = Y_1 T^T v_2 = Y_1 T^T v_0$$

$$i_p \Rightarrow T i_p = -i_2 = i_0 \Rightarrow T i_p = T i = T Y_1 T^T v_0 = i_0$$

$$\Rightarrow Y_0 = T Y_1 T^T \Rightarrow Y_1 = T^{-1} Y_0 T^{-T}$$

then $Y_1 = T^{-1} Y_0 T^{-T}$

To transform:

$$T_1 Y_1 T_1^T = \begin{bmatrix} 1 & 0 & 0 \\ 1/4 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 3/2 & -1/4 & -9/8 \\ -1/4 & 0 & 0 \\ -9/8 & 0 & 5/2 \end{bmatrix} \begin{bmatrix} 1 & 1/6 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 3/2 & -1/4 & -9/8 \\ 0 & -(1/4)^2 & (-9/8)(1/4)/3/2 \\ -9/8 & 0 & 5/2 \end{bmatrix} \begin{bmatrix} 1 & 1/6 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 3/2 & 0 & -9/8 \\ 0 & -1/24 & -9/8 \cdot 1/6 \\ -9/8 & -9/8 \cdot 1/6 & 5/2 \end{bmatrix}$$

$$T_2(T_1 Y T_1^T) T_2^T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ +9/8 & 0 & 1 \\ 3/2 & & \end{bmatrix} \begin{bmatrix} 3/2 & 0 & -9/8 \\ 0 & -1/24 & -3/16 \\ -9/8 & -3/16 & 5/2 \end{bmatrix} \begin{bmatrix} 1 & 0 & 3/4 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 3/2 & 0 & 0 \\ 0 & -1/24 & -3/16 \\ 0 & -3/16 & 5/2 - \frac{19/8}{3/2} \end{bmatrix} = \frac{5 \times 16 - 27}{32} = \frac{80 - 27}{32} = \frac{53}{32}$$

$$T_3(T_2 T_1 Y T_1^T T_2^T) T_3^T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & -\frac{3/16}{-1/24} & 1 \end{bmatrix} \begin{bmatrix} 3/2 & 0 & 0 \\ 0 & -1/24 & -3/16 \\ 0 & -3/16 & 5/2 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & -9/2 \\ 0 & 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 3/2 & 0 & 0 \\ 0 & -1/24 & 0 \\ 0 & 0 & \frac{53}{32} - \left(\frac{9}{2} \times \frac{-3}{16}\right) \end{bmatrix} = \frac{80}{32}$$

$$= \begin{bmatrix} 3/2 & 0 & 0 \\ 0 & -1/24 & 0 \\ 0 & 0 & \frac{107}{32} \end{bmatrix} = \text{diagonal} = Y_D$$

$$\frac{3}{16} \cdot \frac{24}{8 \times 2} = \frac{9}{2}$$

$$\frac{16}{5} \cdot \frac{5}{80}$$

$$\frac{80 - 27 + 27}{32} = \frac{80}{32}$$

$$Y_1 = T_1^{-1} T_2^{-1} T_3^{-1} Y_D T_3^T T_2^T T_1^T$$


$$Y_1 = \begin{bmatrix} 1 & 0 & 0 \\ -1/6 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ -3/4 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 9/2 & 1 \end{bmatrix} Y_D \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 9/2 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & -3/4 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & -1/6 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 & 0 \\ -1/6 & 1 & 0 \\ -3/4 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 9/2 & 1 \end{bmatrix} Y_D \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 9/2 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & -1/6 & -3/4 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 & 0 \\ -1/6 & 1 & 0 \\ -3/4 & 9/2 & 1 \end{bmatrix} Y_D \begin{bmatrix} 1 & -1/6 & -3/4 \\ 0 & 1 & 9/2 \\ 0 & 0 & 1 \end{bmatrix} = T^{-1} Y_D T^T = Y_1$$



$$T^T i_a + b_p = 0$$

$$v_a = T^{-T} v_p$$

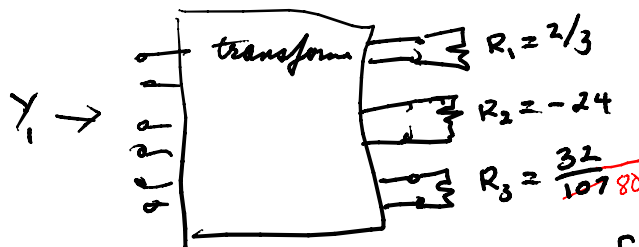

here

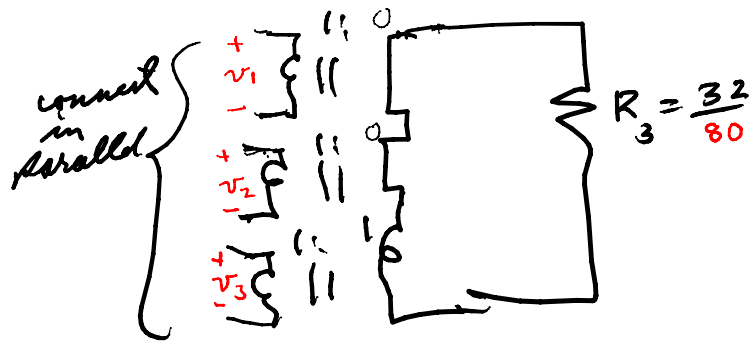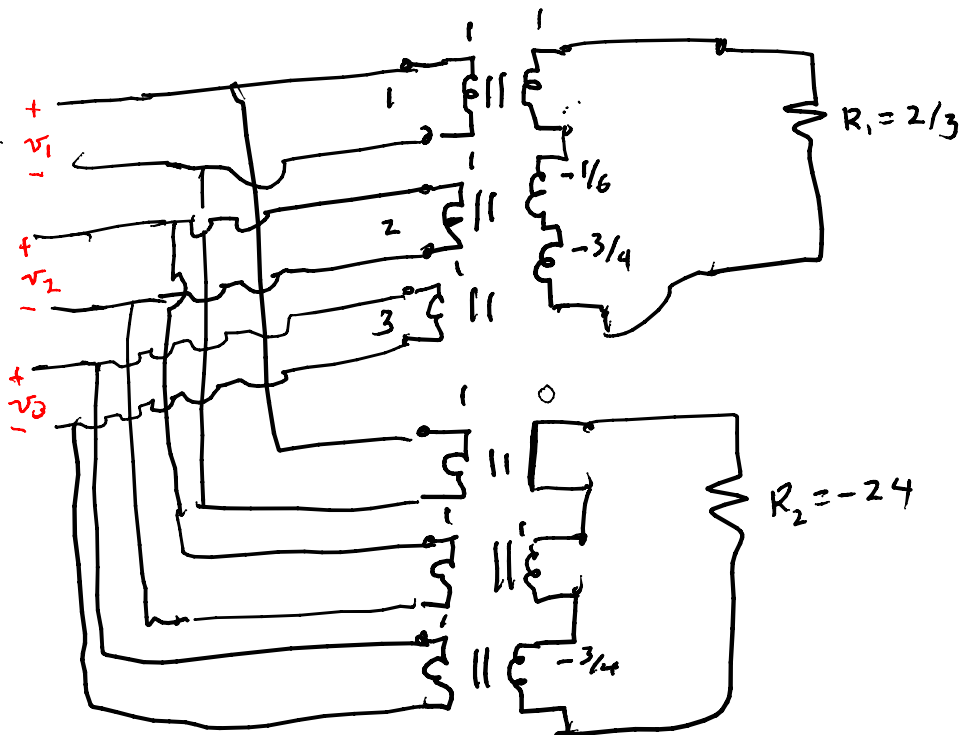
$$\begin{bmatrix} 1 & 0 & 0 \\ -1/6 & 1 & 0 \\ -3/4 & 9/2 & 1 \end{bmatrix} \begin{bmatrix} i_{a1} \\ i_{a2} \\ i_{a3} \end{bmatrix} = - \begin{bmatrix} i_{p1} \\ i_{p2} \\ i_{p3} \end{bmatrix} ; \begin{bmatrix} v_{a1} \\ v_{a2} \\ v_{a3} \end{bmatrix} = \begin{bmatrix} 1 & -1/6 & -3/4 \\ 0 & 1 & 9/2 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_{p1} \\ v_{p2} \\ v_{p3} \end{bmatrix}$$



$$Y_2 = \begin{bmatrix} 0 & -1/4 & -1/8 \\ 1/4 & 0 & 0 \\ 1/8 & 0 & 0 \end{bmatrix} \Rightarrow$$


$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & -1/8 & 1 \end{bmatrix} \begin{bmatrix} 0 & -1/4 & -1/8 \\ 1/4 & 0 & 0 \\ 1/8 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & -1/2 \\ 0 & 0 & 1 \end{bmatrix}$$
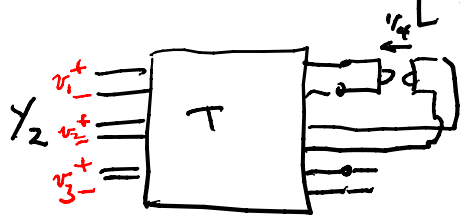
$$= \begin{bmatrix} 0 & -1/4 & 0 \\ 1/4 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \text{ is rank 2} \Rightarrow 1 \text{ qypter}$$



put in parallel with Y_1 circuit & connect capacitors on ports 2 & 3

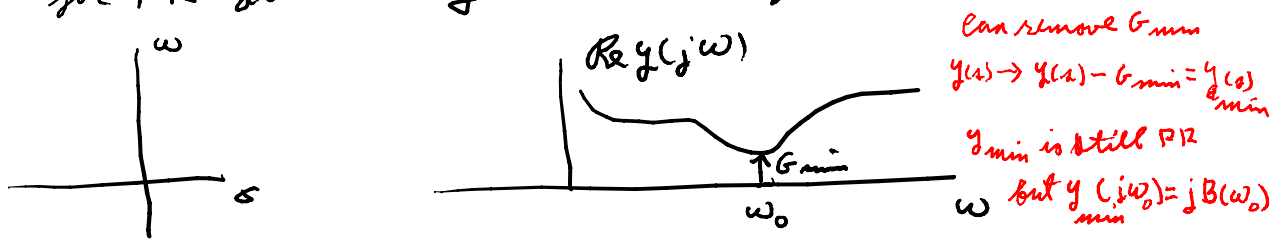Bott-Duffin synthesis \Rightarrow uses no transformers for PR $Y(s)$ using Richards' function



\therefore assume $Y(s)$ has $Re Y(j\omega_0) = 0$; $Y(j\omega_0) = 0 + jB(\omega_0)$


$$Y_R = \frac{kY(k) - sY(s)}{kY(s) - sY(k)} \Rightarrow kY(s)Y_R - sY(k)Y_R = kY(k) - sY(s)$$

$$Y(s) [kY_R + s] = kY(k) + sY(k)Y_R$$

$$Y(s) = \frac{kY(k) + sY(k)Y_R}{s + kY_R} = \frac{1}{\frac{s + kY_R}{kY(k)}} + \frac{1}{\frac{s + kY_R}{sY(k)Y_R}}$$

$$= \frac{1}{\frac{s}{kY(k)} + \frac{Y_R}{Y(k)}} + \frac{1}{\frac{s}{Y(k)Y_R} + \frac{k}{sY(k)}}$$

every term here is PR if $k > 0$

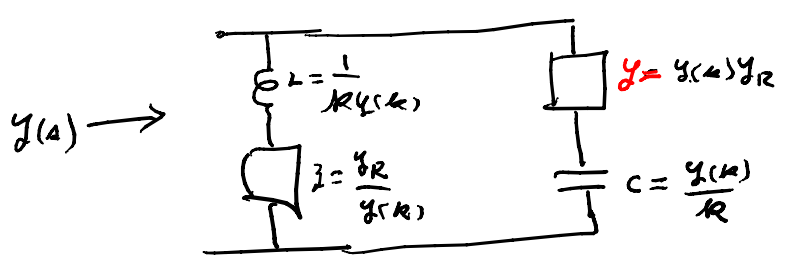

Note: This is a balanced bridge as the product of cross-arm admittances is $Y(k)^2$

Next choose k so $Y_R(j\omega_0) = 0$ or ∞ so can remove a $j\omega_0$ pole of $1/Y_R$ or Y_R which decreases the degree by 2 after the poles are removed. There is always a $k > 0$ to do this so Y_R is PR

