


EE 610 Final Exam Fall 2008

Take Home. Open Book Open Notes 200 points total

Due in Room AVW 1364 at the final period W 12/17/08

along with your notebook. Your signature certifies that the work is your own.

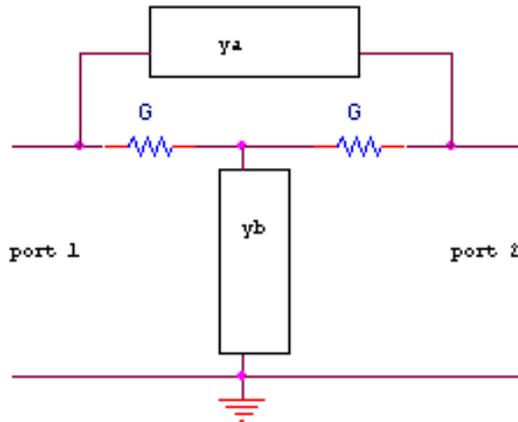1. (50 points) [Y matrix & constant-R 2-port]



For the above circuit $y_a(s)$, $y_b(s)$ and G are 1-port admittances and conductance with constant $G > 0$,

- Give the 3x3 nodal admittance matrix and from it obtain the 2-port $Y(s)$ matrix by eliminating the internal node (which should be numbered 3).
- When a load of conductance G is placed on port 2 find the relationship between $y_a(s)$ and $y_b(s)$ such that the input admittance is G (the 2-port is then called a constant-R 2-port)
- For the constant-R 2-port loaded in conductance G , find the voltage transfer function $V_2(s)/V_1(s)$ [express it in terms of G and $y_a(s)$].
- Given that it is desired to synthesize $V_2(s)/V_1(s) = ks/(s^2 + s + 1)$ by this constant-R circuit, give $y_a(s)$ and the range of real k and G such that $y_a(s)$ is PR.

2. (50 points) [even parts]


- Find the zeros of the even part, $Ev[y(s)]$, of
 - $y(s) = [s^2 + 3s + 4]/[s^2 + 6]$
 - $y(s) = [s^2 - 3s + 4]/[s^2 + 6]$
- Comment upon uniqueness of a PR $y(s)$ if only given its $Ev[y(s)]$.
- Show that if k is a zero of the even part of $y(s)$ it is also a zero of the even part of $z(s) = 1/y(s)$ with some exceptions. Consider $y(s) = s/(s+1)$ and discuss exceptions.
- It is possible that there are no zeros of the even part of $y(s)$. Give necessary and sufficient conditions for this to occur when $y(s)$ is PR.

3. (50 points) [Richards' function problem]

Assume that the even part of a PR admittance $y(s)$ is a positive constant, G (independent of s). This $y(s)$ can be relatively easily synthesized.

- Give the partial fraction expansions of $y(s)$ and of $z(s)$ and the resulting syntheses.
- Discuss why there is no good choice of k for synthesis of $y(s)$ directly via the Richards' function. How about using $z(s)=1/y(s)$ instead.
- In view of b) and your result of a) show how the Richards' function can be used on $y(s)$ after an initial parallel resistor extraction.

4. (50 points) [Op-Amp]

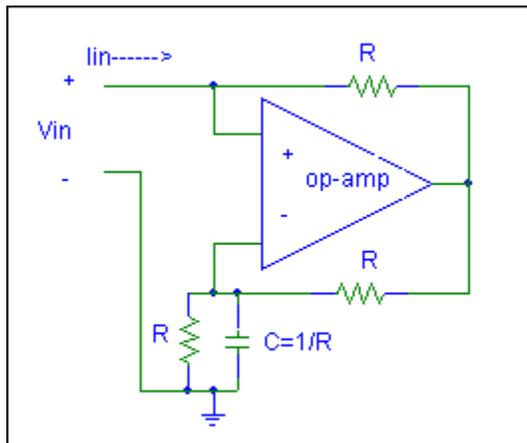

In this circuit the op=amp is ideal (zero input current and voltage).

- Give semi-state equations governing this circuit for V_{in} as the input and I_{in} as the output and the first component of the semi-state being the capacitor voltage. If possible reduce these to state-variable form with the state being the capacitor voltage.
- Give the input admittance $y(s)$.
- This circuit requires the input admittance to be taken with one terminal at ground. If the same admittance is needed to be for a floating 1-port discuss how you might modify this circuit to obtain such.
- Discuss how you would proceed if the op-amp saturates at V_{dd} and $V_{ss}=-V_{dd}$.