

$$\#1. a) I_{C_{Q_1}} = I_{C_{Q_2}} = 2 \text{ mA} \Rightarrow I_1 = I_{C_{Q_1}} + I_{C_{Q_2}} = 4 \text{ mA}$$

$$\text{at } \beta = 100 \text{ \& } I_C = \beta I_B \Rightarrow I_{B_{Q_1}} = I_{B_{Q_2}} = \frac{1}{\beta} \times \frac{I_1}{2} = \frac{2 \times 10^{-3}}{10^2} = 20 \times 10^{-6}$$

$$\therefore I_2 = I_{B_{Q_1}} = 20 \mu\text{A} \quad (\text{also} = I_{B_{Q_2}})$$

$$\text{For } I_3: I_3 = -I_{E_{Q_1}} - I_{E_{Q_2}} \quad \text{since } I_B + I_C + I_E = 0 \Rightarrow -I_E = I_B + I_C$$


$$= -(I_{C_{Q_1}} + I_{B_{Q_1}}) - I_{B_{Q_2}}$$

$$= -I_{C_{Q_1}} = 2 \text{ mA} = I_3$$


$$b) g_m = \frac{I_C}{V_T} = \frac{2 \times 10^{-3}}{26 \times 10^{-3}} = \frac{1}{13}$$

$$g_{\pi} = \frac{g_m}{\beta} = \frac{1/13}{100}$$
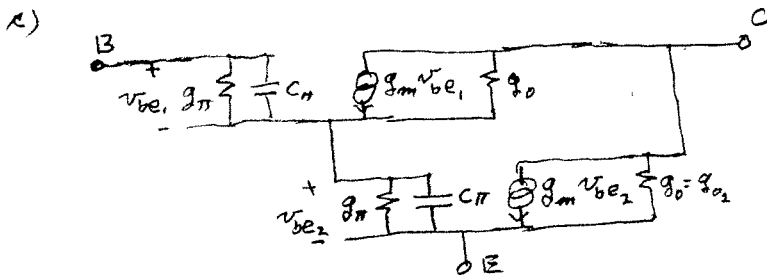
$$g_o = \frac{I_C}{V_A} = \frac{2 \times 10^{-3}}{100} = 2 \times 10^{-5}$$



$$d) y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0 = \text{short}} \Rightarrow$$

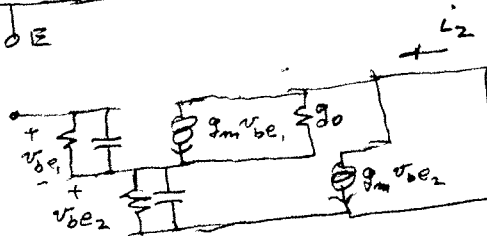

$$v_1 = v_{be1} + v_{be2}, \quad i_2 = g_m v_{be1} + g_m v_{be2} + g_o (-v_{be2})$$

$$= g_m (v_{be1} + v_{be2}) - g_o v_{be2} = g_m v_1 - g_o v_{be2} \quad (*)$$

$$\text{To get } v_{be2}: \text{For } Q_1, i_1 = g_{\pi} v_{be1}, \quad y_{\pi} = g_{\pi} + sC_{\pi}$$

$$\text{For } Q_2: i_1 + (g_m v_{be1} + g_o (-v_{be2})) = y_{\pi} v_{be2}$$

$$= (g_{\pi} + g_m) v_{be1} - g_o v_{be2} \Rightarrow (g_o + y_{\pi}) v_{be2} = (g_m + y_{\pi}) v_{be1}$$

$$\text{at } v_{be1} = v_1 - v_{be2} \Rightarrow (g_o + y_{\pi}) v_{be2} = (g_m + y_{\pi}) v_1 - (g_m + y_{\pi}) v_{be2}$$

$$\Rightarrow (g_o + g_m + 2y_{\pi}) v_{be2} = (g_m + y_{\pi}) v_1 \quad (**)$$

from (\*\*) into (\*)

$$\frac{i_2}{v_1} = g_m - \frac{g_o (g_m + y_{\pi})}{g_o + g_m + 2y_{\pi}} = \frac{g_m^2 + (2g_m - g_o)(g_{\pi} + sC_{\pi})}{g_o + g_m + 2(g_{\pi} + sC_{\pi})} = y_{21}$$

#2 a) If  $V_{in1} > V_{in2}$ , the drains are on the left & sources on the right  
so  $V_{GS} < 0$  for  $M_1 \Rightarrow M_1$  off.

If  $V_{in2} > V_{in1}$ , then reverse 1 & 2 of previous  $\Rightarrow M_2$  off by symmetry

b)  $V_{in1} > V_{in2}$ :  $M_1$ :  $d = I_{in1}$ ,  $s = out$  for  $M_2$ :  $d = out$ ,  $s = I_{in2}$

$V_{in2} > V_{in1}$ :  $M_1$ :  $d = out$ ,  $s = I_{in1}$  for  $M_2$ :  $d = I_{in2}$ ,  $s = out$

c) As one transistor always has  $I_D = 0$  then both have  $I_D = 0$

But when  $V_{in1} > V_{in2}$ , then  $V_{GS2} > 0$  &  $M_2$  has its  $I_D$  vs  $V_{DS}$  curve  
intersect the origin  $\Rightarrow V_{DS2} = 0 \Rightarrow V_{out} = V_{in2} < V_{in1}$

If  $V_{in1} < V_{in2}$  then  $V_{DS1} = 0$  by symmetry  $\Rightarrow V_{out} = V_{in1} < V_{in2}$

If  $V_{in1} = V_{in2}$  then  $V_{out} = V_{in1} = V_{in2}$ , so

$$V_{out} = \min(V_{in1}, V_{in2})$$

#3,

$$a) g_m = \frac{\partial i_{out}}{\partial v_{in}} = \frac{\partial \alpha I_T \sinh(v_i/2V_T)}{\partial v_i} = \alpha I_T \cdot \frac{1}{2V_T} \cdot \left. \frac{\partial \sinh x}{\partial x} \right|_{x=0 = v_i/2V_T}$$

$$\sinh x = \frac{1}{2}(e^x - e^{-x}); \quad \frac{d \sinh x}{dx} = \frac{1}{2}(e^x + e^{-x}) = \cosh x, \quad \cosh 0 = \frac{1}{2}(1+1) = 1$$

$$\therefore g_m = \alpha \frac{I_T}{2V_T}$$

$$b) i_1 = g_m v_1 \Rightarrow y_{11} = g_m, \quad y_{12} = 0$$

$$i_2 = i_o = g_m v_1 + \alpha C v_o = g_m v_1 + \alpha C v_2 = y_{21} v_1 + y_{22} v_2$$

$$\therefore Y(s) = \begin{bmatrix} g_m & 0 \\ g_m & \alpha C \end{bmatrix}$$

4. as no  $\delta$  is given, assume no body effect, that is  $\delta = 0$

if port 2 is open,  $i_2 = 0 \Rightarrow v_{z4} = 0 \Rightarrow v_{z3} = 0 \Rightarrow i_{z3} = 0 \Rightarrow i_{z2} = 0 \Rightarrow i_{z1} = 0 \Rightarrow v_{z1} = 0$   
 $\Rightarrow i_1 = 0 \Rightarrow y_m(\omega) = 0$

if port 2 is shorted,  $v_{z3} + v_{z4} = 0 \Rightarrow v_{z1} + v_{z2} = 0 \Rightarrow$  input open  $\Rightarrow y_m(\omega) = 0$