


303 Fall 2009 – Midterm Exam Th 11/05/09

Open book open notes but not open computers; 150 points total; if stuck go on to the next problem. Good luck


DATA: For DC characterization of NMOS transistors assume $K_P=2\text{mA}/\text{V}^2$, $W=L$, $V_{TO}=2\text{V}$, $LAMBDA=0$

1. (50 points, 15 min)

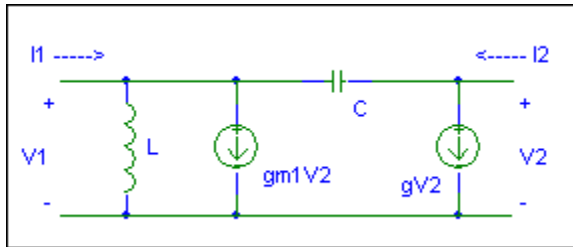a) For the following circuit find the admittance matrix $Y(s)$ as a function of complex frequency s .



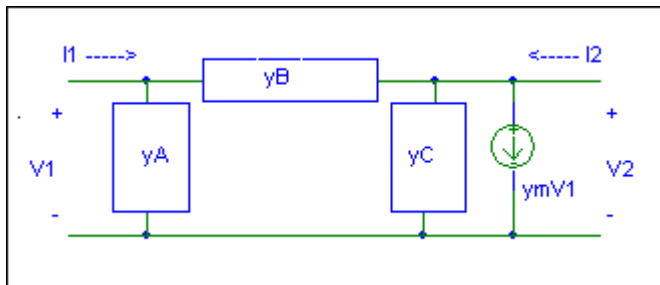b) Give the admittances $y_A(s)$, $y_B(s)$, $y_C(s)$, $y_m(s)$ for the following circuit to be equivalent at the ports to the one of part a).



2. (50 points, 25 min)

For the following circuit when M2 is on use for i_{D2} [from the formula (7.19) p. 694]


$$i_{D2} = I_T \left[\frac{1}{2} - \left(a \frac{v_{id}}{2} \right) \sqrt{1 - \left(a \frac{v_{id}}{2} \right)^2} \right] \quad \text{where } a = \sqrt{\frac{KP}{I_T} * \frac{W}{L}}$$

also

$$V_{ov} = \frac{1}{a}$$

Choose $V_{dd}=10V$, the tail current $I_T=8mA$ and the load resistor to be $R=V_{dd}/(2I_T)$.

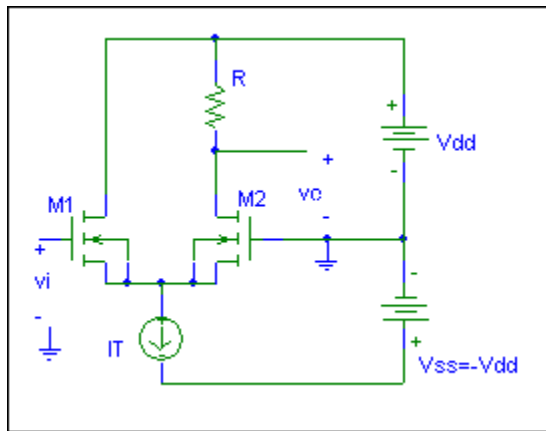- evaluate numerically a and V_{ov} of the above formulas and
- Determine V_o (numerically) as a function of the input voltage v_i and sketch for $-V_{dd} < v_i < V_{dd}$ indicating important points.



3. (50 points, 25 min)

Here $V_{dd}=10V$, $R=100 \text{ Ohm}$, $C=20nFd$. The circuit has had $v_i=0$ for $-\infty < t < 0$; v_i changes at $t=0$ to $V_{dd}/2$ [that is $v_i(t)=(V_{dd}/2)1(t)$ with $1(t)$ the unit step]. Write $v_d(t)$ for the voltage at the drain of the transistor.

- Find $v_d(0^+)$ [= $v_d(0^-)$].
- Find $v_d(+\infty)$, that is when M is on but $dv_d(t)/dt=0$. From this show that M is in the saturation region for $0^+ < t < +\infty$.
- Sketch the load line on two transistor [I_d versus V_d] curves holding for $t=0^-$ and for $t=+\infty$; use just one graph.
- Write the differential equation for $v_d(t)$ for $t > 0$, solve, and sketch the solution.

