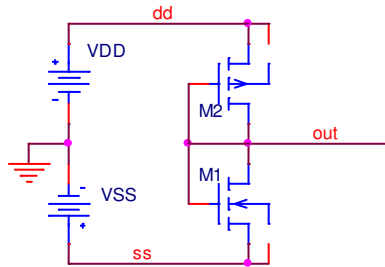



1. [40 points] [a DC voltage/current source]



For the above circuit assume that the transistors are the 4007 ones, the output voltage,  $V_{out}$ , is measured with respect to ground and  $V_{SS} = -V_{DD}$ ,  $V_{DD} > 2|V_{T0p}| > 0$  where  $V_{T0p}$  is the PMOS VTO. [note that  $V_{SS}$  is negative,  $V_{DD}$  is large enough to insure the transistors are turned on]

- Show that the transistors are in saturation.
- Ignore the Early effect, that is assume  $\lambda = 0$ . Calculate  $V_{out}$  in terms of  $V_{DD}$ .
- Calculate the current flowing in the drain of M1.
- If the gate and ~~drain~~ source of M3, another identical NMOS, are placed in parallel with the gate and source of M1, as a load on the output & ss leads, respectively, find the voltage on the drain of M3 needed to give the drain current in M3 to be the same as that in M1; M3 acts as a current source “sink.”

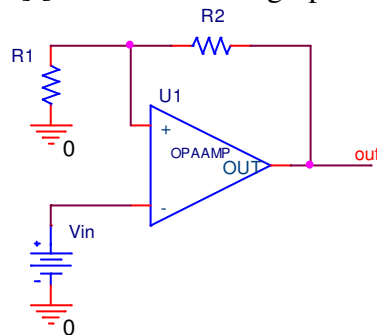2. [60 points] [load lines/running Spice for multi-valued curves]



Assume that the op-amp is biased with  $V_{CC} = -V_{EE} > 0$ , so that it saturates at these two voltages, and has otherwise infinite gain.

- Sketch as a set valued function the opamp curve of  $V_{out}$  versus  $V_d$  where  $V_d$  is the opamp input voltage. Label the saturation values.
- Give the equation for  $V_{out}$  versus  $V_d$  in terms of  $R_1$ ,  $R_2$  and  $V_{in}$ . This acts as a load line so sketch it for various values of  $V_{in}$  as a parameter. Sketch it on the sketch of the opamp characteristics.
- Choose the resistors so that hysteresis results, sketch the resulting hysteresis and give its width. Label saturation and jump points along with saturation values.
- Use a uA741 with  $V_{CC} = 10V$ ,  $R_1 = R_2 = 10K\Omega$  and run PSpice to obtain this hysteresis. Since the DC curve is multi-valued you will need to do a transient analysis by first replacing the DC source,  $V_{in}$ , by a piecewise linear voltage source, VPWL in PSpice, to give a triangular voltage (of peaks above and below the hysteresis breaks). Submit the hysteresis curve.