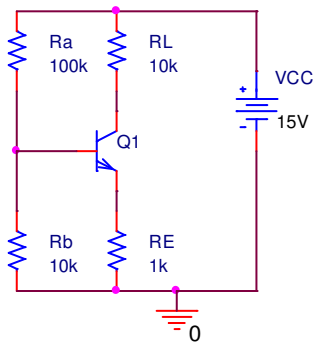



1. [50 points] [biasing a BJT]



For the above circuit the transistor is a 2N3904. [the models in the ECE PSpice bipolar library seem to be in error; use those on the 303H web page]. The problem is to check its biasing.

- Find the Q point for this circuit and give the voltages on Rb and RE, referenced to ground; also give the transistor Q point IC, IB, VCE, VCB.
- Run Spice and compare the Q point found in Spice with that found in part a).
- Do a parametric run in Spice for RE=500, 1K, and 2KOhms and compare the resulting Q points.

2. [50 points] [cascade current mirrors]

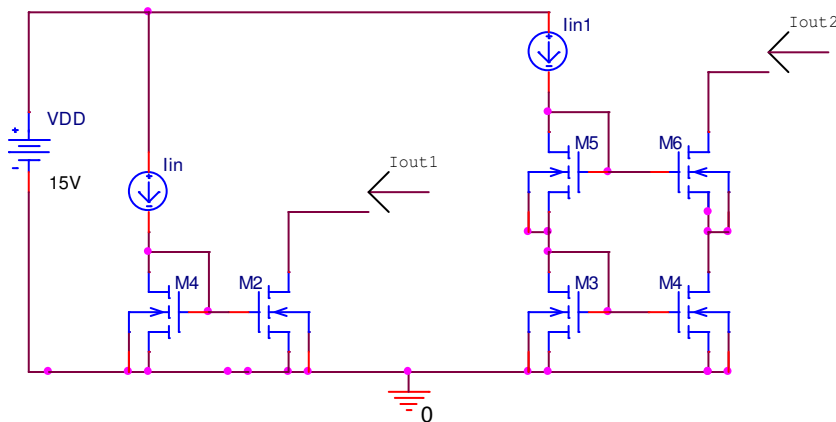

Here all transistors are 4007's and the problem is to show how the cascade current mirror is an improvement.

- Form the current sources  $I_{in}=I_{in1}$  by a 4007 PMOS and a source to gate voltage to give  $I_{in}$  to be 2mA.
- Apply DC sources to the drains of the two output transistors, M2 and M6. Find the minimum value of these voltages needed to keep M2 and M6 in saturation.
- Make the voltages of these two applied sources equal by making their values to be a parameter. Run a DC sweep in Spice varying this voltage parameter from 0 to VDD. Compare the two currents  $I_{out1}$  and  $I_{out2}$ ; plot their difference in PSpice as well as the actual currents; include  $I_{in}$  in your plots..