

1. [60 points] [gain of a source follower]

For the source follower of the small-~~frequency~~ signal equivalent circuit of Figure 6.51 (a), p. 638 of Sedra/Smith, [with symbolic but real parameters]

- Draw the full circuit diagram with the transistor symbol and biasing including an input coupling capacitor (note especially the bulk connection).
- Using node equations find the 1x2 transfer function matrix,  $T(s)$ , for the given equivalent circuit of the above mentioned figure. Here

$$[V_o] = T(s) \begin{bmatrix} V_{sig} \\ V_{bs} \end{bmatrix}$$

- Explain why the entries of the transfer function matrix are at most degree 2 in the complex frequency,  $s$ , even though there are three capacitors present {which normally means degree 3}.
- That being the case, the numerators and denominators can be factored exactly. Give the zeros and poles and indicate their relative positions in the complex  $s$ -plane.
- Sketch the {magnitude of the} frequency response of  $V_o/V_{sig}(j\omega)$  assuming  $V_{bs}=0$ ; repeat for  $V_o/V_{bs}(j\omega)$  assuming  $V_{sig}=0$  and compare.

2. [40 points] [cascade of inverters]

Use the 4007s to make CMOS inverters which are biased at  $V_{DD}=10V$  and  $V_{SS}=0$ .

- Connect the inverters in cascade as shown in Figure 11.1 (b), page 1014 of Sedra/Smith, and run Spice to obtain the curves of Figure 11.1 (c) [this is a DC run]. Plot  $v_x$  and  $v_z$  versus  $v_w$  as well as the straight line shown in that figure. Record the location of the points A, B and C and comment upon them with respect to  $V_{DD}$  {especially note B in relation to  $V_{DD}/2$ }.
- Connect the inverters as shown in Figure 11.1 (a) and obtain Spice runs of the three voltages (now in time via transient response). Submit those as well as  $v_x$  and  $v_z$  versus  $v_w$ . You will probably need to move off of an equilibrium point, which can be done by shocking the W lead with a short current source pulse.
- Insert a capacitor,  $C_w$ , of 10nFd from W to ground and repeat part b) above for various initial conditions on  $C_w$ , especially ones for the points A, B, C.