

Transistors = transfer resistor



EE303H

09/03/09




BJT = bipolar junction transistor

MOS = metal oxide silicon




BJT

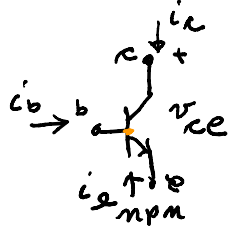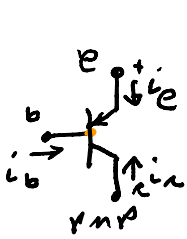

e = emitter
b = base
c = collector

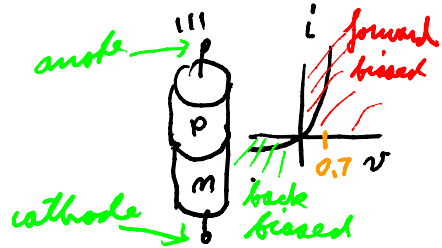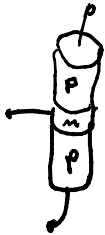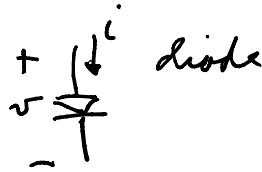


original

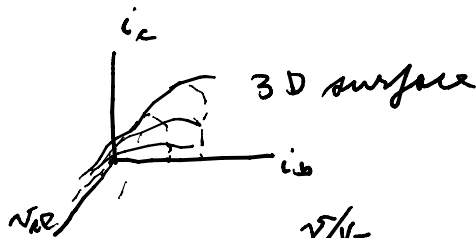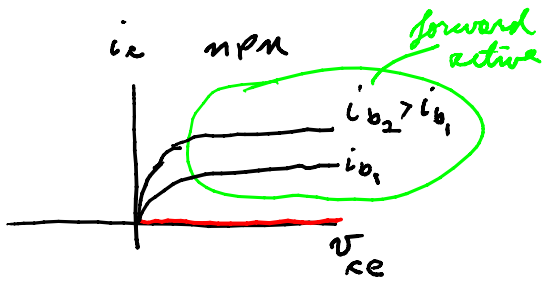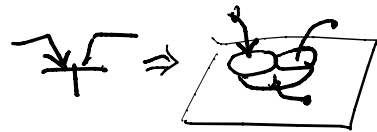


has equations which are exponential since

in constructing the base is very thin so $|i_c| \approx |i_e|$

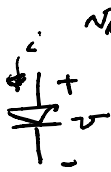

$$i = I_s (e^{v/V_T} - 1)$$

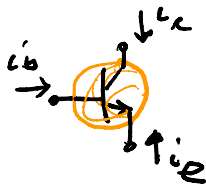I_s = saturation current
 V_T = thermal voltage
 $= \frac{kT}{q}$; T = temperature



by KCL $i_b + i_c + i_e = 0$

Here $i_c = -\alpha i_e$; $\alpha \approx 1$
 < 1

$$i_b + i_c + (-\frac{1}{\alpha} i_c) = 0$$


$$i_b = (\frac{1}{\alpha} - 1) i_c = \frac{1-\alpha}{\alpha} i_c$$

$$\Rightarrow i_c = \frac{\alpha}{1-\alpha} i_b = \beta i_b$$


$\beta = \text{beta} = \frac{\alpha}{1-\alpha}$ large
($\approx 50 \rightarrow 500$)

(forward beta = $\beta_F = \text{BETA F}$)


MOS

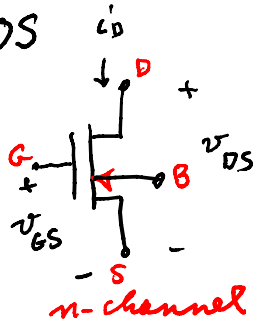

n-channel

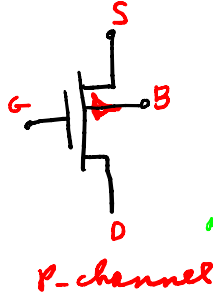


p-channel

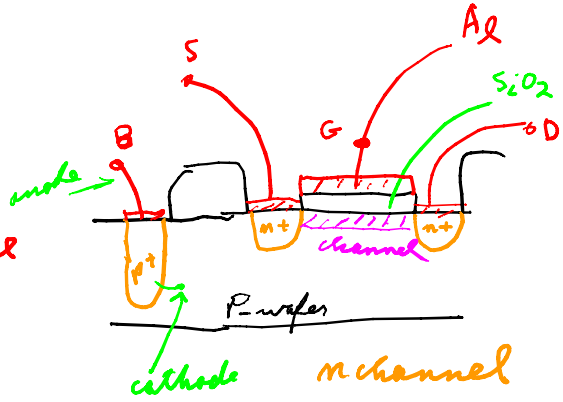


- B = bulk
- D = drain
- G = gate
- S = source


↓ if B is connected to S

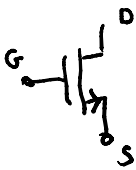


for a p channel

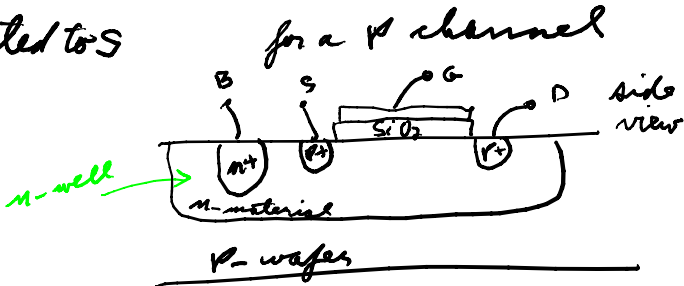

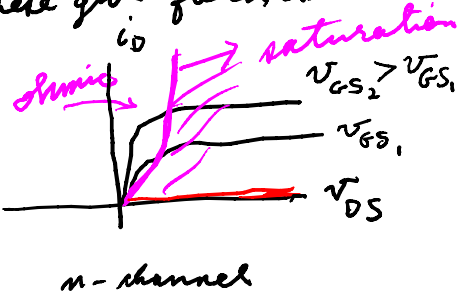these give quadratic curves (if operate above threshold)



n-channel

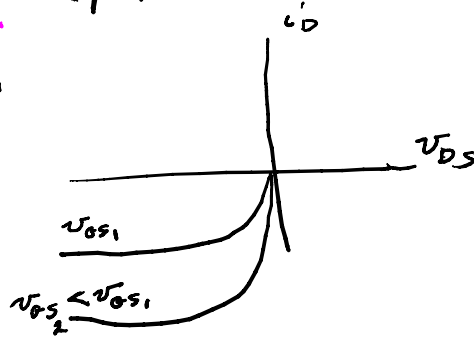


p-channel

equations

$$i_D = \begin{cases} 0 & \text{if } V_{DS} \leq V_{TO} = \text{turn on voltage} \\ \frac{K_P W}{2 L} \left\{ \begin{array}{ll} (V_{GS} - V_{TO})^2 & \text{if } V_{DS} > V_{GS} - V_{TO} \text{ saturation} \\ 2(V_{GS} - V_{TO})V_{DS} - V_{DS}^2 & \text{if } 0 \leq V_{DS} \leq V_{GS} - V_{TO} \end{array} \right. \end{cases}$$

ohmic = triode

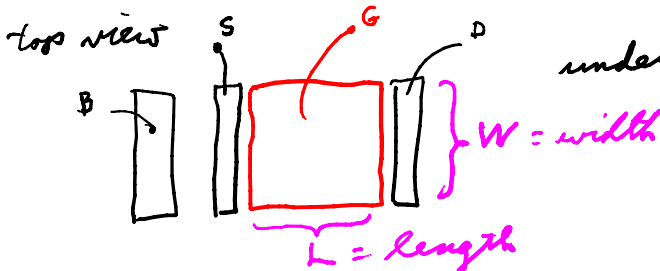

under G is the channel

