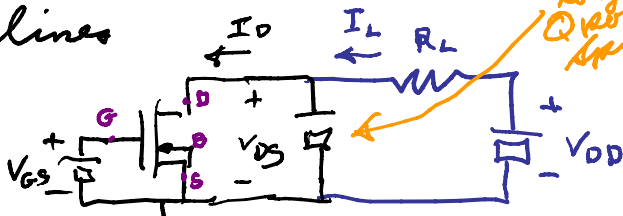


Homework for today due on Tu

EE 303H
09/15/09

Load lines



$$+V_{DS} + R_L I_L - V_{DD} = 0$$



KVL

$$R_L I_L = +V_{DD} - V_{DS}$$

$$I_L = G_L V_{DD} - G_L V_{DS}$$

if $I_L = 0$, $V_{DS} = V_{DD}$

slope = $-G_L$ for I_L/V_{DS}

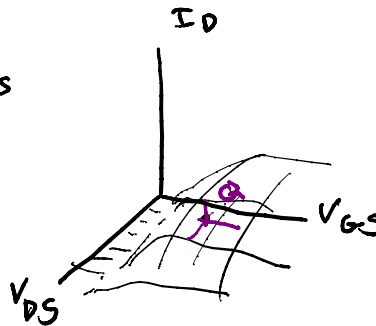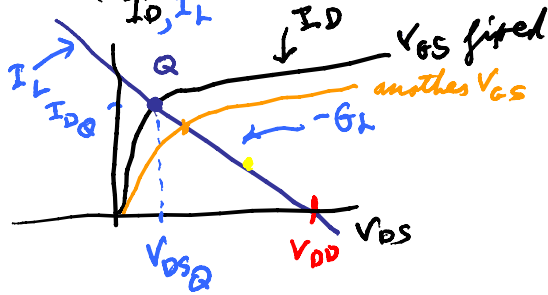

$$I_D = f(V_{GS}, V_{DS}) = \text{DC version}$$

$$i_D = f(V_{GS}, V_{DS}) \text{ for total behavior}$$

V_{DS} (ignore for now)

$$i_D = I_D + \left. \frac{\partial f}{\partial V_{GS}} \right|_Q (v_{GS} - V_{GS}) + \left. \frac{\partial f}{\partial V_{DS}} \right|_Q (v_{DS} - V_{DS}) + \text{higher order terms}$$

$$i_D - I_D = i_d \text{ signal current}$$

$$v_{GS} - V_{GS} = v_{gs} \text{ signal voltage, gate to source}$$

$$v_{DS} - V_{DS} = v_{ds} \text{ " " drain to source}$$


$$i_d = \left. \frac{\partial f}{\partial V_{GS}} \right|_Q v_{gs} + \left. \frac{\partial f}{\partial V_{DS}} \right|_Q v_{ds}$$

for $\left. \frac{\partial f}{\partial V_{DS}} \right|_Q$ hold $v_{GS} = V_{GS}$


= slope @ the Q point

= incremental drain to source conductance



$$= g_o$$

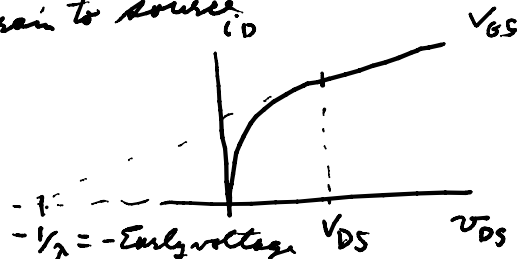


for $\left. \frac{\partial I_D}{\partial V_{GS}} \right|_{Q=V_{DS}=\text{constant}}$
small changes around V_{GS}
 $= g_m = \text{mutual conductance}$
 $= \text{transconductance}$

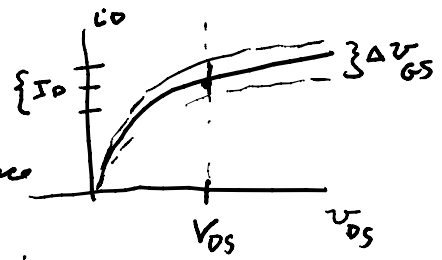

$$i_d = g_m v_{gs} + g_o v_{ds}$$

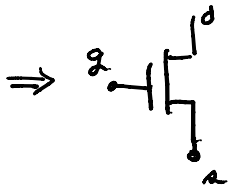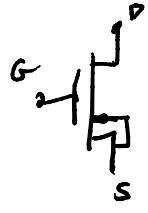

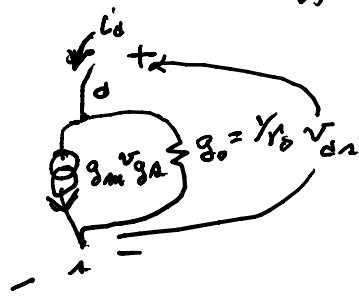\Rightarrow equivalent circuit for small signals





If NMOS is at a Q point in its saturation region

$$I_D = \frac{K_P W}{2 L} (V_{GS} - V_{TO})^2 (1 + \lambda V_{DS})$$

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_Q = 2 \left(\frac{K_P W}{2 L} \right) (V_{GS} - V_{TO}) (1 + \lambda V_{DS}) \Big|_Q = \frac{2 \left(\frac{K_P W}{2 L} \right) (V_{GS} - V_{TO}) (1 + \lambda V_{DS})}{(V_{GS} - V_{TO})} \Big|_Q = \frac{2 I_D}{V_{GS} - V_{TO}}$$


$$g_o = \left. \frac{\partial I_D}{\partial V_{DS}} \right|_Q = \left(\frac{K_P W}{2 L} \right) (V_{GS} - V_{TO})^2 \lambda \Big|_Q = I_D \lambda \frac{1}{1 + \lambda V_{DS}}$$

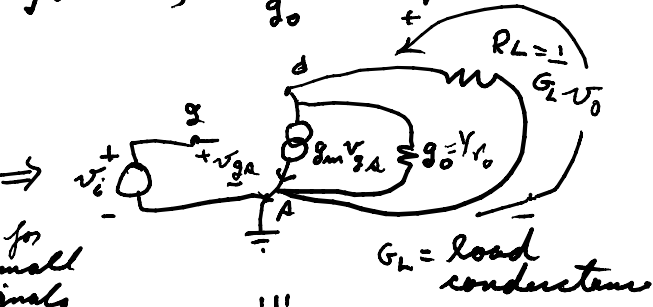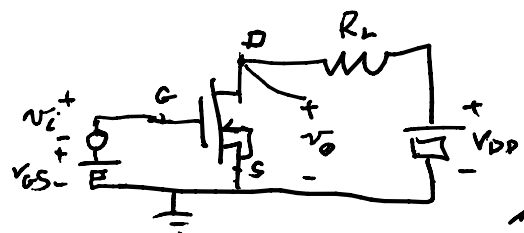usually small, $r_o = \frac{1}{g_o}$ is large







$$v_o = \frac{1}{G_{out}} (-g_m v_i)$$

$$= -\frac{g_m}{G_{out}} v_i$$

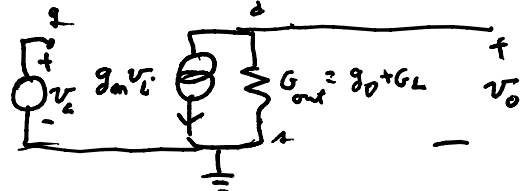

$$\frac{v_o}{v_i} \approx -g_m R_L \quad \text{slow small signal (DC)}$$

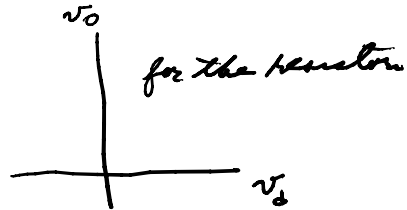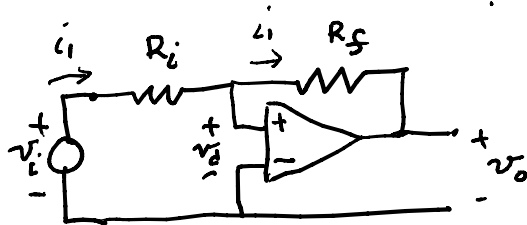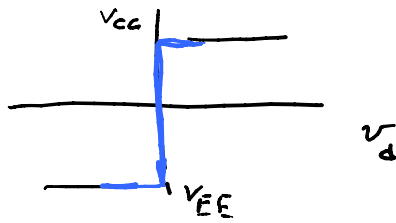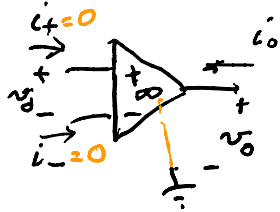Load line on op-amp for large signal at low frequency



$$\begin{cases} (v_i - v_d) = R_i i_i \\ (v_d - v_o) = R_f i_i \end{cases} \Rightarrow v_i - v_d = \frac{R_i}{R_f} (v_d - v_o)$$

$$v_i - (1 + \frac{R_i}{R_f}) v_d = -\frac{R_i}{R_f} v_o$$

$$v_o = -\frac{R_f}{R_i} v_i + (1 + \frac{R_f}{R_i}) v_d$$

