
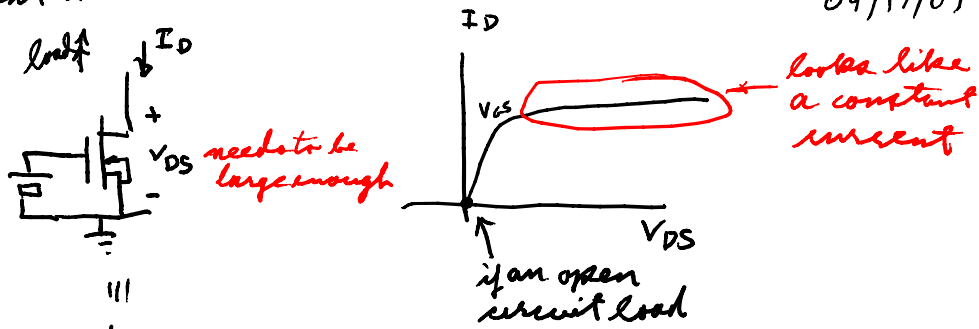


Current sources - mirrors


EE303H  
09/17/09

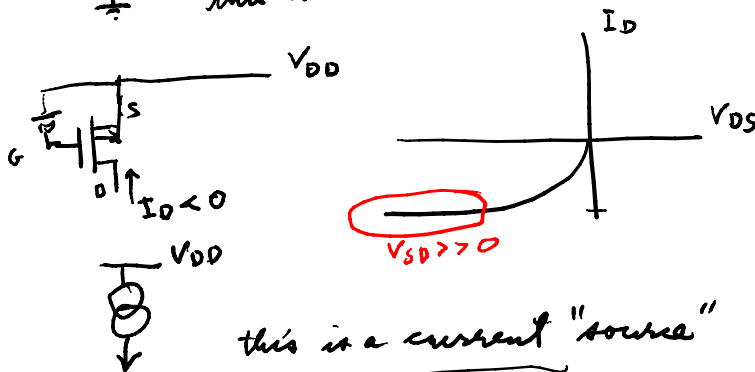

this is a current "sink"



this is a current "source"


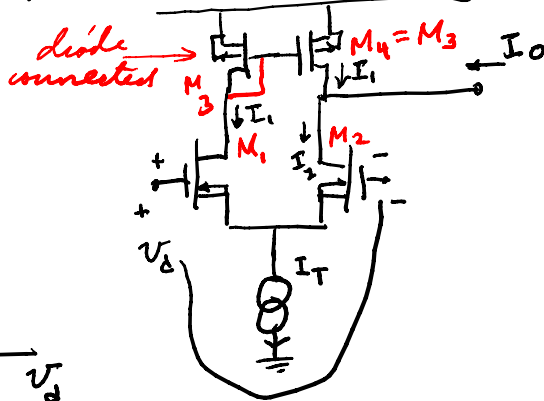


OTA = operational transconductance amplifiers


$I_T$  = tail current source

when  $V_d >> 0$ ,  $I_T$  goes all through  $M_1$

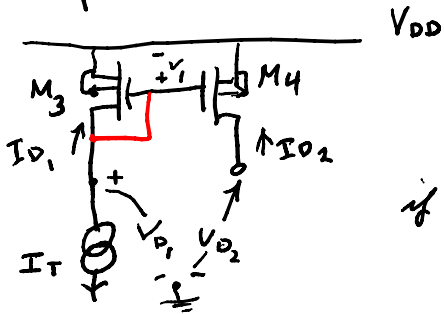
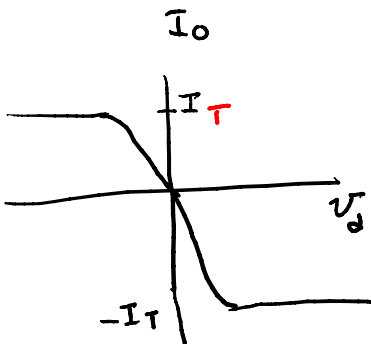
$V_d << 0$   $I_T$  goes all through  $M_2$   
( $I_1 = 0, I_2 = I_T$ )



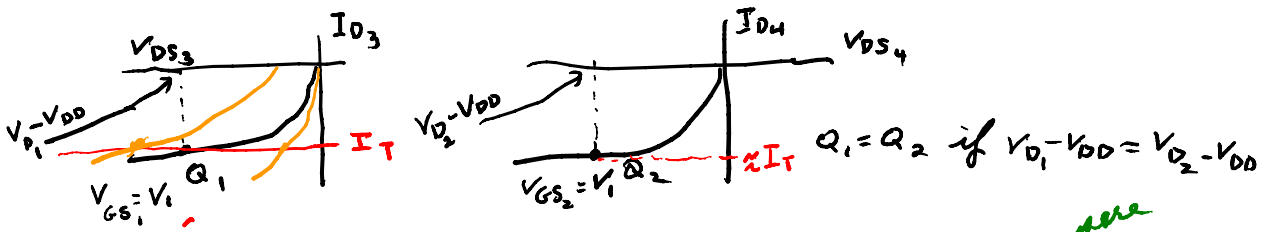if  $V_{d1} = V_{d2}$  then  $I_{D1} = I_{D2}$  if  $M_3 = M_4$   
as both would have the same operating point



short G to Drain  $M_3$

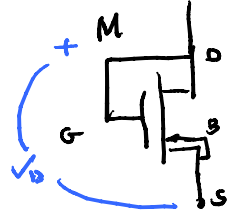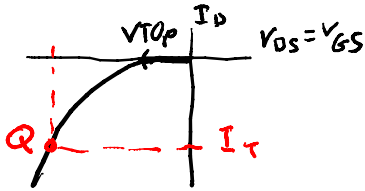


$V_{GS} - V_{TO_n}$  *sumere*  $V_{DS}$   
 here  $V_{DS} = V_{GS}$   
 $V_{GS} - V_{TO_n} = V_{DS} - V_{TO_n} < V_{DS}$   
 if  $V_{TO_n} > 0$  then  $M$  is in saturation


$$I_D = \frac{K_P W}{2 L} (V_{GS} - V_{TO_n})^2 = \frac{K_P W}{2 L} (V_D - V_{TO_n})^2$$

(for  $V_{GS} = V_D > V_{TO_n}$ )
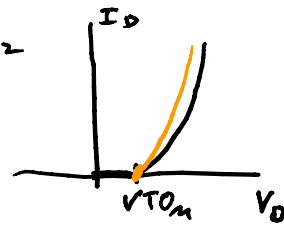
$$= \frac{K_P W}{2 L} (V_D - V_{TO_n})^2 (1 + \lambda V_D)$$


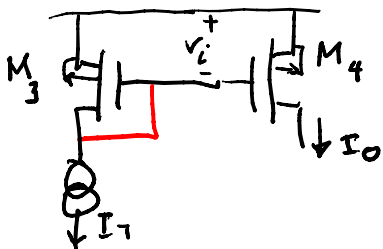
$$V_D = V_{TO_n} + \sqrt{\frac{I_T}{\frac{K_P W}{2 L}}} \quad \text{for } I_T > 0$$




$$I_O = -I_{D_{M4}} = \frac{K_P W}{2 L} (V_i - |V_{TO_p}|)^2 \quad \text{if } M_4 \text{ is in saturation}$$



where  $V_i = |V_{TO_p}| + \sqrt{\frac{I_T}{\frac{K_P}{2} \left(\frac{W}{L}\right)_3}}$

$$I_O = \left(\frac{K_P}{2}\right) \left(\frac{W}{L}\right)_4 \left(\sqrt{\frac{I_T}{\frac{K_P}{2} \left(\frac{W}{L}\right)_3}}\right)^2$$

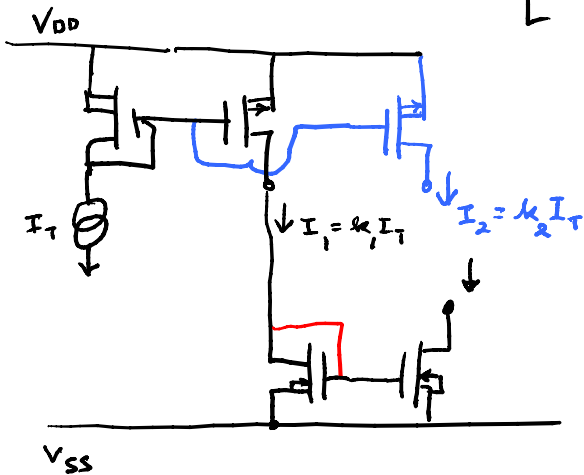
$$= \left[\frac{\left(\frac{W}{L}\right)_4}{\left(\frac{W}{L}\right)_3}\right] I_T$$



Using in the OTA

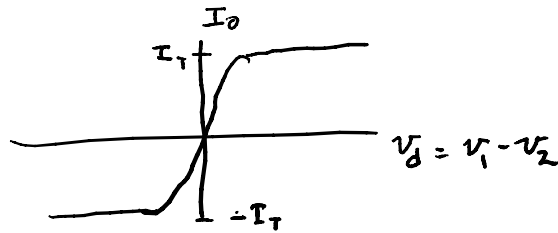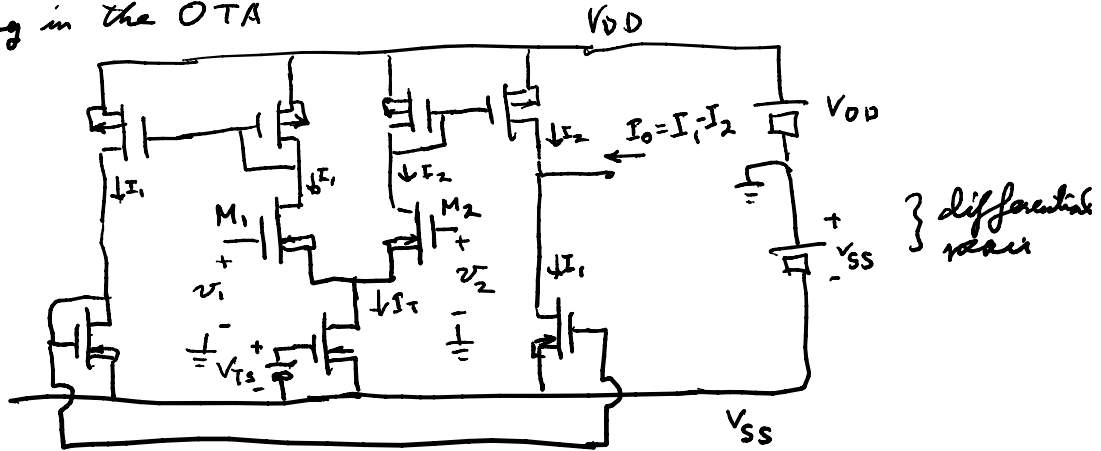

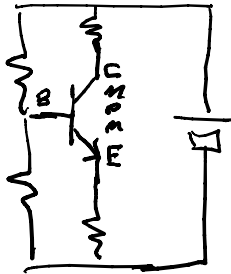BJT equivalent circuit (we use 2-port Y matrices appendix B, B2)



back biased C-B diode  
n-p

forward biased B-E diode  
p-n

$$i_c \approx \beta i_B e^{v_{BE}/V_T}$$

$$-i_E = I_S e^{v_{BE}/V_T}$$

$$V_T = kT/q$$

For small signal behaviours desire the Q point & make a Taylor series expansion of  $i_c$

