
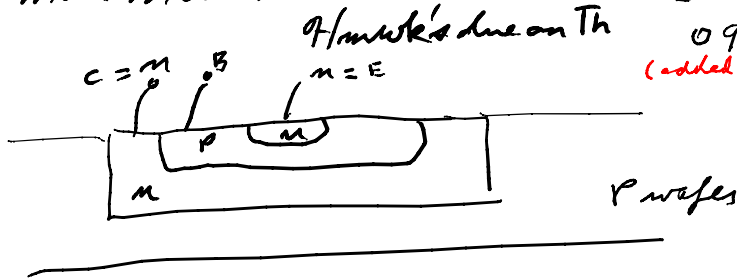


P. 387 = Ebers-Moll Model


EE 303H

09/24/09


(added notes 09/25)

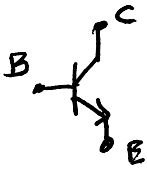



Homework due on Th

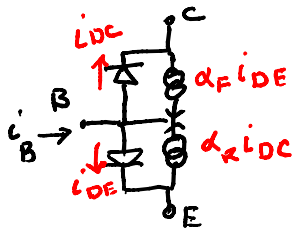

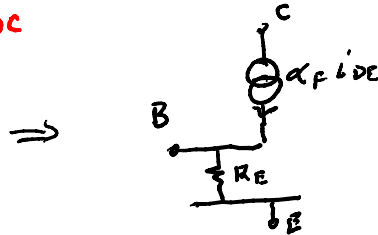for small signal back bias B-C
forward bias B-E


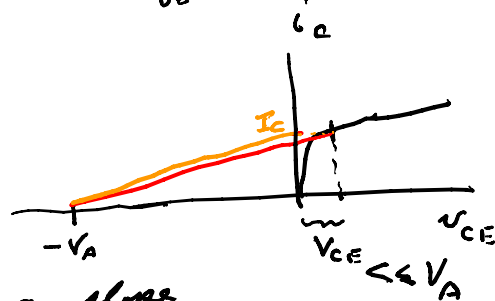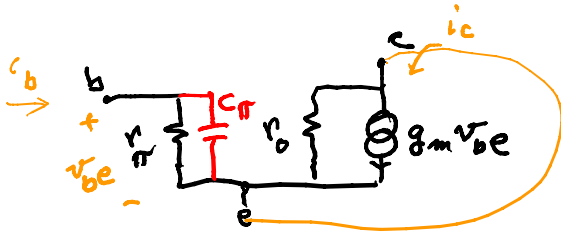
$$-\frac{\partial I_E}{\partial V_{BE}} = \frac{1}{R_E}$$



$$g_0 = \text{slope} = \frac{I_C}{V_A + V_{CE}} \approx \frac{I_C}{V_A}$$

$$g_{\pi} = -\frac{\partial I_E}{\partial V_{BE}}$$

$$g_m = I_C / V_T$$

$$g_{\pi} = \frac{I_C}{V_T} \cdot \frac{1}{\beta} = \frac{g_m}{\beta}$$

$$\frac{i_C}{i_b} \Big|_{V_{CE}=0} \Rightarrow$$


$$i_b = (g_{\pi} + \alpha C_{\pi}) v_{be}$$

$$i_c = g_m v_{be}$$

$$\therefore \frac{i_c}{i_b} = \frac{g_m}{g_{\pi} + \alpha C_{\pi}} = \frac{g_m / g_{\pi}}{1 + \alpha C_{\pi} / g_{\pi}}$$

evaluate @ $s = j\omega$

Frequency response $\left| \frac{i_c}{i_b}(j\omega) \right| = \frac{\beta}{\left| 1 + j\omega \frac{C_{\pi}}{g_{\pi}} \right|} = \frac{\beta}{\sqrt{1 + \omega^2 \frac{C_{\pi}^2}{g_{\pi}^2}}}$

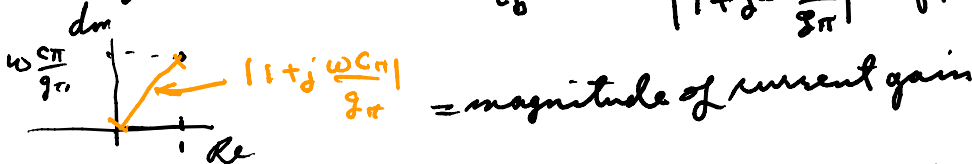


when $\left| \frac{i_c}{i_b}(j\omega) \right| = 1$ stops amplifying, that frequency is f_T $\omega_T = 2\pi f_T$



$$\beta^2 = 1 + \omega_T^2 \frac{C_{\pi}^2}{f_{\pi}^2}; \quad \omega_T = \sqrt{\frac{\beta^2 - 1}{C_{\pi}^2 / g_m^2}}$$

f_T is specified in data sheets

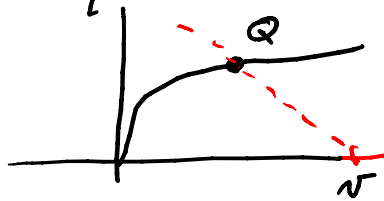--- Biasing; bias is the quiescent point = Q point (at DC)



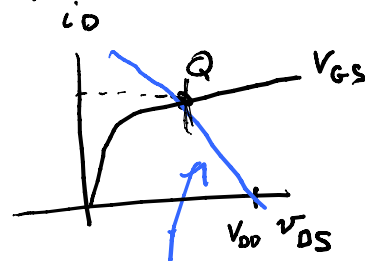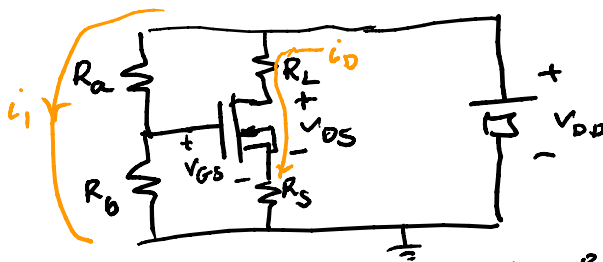For an MOS transistor we want to fix V_{GS}, V_{DS}



1) $V_{DD} = (R_a + R_b) i_1$

2) $V_{DD} = (R_L + R_S) i_D + V_{DS}$

3) $V_{GS} = R_b i_1 - R_S i_D$

here R_S is such that $V_{GS} \downarrow$ if $I_D \uparrow$ or stabilizes to changes in I_D

$$i_D = \frac{V_{DD} - V_{DS}}{R_L + R_S}$$

1) solved for $i_1 \rightarrow 3$ $V_{GS} = \frac{R_b \cdot V_{DD}}{R_a + R_b} - R_S i_D = \frac{V_{DD}}{1 + \frac{R_a}{R_b}} - R_S i_D$

Given V_{GS} & $I_D \Rightarrow$ find $\frac{R_a}{R_b}$ if know R_S & R_S

solve for $\frac{R_a}{R_b} \Rightarrow \left(1 + \frac{R_a}{R_b}\right) (V_{GS} + R_S I_D) = V_{DD}$

$$\frac{R_a}{R_b} = -1 + \frac{V_{DD}}{V_{GS} + R_S I_D}$$

$\therefore \frac{R_a}{R_b}$ will be known (can choose one of R_a or R_b choose one large to keep small bias power)

This means have to use an R_L from the above equation:



$$(R_L + R_S) I_D = V_{DD} - V_{DS}$$

$$R_L = -R_S + \frac{V_{DD} - V_{DS}}{I_D}$$

This now biases the transistor

dd ← at ground potential for signal

(short for signal open for bias)
large

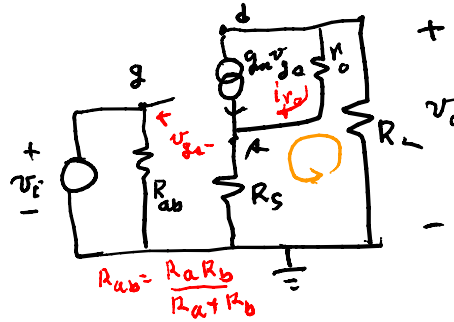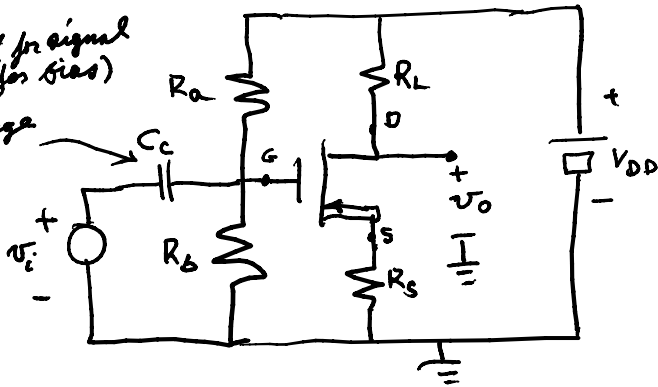

derive $\frac{v_o}{v_i}$:

$$v_{gs} = v_i - R_S (g_m v_{gs} + i_{v_o}) \quad 1)$$

$$v_o = r_o i_{v_o} + R_S (g_m v_{gs} + i_{v_o}) \quad 2)$$

$$v_o = -R_L (g_m v_{gs} + i_{v_o}) \quad 3)$$

from 2):

$$v_o = (r_o + R_S) i_{v_o} + R_S g_m v_{gs} \quad 1)$$

$$i_{v_o} = \frac{v_o - R_S g_m v_{gs}}{r_o + R_S} \quad 2)$$

into 1)

$$v_{gs} = v_i - R_S g_m v_{gs} - \frac{R_S}{r_o + R_S} (v_o - R_S g_m v_{gs})$$

$$(1 + R_S g_m - \frac{R_S^2 g_m}{r_o + R_S}) v_{gs} = v_i - \frac{R_S}{r_o + R_S} v_o$$

If $R_S = 0$ then $i_{v_o} = \frac{v_o}{r_o} \Rightarrow$ from 3) $v_o = -R_L g_m v_{gs} - \frac{R_L}{r_o} v_o$

$$(1 + \frac{R_L}{r_o}) v_o = -R_L g_m v_{gs}$$

$$\frac{v_o}{v_i} \Big|_{v_{gs}} = \frac{v_o}{v_{gs}} = \frac{-R_L g_m}{1 + \frac{R_L}{r_o}} = \frac{v_o}{v_i} \Rightarrow$$

ideal gain is $-R_L g_m$

when $R_S = 0$

--- notes added 09/25/09

for the general case, $G_L = 1/R_L$

$$i_{v_o} \text{ of 3) } = i_{v_o} \text{ of 2): } i_{v_o} = -G_L v_o - g_m v_{gs} = \frac{v_o}{r_o + R_S} - \frac{R_S}{r_o + R_S} g_m v_{gs} = i_{v_o} \quad 1)$$

$$4) \Rightarrow v_{gs} = -\frac{(G_L + \frac{1}{r_o + R_S}) v_o}{g_m (1 - \frac{R_S}{r_o + R_S})} = -\frac{(1 + G_L (r_o + R_S)) v_o}{r_o g_m}$$

$$4) \text{ into } i_{v_o} \text{ of 3) } \Rightarrow i_{v_o} = -G_L v_o + \left(\frac{G_L + \frac{1}{r_o + R_S}}{\frac{r_o}{r_o + R_S}} \right) v_o = \left(-G_L + \frac{G_L (r_o + R_S) + 1}{r_o} \right) v_o = \frac{(1 + G_L R_S) v_o}{r_o}$$

$$5) \therefore i_{v_o} = \frac{(1 + G_L R_S) v_o}{r_o}$$

from 4) & 5) into 1):

$$(1 + g_m R_S) v_{\pi} \stackrel{4)}{=} - (1 + g_m R_S) \frac{(1 + G_L [r_o + R_S]) v_o \stackrel{5)}{=} v_i - R_S i_{v_o} = v_i - \frac{R_S (1 + G_L R_S) v_o}{r_o g_m}}$$

$$\Rightarrow \left\{ \frac{R_S + G_L R_S^2}{r_o} - \frac{[1 + g_m R_S + G_L r_o + G_L R_S + g_m R_S G_L r_o + g_m G_L R_S^2]}{r_o g_m} \right\} v_o = v_i$$

$$\Rightarrow \frac{v_o}{v_i} = \frac{-g_m r_o}{1 + G_L (r_o + R_S + g_m R_S r_o)} = \frac{-g_m R_L}{g_o (R_L + R_S) + (1 + g_m R_S)}$$

$$\text{if } R_S \rightarrow 0 \quad \left. \frac{v_o}{v_i} \right|_{R_S=0} = \frac{-g_m R_L}{1 + g_o R_L}$$

$$\text{if also } g_o \rightarrow 0 \quad \left. \frac{v_o}{v_i} \right|_{R_S=0, g_o=0} = -g_m R_L$$

$$R_S = g_o = 0$$

(theoretical highest achievable voltage gain)