
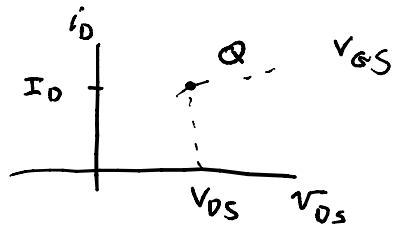


Ex:

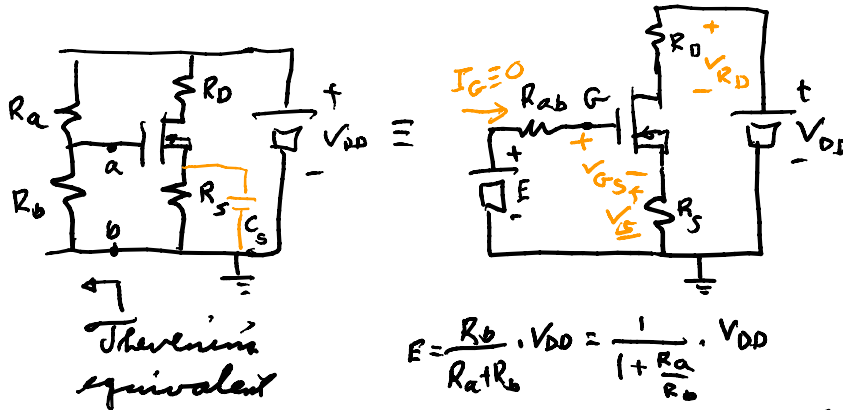

EE303H
09/19/09

$V_{DD} = 10V, V_{DS} = 3V, I_D = 10^{-3}, V_{GS} = 3, V_{T0_n} = 1$



Theremin's equivalent

$$E = \frac{R_b}{R_a + R_b} \cdot V_{DD} = \frac{1}{1 + \frac{R_a}{R_b}} \cdot V_{DD}$$

$r_o \approx \infty$, for gain assume C_S large $\rightarrow R_S \rightarrow 0$ in the gain formula but not bias

$$A_v = \frac{v_o}{v_i} \Big|_{v_o \approx R_D} = -g_m R_D \quad \text{assume } A_v \text{ is given } = -10$$

need g_m : assume transistor is in saturation

$$I_D = \frac{K_P \mu_n}{2} (V_{GS} - V_{T0_n})^2 (1 + \lambda V_{DS})$$

$$g_m = \frac{2I_D}{2V_{GS} Q} = \frac{2I_D}{V_{GS} - V_{T0_n}} = \frac{2 \times 10^{-3}}{3 - 1} = 10^{-3} \text{ V}^{-1}$$

$$R_D = \frac{|A_v|}{g_m} = \frac{10}{10^{-3}} = 10 \text{ k}\Omega \Rightarrow \text{volley on } R_D = 10^4 \times 10^{-3} = 10V$$

\therefore raise (here) V_{DD} , try $20 = V_{DD} \Rightarrow V_{R_S} = V_{DD} - V_{R_D} - V_{DS} = 20 - 10 - 3 = 7V \text{ on } R_S$



$$I_D = 10^{-3}, 7V \text{ on } R_S \Rightarrow V_{R_S} = R_S I_D \Rightarrow R_S = \frac{7}{10^{-3}} = 7 \text{ k}\Omega$$

$$E = \frac{1}{1 + \frac{R_a}{R_b}} \times 20, V_{GS} = 3 \ \& \ V_{R_S} = 7, E = V_{GS} + V_{R_S} = 3 + 7 = 10$$

$$10 = \frac{1}{1 + \frac{R_a}{R_b}} \times 20 \Rightarrow 10 \frac{R_a}{R_b} = 20 - 10 = 10 \Rightarrow \frac{R_a}{R_b} = 1$$

Choose large so small power is used in them
(power in R_a & $R_b = \frac{V_{DD}^2}{(R_a + R_b)}$) choose $R_a = 10 \text{ Meg}\Omega = R_b$

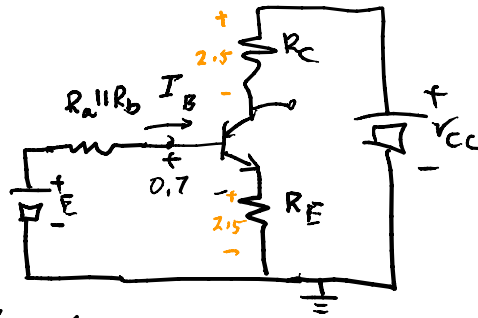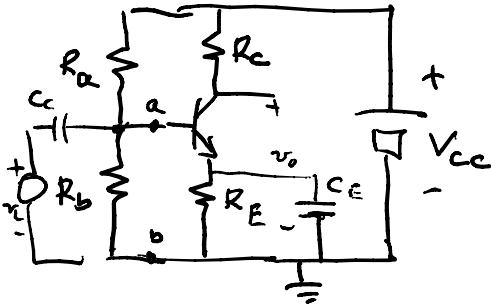For the BJT, almost the same as for MOS but draw base current




$$E = \frac{R_b}{R_a + R_b} V_{CC}$$

$$\frac{v_o}{v_i} = -g_m R_c \quad ; \quad g_m = \frac{I_c}{V_T} \quad \text{choose } I_c = 0.1 \text{ mA}$$

$$= A_v = \frac{10^{-4}}{0.025} = \frac{10^{-4}}{2.5 \times 10^{-3}} = 4 \times 10^{-3} \quad V_c = -100$$

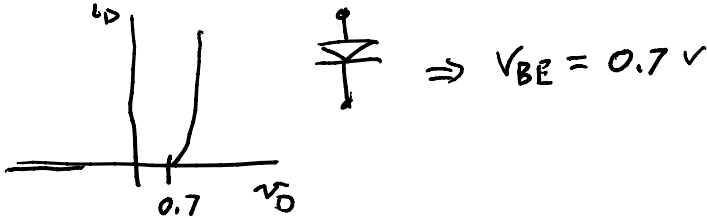for the BJT, the B-E diode is forward biased




$$\text{also } R_c = \frac{-A_v}{g_m} = \frac{100}{4 \times 10^{-3}} = 25 \times 10^3 = 25 \text{ k}\Omega$$

$$V_{R_c} = R_c I_c = 25 \times 10^3 \times 10^{-4} = 2.5 \text{ V}$$

$$R_E = R_c \Rightarrow \text{if } \alpha \approx 1 \text{ then } |I_E| \approx I_c \Rightarrow V_{R_E} = V_{R_c} = 2.5 \text{ V}$$
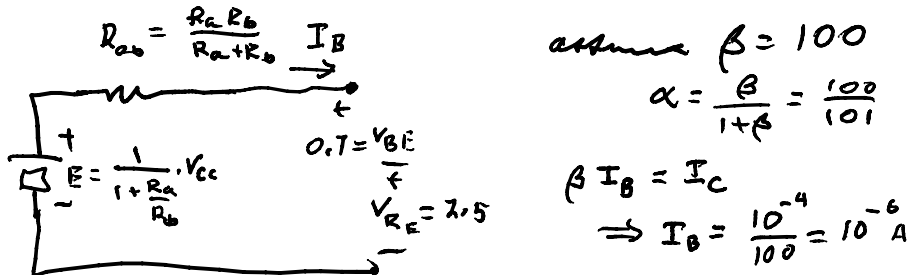
$$V_{CE} = V_{CC} - V_{R_c} - V_{R_E} = V_{CC} - 5 \Rightarrow \text{choose } V_{CC} = 9 \text{ V}$$



$$\text{assume } \beta = 100$$


$$\alpha = \frac{\beta}{1 + \beta} = \frac{100}{101}$$

$$\beta I_B = I_c$$

$$\Rightarrow I_B = \frac{10^{-4}}{100} = 10^{-6} \text{ A}$$

$$E = R_{ab} \times I_B + 0.7 + 2.5 = \frac{R_a R_b}{R_a + R_b} \cdot 10^{-6} + 3.2 \text{ V} = \frac{1}{1 + \frac{R_a}{R_b}} \cdot 9$$
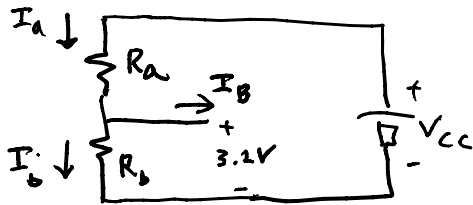
$$= \frac{R_a}{R_a + 1} \cdot 10^{-6} + 3.2$$



$$1) R_b \cdot I_b = 3.2V$$

$$2) R_a I_a = V_{cc} - 3.2 = 5.8V$$

$$3) I_a = I_b + I_B = I_b + 10^{-6}$$

3) \rightarrow 2)

$$3') R_a I_b + R_a 10^{-6} = 5.8 \Rightarrow I_b = \frac{5.8}{R_a} - 10^{-6}$$

$$3') \rightarrow 1) R_b \left(\frac{5.8}{R_a} \right) - R_b 10^{-6} = 3.2$$

from above 4): $\frac{9}{1 + \frac{R_b}{R_a}} = \frac{R_b}{1 + \frac{R_b}{R_a}} \times 10^{-6} + 3.2 \Rightarrow 9 = R_b \times 10^{-6} + 3.2 \left(1 + \frac{R_b}{R_a} \right)$

let $x = \frac{R_b}{R_a}$, $y = R_b$

$$3') 5.8x - 10^{-6}y = 3.2$$

$$4) 3.2x + 10^{-6}y = 9 - 3.2 = 5.8$$

$$\begin{bmatrix} 5.8 & -10^{-6} \\ 3.2 & 10^{-6} \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} 3.2 \\ 5.8 \end{bmatrix}$$

$$9x = 9, x = 1 = \frac{R_b}{R_a}$$



$$10^{-6}y = 5.8 - 3.2 = 2.6$$

$$y = 2.6 \times 10^6 = R_b = 2.6 \text{ Meg}\Omega$$

$$R_a = R_b = 2.6 \text{ Meg}\Omega$$

\therefore can bias with the given values

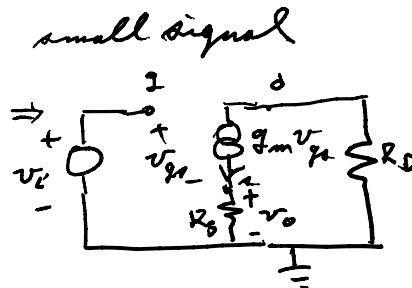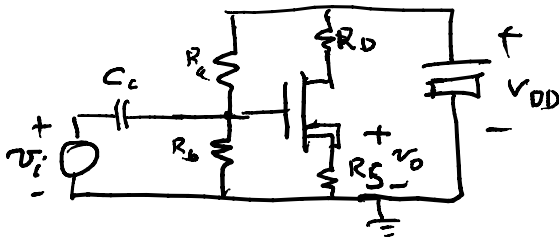For the signal out of the emitter or source



$$v_{be}: 1) v_{be} = v_i - R_s \cdot g_m v_{be} ; v_o = R_s g_m v_{be} \quad 2)$$

solving 1) for v_{be}

$$1) v_{be} = \frac{v_i}{1 + g_m R_s} ; 1) \rightarrow 2) v_o = \frac{g_m R_s}{1 + g_m R_s} \cdot v_i$$

$$\frac{v_o}{v_i} = \frac{1}{1 + \frac{1}{g_m R_s}} < 1$$