

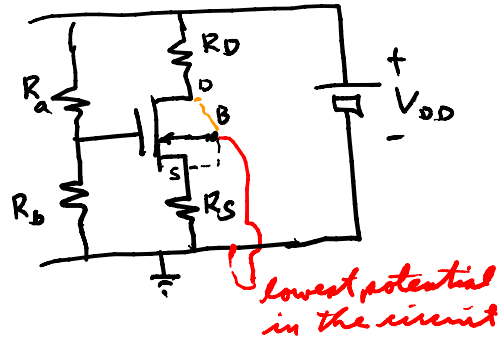
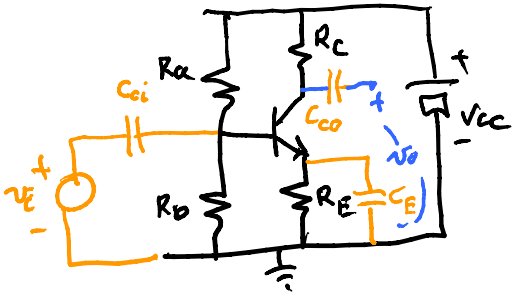


Biasing

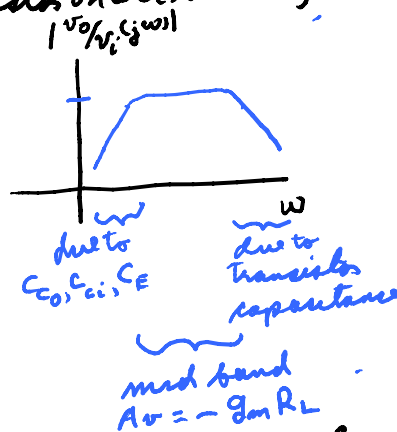


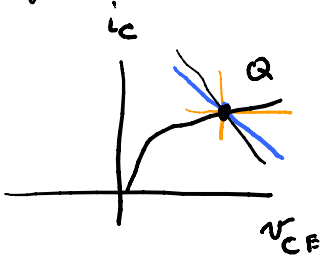use for small signals, class A  
(transistor on all the time)




interesting problem: biasing as an optimization problem with equality and inequality constraints

Biasing problem with MOS

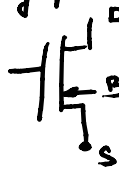


then D = drain if  $V_{Dqnd} \geq V_{Sqnd}$   
S = drain if  $V_{Dqnd} < V_{Sqnd}$

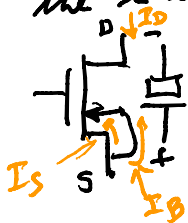if S becomes the drain and if B is tied to S then the bulk to source (BtoD) is forward biased  $\Rightarrow$  bulk current is large (very)



if monitor  $I_S$  &  $I_D \approx I_B$   
 $I_S + I_B \approx -I_D$  (also large)

an OTA

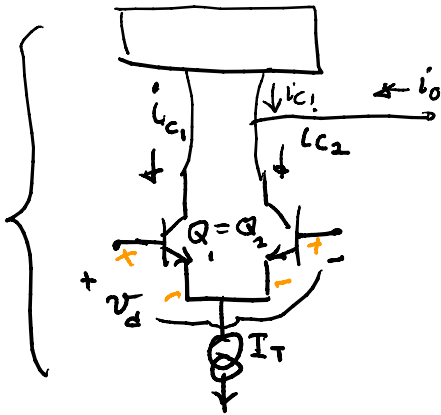

$$out = i_o = i_{c2} - i_{c1}$$

$$i_{c1} + i_{c2} = -\alpha i_{E1} - \alpha i_{E2}$$

$$-i_{E1} - i_{E2} = I_T$$

$$\alpha I_T = i_{c1} + i_{c2}$$

$$i_{c1} = \alpha I_S e^{v_{BE1}/V_T}, \quad i_{c2} = \alpha I_S e^{v_{BE2}/V_T}$$

$$i_{c1} = \alpha I_S e^{(v_{BE1} - v_d)/V_T} = \alpha I_S e^{v_{BE1}/V_T} e^{-v_d/V_T}$$

$$v_d = v_{BE1} - v_{BE2}$$

$$i_o = \alpha I_S \left[ e^{(v_{BE1} - v_d)/V_T} - e^{v_{BE1}/V_T} \right] = \alpha I_S e^{v_{BE1}/V_T} \left[ e^{-v_d/V_T} - 1 \right]$$

$$I_T = \frac{1}{\alpha} \{ i_{c1} + i_{c2} \} = \frac{\alpha I_S}{\alpha} \left\{ e^{v_{BE1}/V_T} + e^{(v_{BE1} - v_d)/V_T} \right\}$$



$$= I_S e^{v_{BE1}/V_T} \left\{ 1 + e^{-v_d/V_T} \right\}$$

gives

$$\frac{i_o}{I_T} = \frac{\alpha I_S e^{v_{BE1}/V_T} \left[ e^{-v_d/V_T} - 1 \right]}{I_S e^{v_{BE1}/V_T} \left[ e^{v_d/V_T} + 1 \right]} \Rightarrow i_o = -\alpha I_T \left[ \frac{1 - e^{-v_d/V_T}}{1 + e^{v_d/V_T}} \right]$$

$$i_o = -\alpha I_T \frac{e^{-v_d/2V_T} \left[ \frac{e^{v_d/2V_T} - e^{-v_d/2V_T}}{2} \right]}{e^{-v_d/2V_T} \left[ \frac{e^{v_d/2V_T} + e^{-v_d/2V_T}}{2} \right]} =$$
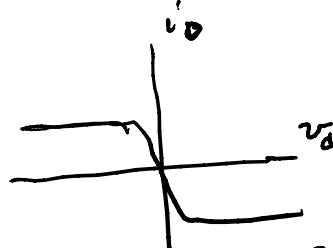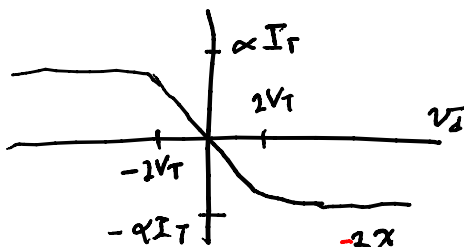
$$= -\alpha I_T \frac{\sinh(v_d/2V_T)}{\cosh(v_d/2V_T)} = -\alpha I_T \tanh(v_d/2V_T)$$



$$\frac{d \tanh x}{dx} = \frac{d}{dx} \left( \frac{1 - e^{-2x}}{1 + e^{2x}} \right) = \frac{+2e^{-2x}}{1 + e^{2x}} - \frac{(1 - e^{-2x})(2e^{2x})}{(1 + e^{2x})^2}$$


$$= 2e^{-2x} \left( \frac{1 + e^{2x}}{(1 + e^{2x})^2} + \frac{1 - e^{-2x}}{(1 + e^{2x})^2} \right) = \frac{2(2e^{-2x})}{(1 + e^{2x})^2} = \frac{4(1 - \tanh^2 x)}{(1 + e^{2x})^2}$$

$$= 1 - \tanh^2 x$$

$$= 1 - \left( \frac{1 - e^{-2x}}{1 + e^{2x}} \right)^2 = \frac{(1 + e^{2x})^2 - (1 - e^{-2x})^2}{(1 + e^{2x})^2}$$


$$= \frac{1 + 2e^{2x} + e^{4x} - 1 + 2e^{-2x} - e^{-4x}}{(1 + e^{2x})^2} = \frac{4e^{2x}}{(1 + e^{2x})^2}$$

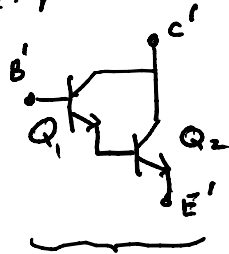This diff. pair needs  $i_B$  for transistors




here  $i_{c'} \approx \beta^2 i_{b'}$  if  $\beta$  is the  $\beta$  of  $Q_1, Q_2$

Darlington pair

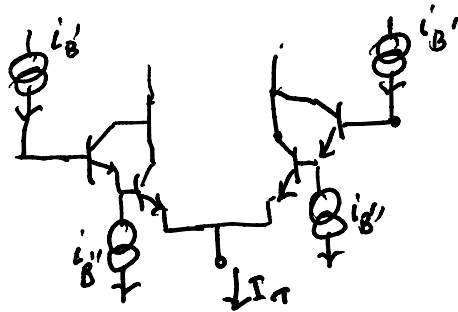

MOS

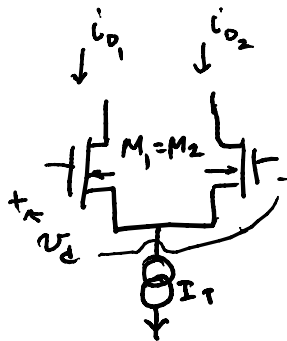

$$v_d = v_{GS1} - v_{S2}$$

$$i_{D2} - i_{D1} = i_o$$

$$I_T = i_{D1} + i_{D2}$$

$$i_{D1} = \frac{K_P W}{2 L} (v_{GS1} - V_{T0n})^2$$

$$i_{D2} = \frac{K_P W}{2 L} (v_{GS1} - v_d - V_{T0n})^2$$

$$\sqrt{i_{D1}} = \sqrt{\frac{K_P W}{2 L}} (v_{GS1} - V_{T0n})$$

$$\sqrt{i_{D2}} = \sqrt{\frac{K_P W}{2 L}} (v_{GS1} - v_d - V_{T0n})$$

$$\sqrt{i_{D2}} - \sqrt{i_{D1}} = \sqrt{\frac{K_P W}{2 L}} v_d$$