

$$i_o = i_2 - i_1$$

$$I_T = i_1 + i_2 \Rightarrow i_2 = I_T - i_1$$

$$i_1 = K_1 (v_{GS1} - V_{TO})^2, \quad i_2 = K_1 (v_{GS2} - V_{TO})^2$$

$$K_1 = \frac{K_P W}{2 L}$$

$$v_{GS1} = V_{TO} \pm \sqrt{i_1/K_1}, \quad v_{GS2} = V_{TO} \pm \sqrt{i_2/K_1} \quad \text{at } v_{GS} > V_{TO} \text{ need + sign}$$

$$v_{id} = v_{GS1} - v_{GS2} = \sqrt{i_1/K_1} - \sqrt{i_2/K_1}$$

$$K_1 v_{id}^2 = i_1 + i_2 - 2\sqrt{i_1 i_2} = I_T - 2\sqrt{i_1 i_2} \Rightarrow \sqrt{i_1 i_2} = \frac{I_T - K_1 v_{id}^2}{2}$$

square $i_1 i_2 = \frac{(I_T - K_1 v_{id}^2)^2}{4} \Rightarrow i_1^2 - I_T i_1 + \frac{1}{4}(I_T - K_1 v_{id}^2)^2 = 0$
 $(i_2 = I_T - i_1)$

$$i_1 (I_T - i_1)$$

solve the quadratic for i_1

$$i_1 = \frac{I_T}{2} \pm \frac{1}{2} \sqrt{(-I_T)^2 - 4 \cdot \frac{1}{4} (I_T - K_1 v_{id}^2)^2}$$

$$= \frac{I_T}{2} \left[1 \pm \sqrt{1 - \frac{(I_T - K_1 v_{id}^2)^2}{I_T^2}} \right]$$

$$1 - 2 \frac{K_1 v_{id}^2}{I_T} + \left(\frac{K_1}{I_T}\right)^2 v_{id}^4$$

$$= \frac{I_T}{2} \left[1 \pm \sqrt{v_{id}^2 \frac{K_1}{I_T} \left(2 - \frac{K_1}{I_T} v_{id}^2\right)} \right]$$

$$= \frac{I_T}{2} \left[1 \pm v_{id} \frac{K_1}{I_T} \sqrt{2 - \frac{K_1}{I_T} v_{id}^2} \right] \quad \text{choose + sign}$$

$$i_2 = I_T - i_1 = \frac{I_T}{2} \left[1 - \sqrt{\frac{K_1}{I_T} v_{id}^2 \left(2 - \frac{K_1}{I_T} v_{id}^2\right)} \right]$$

for an OTA $i_o = i_2 - i_1$

$$i_o = i_2 - i_1 = -I_T \cdot \sqrt{\frac{K_1}{I_T} v_{id}^2 \left(2 - \frac{K_1}{I_T} v_{id}^2\right)}$$

Min
Max of i_o vs v_{id} ; $x = \sqrt{\frac{K_1}{I_T}} v_{id}$

$$\frac{d i_o}{d \left(\sqrt{\frac{K_1}{I_T}} v_{id}\right)} = -I_T \sqrt{2 - x^2} - I_T x \frac{\frac{1}{2}(-2x)}{\sqrt{2 - x^2}} = -I_T \frac{[2 - x^2 - 2x^2]}{\sqrt{2 - x^2}}$$


find x for this = 0:

$$= 0 @ \quad 2 - 2x^2 = 0 \quad x^2 = 1$$



$$x^2 = \frac{k_i}{I_T} v_{id}^2 = 1 \Rightarrow v_{id} = \pm \sqrt{\frac{I_T}{k_i}}$$
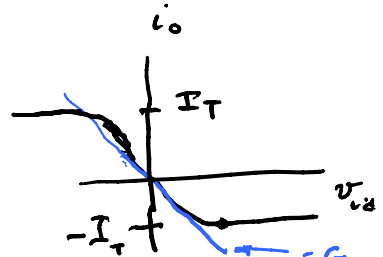
$$i_o = -I_T \sqrt{\frac{k_i}{I_T}} \sqrt{\frac{I_T}{k_i}} \sqrt{2-1} = -I_T$$





$$i_o = \begin{cases} -I_T \sqrt{\frac{k_i}{I_T}} v_{id} \sqrt{2 - \left(\frac{k_i}{I_T} v_{id}^2\right)} & \text{for } -\sqrt{\frac{I_T}{k_i}} \leq v_{id} \leq \sqrt{\frac{I_T}{k_i}} \\ -I_T & \text{for } \sqrt{\frac{I_T}{k_i}} \leq v_{id} \\ +I_T & \text{for } v_{id} \leq -\sqrt{\frac{I_T}{k_i}} \end{cases}$$


$\left. \frac{di_o}{dv_{id}} \right|_{v_{id}=0} = G_m$ of an OTA = voltage to current gain for small signals

$$= -I_T \cdot \sqrt{\frac{k_i}{I_T}} \sqrt{2} = I_T \sqrt{\frac{2k_i}{I_T}} = \sqrt{2k_i I_T}, \quad k_i = \frac{k_p}{2} \frac{W}{L}$$



Inverter behavior: pp. 336-346

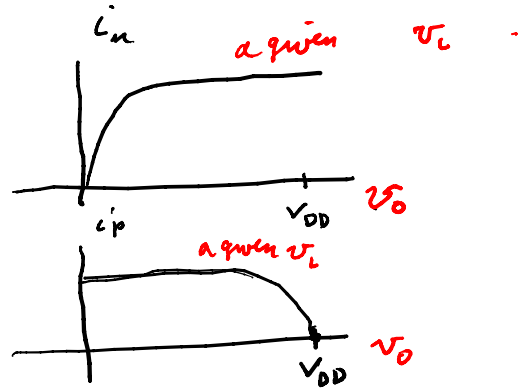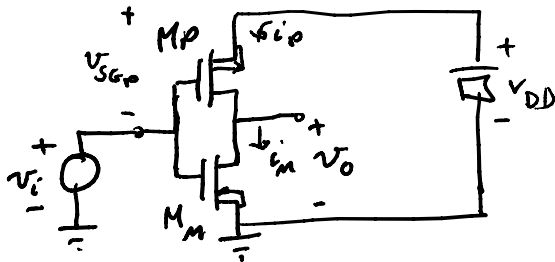


as $i_m = i_p$ the intersection gives v_o

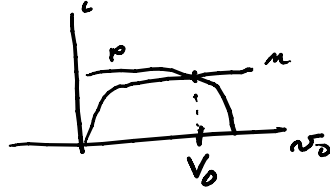



Case 1: $v_i = 0 \Rightarrow$ digital 0
 $\Rightarrow v_o = V_{DD} \Rightarrow$ digital 1

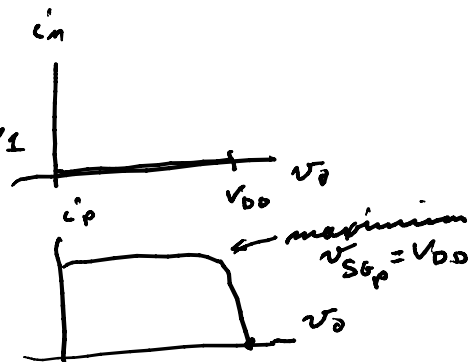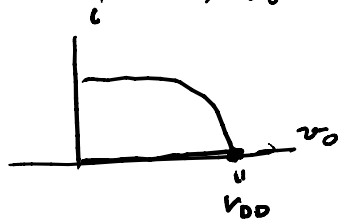

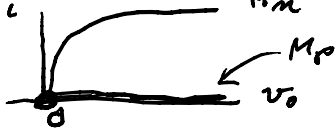Case 2: $v_i = V_{DD} \Rightarrow$ digital 1
 $\Rightarrow v_o = 0 \Rightarrow$ digital 0



Next pulse v_i with the inverters loaded

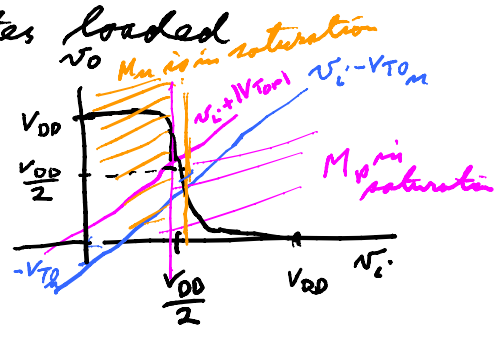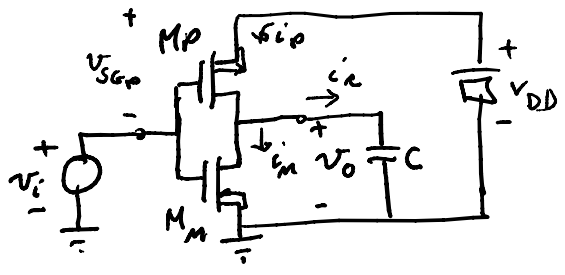


here
 M_n is in saturation when $v_i - V_{Tn} \leq v_0$
 M_p is in saturation when $v_{SGp} - |V_{Tp}| = V_{DD} - v_i - |V_{Tp}| \leq V_{DD} - v_0 = V_{SDp}$
 $v_i + |V_{Tp}| \geq v_0$

Output delay time, Eq. (4.156)

assume $v_0 = \text{digital 1} = V_{DD}$ & $v_i|_{t < 0} = 0$

and change v_i instantaneously to a digital 1, $v_i = V_{DD}$

this turns off M_p

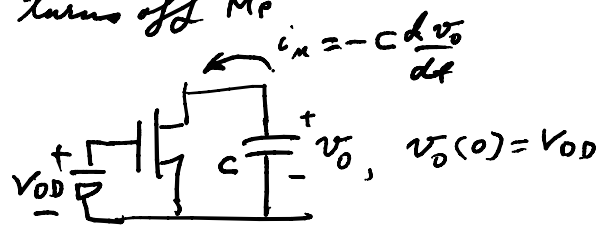

$$\text{at } t=0, i_n = k_n (v_{GS} - V_{Tn})^2 = k_n (V_{DD} - V_{Tn})^2$$

$$C \frac{dv_0}{dt} = -k_n (V_{DD} - V_{Tn})^2 \Rightarrow v_0(t) = -\frac{k_n}{C} (V_{DD} - V_{Tn})^2 \cdot t + v_0(0)$$

$$\text{or } \int_0^t \frac{dv_0(\tau)}{d\tau} d\tau = v_0(t) - v_0(0) \quad \text{valid until } v_0 = v_i - V_{Tn}$$

