

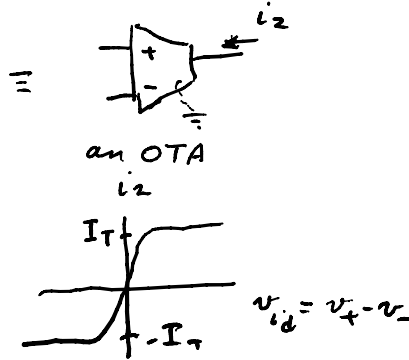


EE303H  
10/08/09

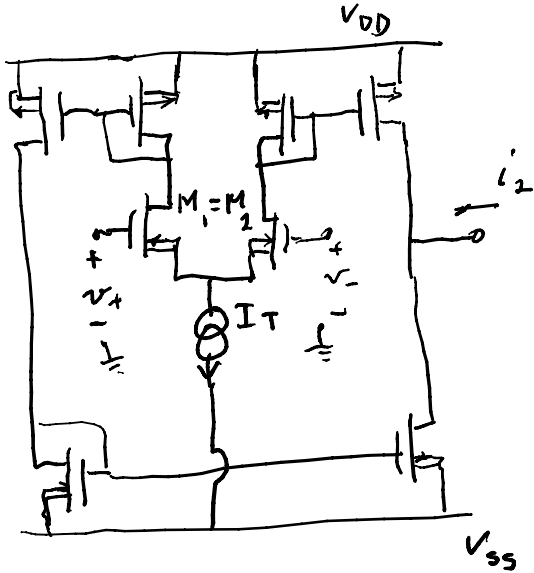

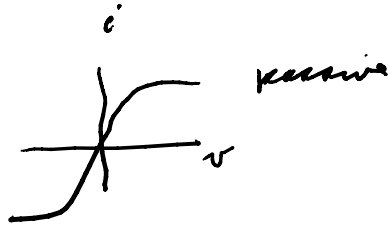
$$G_{m1} = \sqrt{2 \frac{K_P W}{2 L} I_T} = \text{slope at } v_{id} = 0$$




this is like a resistor of value  $R = \frac{1}{G_{m1}}$  at the origin



here  $R = -\frac{1}{G_{m1}}$

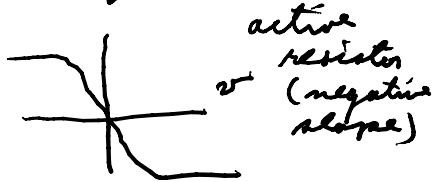

To compare with R from an NMOS

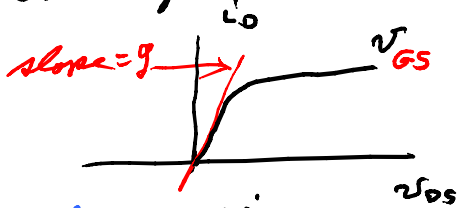

near the origin


$$i_D = \frac{K_P W}{2 L} (2(V_{GS} - V_{TO_n})v_{DS} - v_{DS}^2)$$

for small  $v_{DS}$

$$i_D \sim \left[ \frac{K_P W}{2 L} \cdot 2(V_{GS} - V_{TO_n}) \right] v_{DS}$$

$$g = \frac{i_D}{v_{DS}} = \frac{\partial i_D}{\partial v_{DS}} = \frac{K_P \cdot W}{2 L} \cdot 2(V_{GS} - V_{TO_n})$$

this make a voltage variable resistor

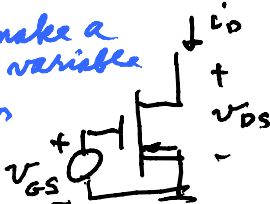

Ex:  $K_P = 9 \times 10^{-5}$ ,  $I_T = 10^{-3}$ ,  $\frac{W}{L} = 4$ ,  $V_{GS} = 5$ ,  $V_{TO_n} = 1$


$$G_m = \sqrt{K_P \frac{W}{L} I_T} = \sqrt{9 \times 10^{-5} \cdot 4 \times 10^{-3}} = 6 \times 10^{-4} \text{ } \Omega^{-1}; R = \frac{10 \times 10^3}{6} = 1.33 \text{ k}\Omega$$

for OTA


$$g_{NMOS} = 9 \times 10^{-5} \times 4(5-1) = 36 \times 4 \times 10^{-5} = 144 \times 10^{-5} = 1.44 \times 10^{-3}$$

$$R = \frac{1}{1.44} \times 10^3 \approx 0.8 \text{ k}\Omega$$

Back to the inverter

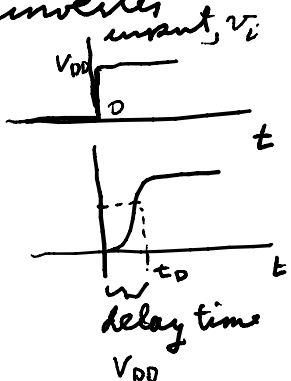


delay time tells how fast can switch

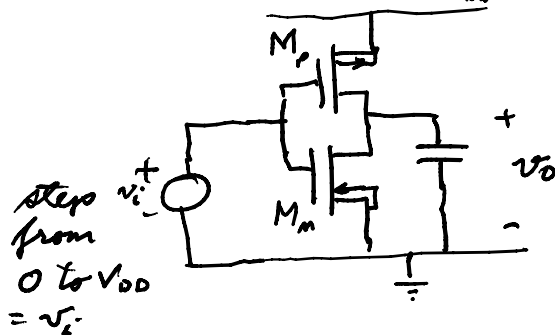

at  $t=0$  assume  $v_o = V_{DD}$

switch at  $t=0$   
at  $t=0$

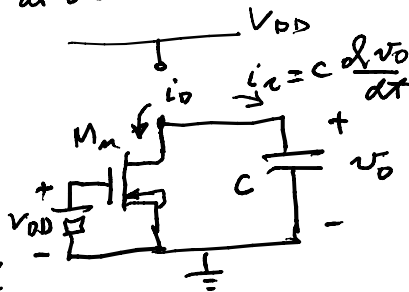

desire to find time to switch

to  $v_o = \frac{V_{DD}}{2}$

@  $t=0$   $V_{GS} - V_{T0n} = V_{DD} - V_{T0n} < V_{DD} = v_{DS} \downarrow$

if  $M_n$  is enhancement

$M_n$  is in the saturation state

$$i_D = \frac{K_P W}{2 L} (V_{GS} - V_{T0n})^2; \text{ let } K = \frac{K_P W}{2 L}$$

$$i_c = C \frac{dv_o}{dt} = -i_D = -K (V_{DD} - V_{T0n})^2$$

Solve:

$$\int_0^t C \frac{dv_o}{dt} dt = C \int_{v_o(0)}^{v_o(t)} dv_o = C v_o(t) - C v_o(0)$$

$$= -K (V_{DD} - V_{T0n})^2 \int_0^t dt = -K (V_{DD} - V_{T0n})^2 t$$

eventually  $v_{DS} = v_0$  becomes  $= v_{GS} - V_{T0n} = V_{DD} - V_{T0n}$

$$C v_0(t) = C V_{DD} - k(V_{DD} - V_{T0n})^2 t$$

define  $t_0$  @ which  $v_0(t_0) = v_{DS}(t_0) = V_{DD} - V_{T0n}$

$$v_0(t_0) = V_{DD} - V_{T0n} = V_{DD} - \frac{k}{C}(V_{DD} - V_{T0n})^2 t_0$$

$$t_0 = \frac{V_{T0n}}{(V_{DD} - V_{T0n})^2} \cdot \frac{C}{k}$$

@ this time we switch to the Ohmic region

$$C \frac{dv_0}{dt} = -i_D = -k(2(V_{GS} - V_{T0n})v_0 - v_0^2) \quad \text{this is a Riccati equation}$$

$$\frac{dv_0}{dt} = -\frac{k}{C}(a v_0 - v_0^2) \quad a = 2(V_{GS} - V_{T0n}) = 2(V_{DD} - V_{T0n})$$

$$dv_0 = -\frac{k}{C}(a v_0 - v_0^2) dt \Rightarrow -\frac{C}{k} \frac{dv_0}{(a v_0 - v_0^2)} = dt$$

$$-\frac{C}{k} \int_{v_0(t_0)}^{v_0(t)} \frac{dv_0}{v_0(a - v_0)} = \int_{t_0}^t d\tau = t - t_0$$

make a partial fraction expansion of  $\frac{1}{x(a-x)}$ ,  $x = v_0$

$$\frac{1}{x(a-x)} = \frac{k_1}{x} + \frac{k_2}{x-a}; \quad k_1 + \frac{k_2 x}{x-a} = \frac{x}{x(a-x)} \Big|_{x=0} = \frac{1}{a-x} \Big|_{x=0}$$

$$= \frac{1/a}{x} + \frac{-1/a}{x-a} \quad = k_1 = 1/a$$

check by cross multiplying

$$\frac{1/a(x-a) + (-1/a)x}{x(x-a)} = \frac{-1}{x(x-a)}$$

$$k_2 = \frac{x-a}{x(a-x)} \Big|_{x=a} - \frac{k_1(x-a)}{x} \Big|_{x=a} = \frac{-1}{a} + 0$$

$$-\frac{C}{k} \left[ \int_{v_0(t_0)}^{v_0(t)} \frac{1/a dv_0}{v_0} + \int_{v_0(t_0)}^{v_0(t)} \frac{-1/a d(v_0-a)}{v_0-a} \right] = -\frac{C}{k} \left[ \frac{1}{a} \ln v_0 \Big|_{v_0(t_0)}^{v_0(t)} - \frac{1}{a} \ln(v_0-a) \Big|_{v_0(t_0)}^{v_0(t)} \right]$$

$$= -\frac{C}{a k} \left[ \ln \left( \frac{v_0}{v_0-a} \right) \Big|_{v_0(t_0)}^{v_0(t)} \right] = t - t_0$$

find  $t$  for which  $v_0(t) = \frac{V_{DD}}{2} \Rightarrow t_D = t_0 + \left( \frac{-C}{a k} \left[ \ln \left( \frac{V_{DD}/2}{V_{DD}-a} \right) - \ln \left( \frac{v_0(t_0)}{v_0(t_0)-a} \right) \right] \right)$

$$\frac{a}{2} = V_{DD} - V_{T0n}, \quad t_0 = t_0 = \frac{V_{T0n}}{(V_{DD} - V_{T0n})^2} \cdot \frac{C}{K}, \quad v_0(t_0) = \frac{a}{2}$$

$$\frac{V_{DD} - a}{2} = \frac{V_{DD}}{2} - 2(V_{DD} - V_{T0n}) = -\frac{3}{2}V_{DD} + 2V_{T0n}$$

$$t_0 = t_0 - \frac{C}{aK} \left[ \ln \left( \frac{V_{DD}/2}{\frac{V_{DD} - a}{2}} \right) / \left( \frac{a/2}{\frac{a}{2} - a} \right) \right] = t_0 - \frac{C}{aK} \ln \left( \frac{V_{DD}/2}{a - \frac{V_{DD}}{2}} \right)$$

$$= \frac{C}{K} \left\{ \frac{V_{T0n}}{(V_{DD} - V_{T0n})^2} + \ln \left( \frac{\frac{3}{2}V_{DD} - 2V_{T0n}}{V_{DD}/2} \right) \right\}$$

the delay to  
move a pulse  
through an  
inverter