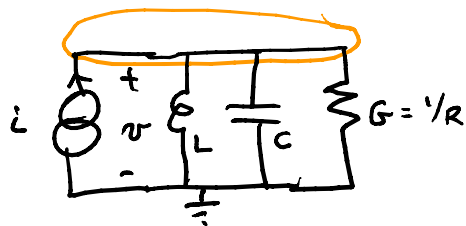


oscillators - v. 1179

EE303H
10/15/09 \Rightarrow 10/23/09
nohction



$$i = \frac{1}{L} v + C \dot{v} + G v$$

$$L \dot{i} = (1 + CL \dot{v}^2 + LG v) v$$

$$= CL \left(\dot{v}^2 + \frac{G}{C} \dot{v} + \frac{1}{LC} v \right) v$$

$$\frac{1}{C} \dot{i} = \left(\dot{v}^2 + \frac{G}{C} \dot{v} + \frac{1}{LC} v \right) v$$

$$v = \frac{\frac{1}{C} \dot{i}}{\dot{v}^2 + \frac{G}{C} \dot{v} + \frac{1}{LC}} \cdot i = T(\dot{v}) \cdot i$$

$-\infty < t < \infty$

let $i(t) = I e^{s_0 t}$

assume $v(t) = V e^{s_0 t}$

$$\frac{s_0}{C} I e^{s_0 t} = \left(s_0^2 + \frac{G}{C} s_0 + \frac{1}{LC} \right) V e^{s_0 t}$$

Case of $I=0 \Rightarrow 0 = \left(s_0^2 + \frac{G}{C} s_0 + \frac{1}{LC} \right) V$ can have $V \neq 0$
if s_0 satisfies

$$P(s_0) = s_0^2 + \frac{G}{C} s_0 + \frac{1}{LC} = 0$$

zeros of $P(s_0)$ are open

circuit ($I=0$) natural frequency.

$$P(s) = s^2 + \frac{\omega_0}{Q} s + \omega_0^2, \quad \omega_0^2 = \frac{1}{LC}, \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

$$\frac{\omega_0}{Q} = \frac{G}{C} \Rightarrow Q = \frac{\omega_0 C}{G} = \frac{1}{G} \sqrt{\frac{C}{L}}$$

Q is a measure of damping

(high Q has little damping)

$$s_0 = -\frac{G}{2C} \pm \frac{1}{2} \sqrt{\left(\frac{G}{C}\right)^2 - \frac{4}{LC}} = -\frac{\omega_0}{2Q} \pm \frac{1}{2} \sqrt{\left(\frac{\omega_0}{Q}\right)^2 - 4\omega_0^2}$$

if $Q = \infty$ then $s_0 = \pm j \omega_0$; $e^{s_0 t} = e^{j \omega_0 t}$ & $e^{-j \omega_0 t}$
 $= \cos \omega_0 t + j \sin \omega_0 t$

if $Q \neq \infty$ have damping meaning

when $Q = \infty$ then the circuit oscillates giving responses

that are cosines & sines

any practical circuit has R present so its

"oscillations" will die.


ideal oscillator has $P(s) = s^2 + \omega_0^2$

$$s i = (s^2 + \omega_0^2) v = \frac{d^2 v}{dt^2} + \omega_0^2 v = 0$$


$$i = 0 \Rightarrow v \neq 0 \Rightarrow (s^2 + \omega_0^2) v = 0$$

$$\begin{cases} \dot{v} = v_1 \\ \dot{v}_1 = \ddot{v} = -\omega_0^2 v \end{cases} \quad \begin{cases} \dot{v} = v_1 \\ \dot{v}_1 = -\omega_0^2 v \end{cases}$$

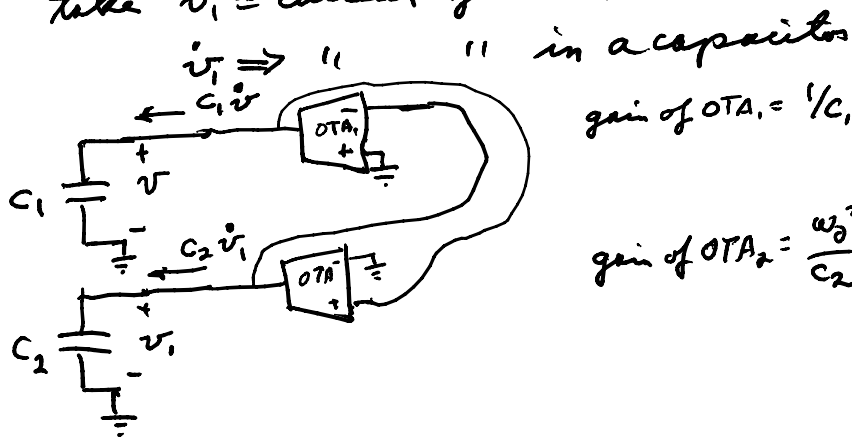
take $v_1 =$ current from $v_1 \Rightarrow$ OTA



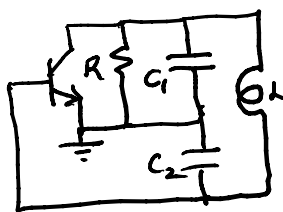Let's look at the Colpitts oscillator, p. 1180




(bias not shown here but on p. 1182)

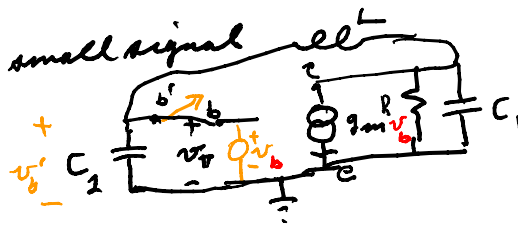

redraw to get the return ratio v_b'/v_b

drive = 1 for an oscillator

Find $v_b' \approx T(s) v_b$

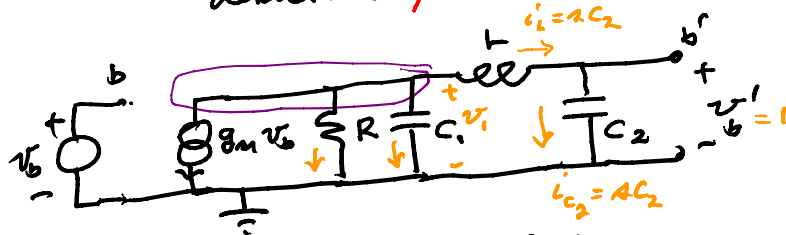

if $v_b' = 1$ then find v_b & force $v_b = 1$ to oscillate

$$v_1 = 1 + LC_2 \omega^2 = LC_2 \omega^2 + 1$$

$$i_{C_1} = \alpha C_1 v_1 = \alpha C_1 (LC_2 \omega^2 + 1)$$

$$i_R = G v_1 = G (LC_2 \omega^2 + 1)$$

by KCL: $g_m v_b + G LC_2 \omega^2 + G + \alpha^3 C_1 LC_2 + \alpha C_1 = -\alpha C_2$
here $v_b' = 1$; $v_b = \frac{(-\alpha C_2 - G LC_2 \omega^2 - G - \alpha^3 C_1 LC_2 - \alpha C_1)}{g_m} \cdot 1$

$$\therefore T(s) = \frac{v_b' = 1}{v_b} = \frac{-g_m}{s^3 L C_1 C_2 + s^2 (G L C_2) + s(C_2 + C_1) + G}$$

$$\text{desire } v_b = 1 \Rightarrow s^3 L C_1 C_2 + s^2 (G L C_2) + s(C_2 + C_1) + G + g_m = 0$$

we desire two known imaginary roots: $s = j\omega_0$
 set $s = j\omega_0$ & force coefficients to give this

$$-j\omega_0^3 L C_1 C_2 - \omega_0^2 G L C_2 + j\omega_0(C_1 + C_2) + G + g_m = 0$$

requires real & imaginary parts both = 0

$$j\omega_0 \{ C_1 + C_2 - \omega_0^2 L C_1 C_2 \} = 0 \quad -\omega_0^2 G L C_2 + G + g_m = 0$$

$$\Rightarrow \omega_0 = \sqrt{\frac{C_1 + C_2}{L C_1 C_2}} \Rightarrow -\frac{(C_1 + C_2) G L C_2 + G + g_m}{L C_1 C_2} = 0$$

$\underbrace{C_1 + C_2}_{\text{a series } C = \frac{C_1 C_2}{C_1 + C_2}}$
 in parallel
 with inductor
 L

$$-\frac{(C_1 + C_2) G}{C_1} = -G - g_m$$

$$g_m = G \left(1 + \frac{C_2}{C_1} \right)$$

$$= G \left(1 + \frac{C_2}{C_1} \right) = \frac{C_2}{C_1} G$$

10/23/09

allows factorization of the

$$P(s) = (s^2 + \omega_0^2)(s + \sigma_0)$$

$$= s^3 + \frac{G}{C_1} s^2 + \frac{(C_2 + C_1)}{L C_1 C_2} s + \frac{G + g_m}{L C_1 C_2}$$

$$\Rightarrow \sigma_0 = \frac{G}{C_1}$$

have created a Colpitts oscillator

