

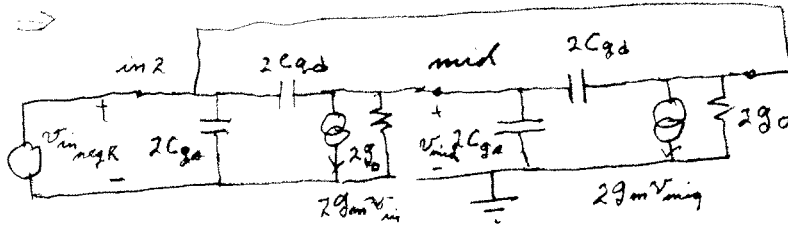

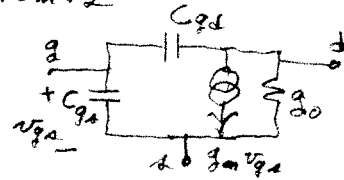
#2.


$$Y_{mos} = \begin{bmatrix} s(2C_{gs} + C_{gd}) & -sC_{gd} \\ -sC_{gd} + g_m & sC_{gd} + g_o \end{bmatrix} \Rightarrow$$



a)

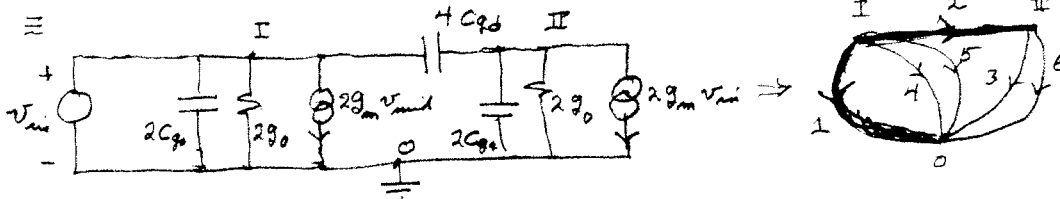

here

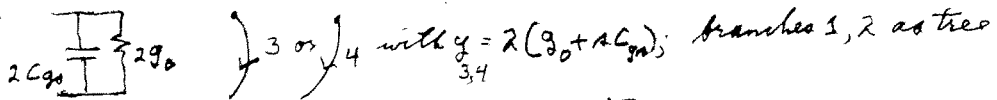

cut set:  $Q_c = eL_b \Rightarrow \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 1 & 1 \\ 0 & 1 & -1 & 0 & -1 \end{bmatrix} \begin{bmatrix} l_1 \\ l_2 \\ l_3 \\ l_4 \\ l_5 \\ l_6 \end{bmatrix}$

tree set:  $Q_t = Jv_b \Rightarrow \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ -1 & 0 & 0 & 1 & 0 & 0 \\ -1 & 0 & 0 & 0 & 1 & 0 \\ -1 & 1 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix}$

as a check the non-identity parts of C & J are -transposes.

b) Remove  $v_{in}$  & consider nodes I & II fed by current sources  $i_I, i_{II}$   
 $\begin{bmatrix} i_I \\ i_{II} \end{bmatrix} = Y_{model} \begin{bmatrix} v_I \\ v_{II} \end{bmatrix}$   $v_I$  &  $v_{II}$  = node voltages referenced to ground,  $v_I = v_1, v_{II} = v_5$

$$Y_{model} = \begin{bmatrix} y_2 + y_4 & -y_2 + 2g_m \\ -y_2 + 2g_m & y_2 + y_3 \end{bmatrix} = \begin{bmatrix} s(4C_{gd} + 2C_{gs}) + 2g_o & 2g_m - 4C_{gd}s \\ 2g_m - 4C_{gd}s & s(4C_{gd} + 2C_{gs}) + 2g_o \end{bmatrix}$$

Eliminate  $v_{II}$  by setting  $i_{II} = 0 \Rightarrow v_{II} = -(2g_m - 4C_{gd}s)v_I / [2g_o + s(4C_{gd} + 2C_{gs})]$

$$y_{in} = y_{11} - y_{12}y_{22}^{-1}y_{21} = 2g_o + s(4C_{gd} + 2C_{gs}) - (2g_m - 4C_{gd}s)^2 / [2g_o + s(4C_{gd} + 2C_{gs})]$$

$$= \frac{\{ [2(g_o + s(2C_{gd} + C_{gs}))]^2 - (2(g_m - 2C_{gd}s))^2 \}}{[2(g_o + s(2C_{gd} + C_{gs}))]}$$

2nd order in s even though 3 C's due to  $\Delta$  of C's

@  $s=0$   
 $y_{in} \Big|_{s=0} = \frac{(4g_o^2) - 4(g_m)^2}{2g_o} = 2g_o - 2\frac{g_m^2}{g_o}$

as usually  $g_m > g_o$ ,  $y_{in}(0) \approx -2\frac{g_m^2}{g_o} < 0$

giving a negative resistance at low frequencies