

Homework 3, #1

1. $Z_{cc}(s) = sL \begin{bmatrix} 1 & -k \\ -k & k^2 \end{bmatrix}$, $\det Z_{cc}(s) = (sL)^2 (1 \cdot k^2 - (-k)^2) \equiv 0 \Rightarrow \text{no } Y = Z^{-1}$

$Z_{cap}(s) = \frac{1}{sC} \begin{bmatrix} 1 & +1 \\ +1 & 1 \end{bmatrix}$

$Z_{2-port}(s) = Z_{cc}(s) + Z_{cap}(s) = \begin{bmatrix} sL + \frac{1}{sC} & -sLk + \frac{1}{sC} \\ -sLk + \frac{1}{sC} & sLk^2 + \frac{1}{sC} \end{bmatrix}$



$\det Z_{2-port} = (sL + \frac{1}{sC})(sLk^2 + \frac{1}{sC}) - (-sLk + \frac{1}{sC})^2$
 $= s^2 L^2 k^2 + \frac{L}{C} + \frac{L}{C} k^2 + \frac{1}{s^2 C^2} - [s^2 L^2 k^2 - 2Lk + \frac{1}{s^2 C^2}]$
 $= \frac{L}{C} [1 + 2k + k^2] = \frac{L}{C} (1+k)^2$

$\therefore Y_{2-port} = Z_{2-port}^{-1} = \frac{1}{\frac{L}{C} (1+k)^2} \begin{bmatrix} sLk^2 + \frac{1}{sC} & sLk - \frac{1}{sC} \\ sLk - \frac{1}{sC} & sL + \frac{1}{sC} \end{bmatrix}$

$= \frac{sC}{(1+k)^2} \begin{bmatrix} k^2 & k \\ k & 1 \end{bmatrix} + \frac{1}{sL(1+k)^2} \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$

$= Y_{cap}(s) + Y_{ind}(s)$

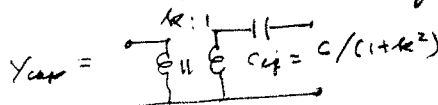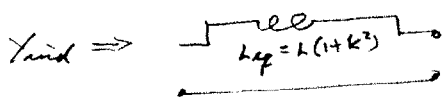indicating the parallel connection of two 2-ports



here the capacitor is a mutually coupled one, coupled through an ideal transformer

b)



cutsets: $O_3 = \begin{bmatrix} 1 & 0 & 0 & 1 & 1 \\ 0 & 1 & 0 & -1 & -1 \\ 0 & 0 & 1 & 0 & 1 \end{bmatrix} i_b$

the sets: $O_2 = \begin{bmatrix} -1 & 1 & 0 & 1 & 0 \\ -1 & 1 & -1 & 0 & 1 \end{bmatrix} v_b$

$v_b = v = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 1 & -1 & 0 & 1 \end{bmatrix} v_b$, $i_b = i + j = \begin{bmatrix} -1 & -1 \\ 1 & 1 \\ 0 & 0 \\ 0 & 1 \end{bmatrix} i_x$

$i_b = [i_1, i_2, i_3, i_4, i_5]^T + [-I_{in}, 0, 0, 0, 0]^T = i + j$, $i_x = [i_1, i_5]^T$
 $v_b = [v_1, v_2, v_3, v_4, v_5]^T = v$, $v_x = [v_1, v_2, v_3]^T$
 $A v = B i \Rightarrow \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \end{bmatrix} v = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 \end{bmatrix} i$
 $\Rightarrow i_4 = 0$
 $\Rightarrow v_4 = 0$

as $i_4 = 0$ then $i_1 = -I_{in} = -i_2 = -i_5$
 $\Rightarrow i_5 = I_{in} = -i_3 = i_2$



$\begin{bmatrix} i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} Y_{2-port} \end{bmatrix} \begin{bmatrix} v_2 \\ v_3 \end{bmatrix}$ (from $A v = B i$)

$\Rightarrow \begin{bmatrix} v_2 \\ v_3 \end{bmatrix} = Z_{2-port} \begin{bmatrix} I_{in} \\ -I_{in} \end{bmatrix}$

$\Rightarrow v_5 = v_3 = Z_{21} I_{in} - Z_{22} I_{in} = [-sLk + \frac{1}{sC} \quad -(sLk^2 + \frac{1}{sC})] I_{in}$

$\frac{v_0}{v_0} = -sL(k+k^2) I_{in}$ (mutual + output) inductance

Homework 3, #2

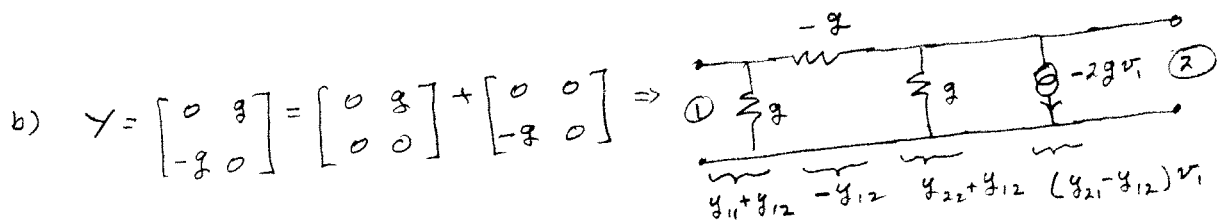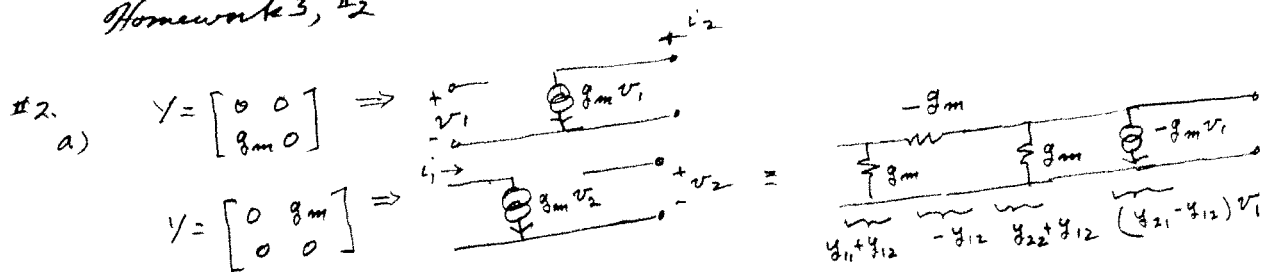

c) $\frac{i}{v} = \frac{G}{v} \Rightarrow \text{power} = v \cdot i = v \cdot Gv = Gv^2$

power $g v_1^2 - g(v_1 - v_2)^2 + g v_2^2 - (2g v_1) \cdot v_2$
 $\Sigma = g v_1^2 - g(v_1^2 - 2v_1 v_2 + v_2^2) + g v_2^2 - 2g v_1 v_2 = 0$
 = 0 = sum of power in each component (some are < 0)

$V_{port}^T I_{port} = V^T \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} V$
 $= [v_1 \ v_2] \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = [-g v_2, g v_1] \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = -g v_2 v_1 + g v_1 v_2 = 0$

i. the power into the ports = sum of powers in components
 $= 0 \Rightarrow$ instantaneously lossless