

## EE 610 Final Exam Fall 2009

Take Home. Open Book Open Notes 200 points total

Due in Room AVW 1364 at the final period Tu 12/15/09 [08-10am]

along with your notebook. Your signature certifies that the work is your own.

1. (6 points/synthesis=30 points) [lossless synthesis]

Synthesize  $y(s) = \frac{s(s^2+6)}{s^2+3}$  by 5 methods (1<sup>st</sup> & 2<sup>nd</sup> Foster & Cauer & via Richards' function sections with  $k=1$ )

2. (10 points/part=40 points) [even part zeros]

Assume that  $k_1$  &  $k_2 \neq \pm k_1$  are two zeros of the even part of a rational  $y(s)$ . Note that if a Richards' section is extracted at  $k_1$  then also  $-k_1$  is also eliminated from the load admittance  $y_L(s)$ .


- a) Since  $-k_1$  is also a zero of the even part, a Richards' function extraction can occur by choosing  $k = -k_1$  in the Richards' function extraction. Draw the (gyrator, capacitor) Richards' section that results.
- b) Determine, in terms of the degree  $\delta[y(s)]$ , what is the minimum number of zeros of the even part of a rational  $y(s)$  that can be removed in a synthesis of a rational  $y(s)$ . In what cases is there no maximum of the number of zeros of this even part?
- c) Show that Richards' functions can be used for synthesis of  $y(s)$  which are not positive-real by synthesizing  $y(s)=s(s^2+3)$  via three Richards' sections all using  $k=+1$ .

3. (30 points) [RL circuits]

The necessary and sufficient conditions that a positive-real rational  $y(s)$  by synthesizable by an LC circuit (with all L's & C's positive) is that  $y(s)=-y(-s)$ . Give (and prove) similar necessary and sufficient conditions that a positive-real rational  $y(s)$  be synthesizable by an LR circuit (with all L's & R's positive).

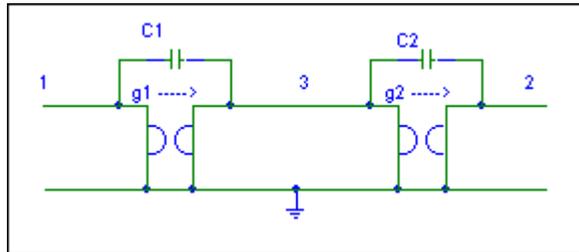4. (50 points) [nodal admittance]

The following represents the extraction of two Richards' sections at positive  $k$ 's for a PR  $y(s)$ . Find the nodal admittance matrix and eliminate node three to obtain the 2-port  $Y(s)$  matrix. By considering  $Y(s)$  as a sum of matrices discuss why it can be synthesized by a passive circuit using only one gyrator, one capacitor, one inductor and one resistor with possible transformer combinations..



5. (50 points) [semistate equations]

For the following circuit

- choose branches 1, 2, 3 for the tree and give the cut set and tie set matrices.
- set up the semistate equations with  $u=[V1 \ V2]^T$  as input voltages,  $y=[-I1 \ -I2]^T$  as output currents [going up through the voltage sources], and tree voltages & link currents for the semistate  $x$ .

