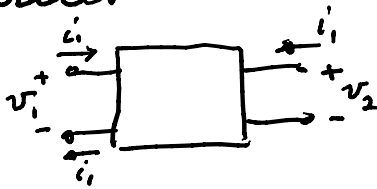


grades: Gagandeep Singh  
 email: g13gagan@gmail.com

EE610  
 09/03/09b


Admittance matrices

2-port



$$V(s) = \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix}$$

$$Y(s)V(s) = I(s)$$

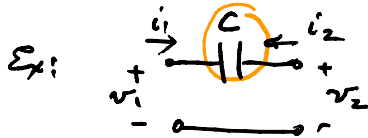

$$y_{cap} = sC = Cs$$

$$i_1(s) = C \frac{d(v_1 - v_2)}{dt}$$

$$I(s) = \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix}$$

KCh:  $i_1 + i_2 = 0$

$$I_1(s) = -I_2(s), \quad I_1(s) = Cs V_1(s) - Cs V_2(s)$$

$$= [Cs \quad -Cs] \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix}$$

$$I_2(s) = -I_1(s)$$

$$= [-Cs \quad Cs] \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Cs & -Cs \\ -Cs & Cs \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow Y(s) = \begin{bmatrix} Cs & -Cs \\ -Cs & Cs \end{bmatrix} = Cs \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$$


$\det Y(s) = C^2 s^2 - (-Cs)^2 = 0$ ,  $\therefore$  no  $Y^{-1}$  exists  
 but  $Y(s) = Y^T(s) = \text{transpose}$ ;  $Y(s)$  is symmetric

$\therefore V(s) = Z(s)I(s)$  has no 2-port  $Z(s)$

Ex: gyrator:  $Y(s) = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix}$ ; here  $Y^T = -Y \Rightarrow Y + Y^T = 0_{2 \times 2}$

$$= \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix} = \begin{bmatrix} -0 & -g \\ -(g) & -0 \end{bmatrix}$$

$\therefore Y(s)$  is skew-symmetric

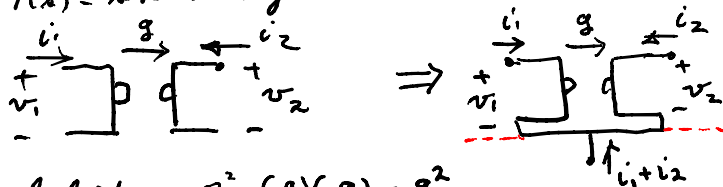

Here  $\det Y(s) = 0^2 - (g)(-g) = g^2$



$\therefore Y$  is not singular if  $g \neq 0$

$$\therefore Y^{-1} \text{ exists (if } g \neq 0) \Rightarrow Y^{-1} = Z_{gm} = \frac{1}{g^2} \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix} = \begin{bmatrix} 0 & -r \\ r & 0 \end{bmatrix}$$

$r = \text{gyration resistance}$

also  $Z_{gms} = -Z_{gm}^T$

Ex:

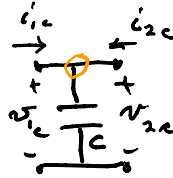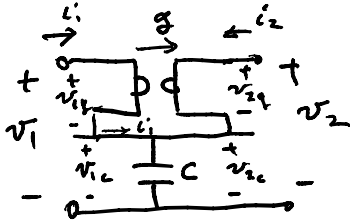

$$I_c = I_{1c} + I_{2c} = AC V_{1,2}$$

$$V = ZI = \begin{bmatrix} \frac{1}{ac} & \frac{1}{ac} \\ \frac{1}{ac} & \frac{1}{ac} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}_c$$

$$i_{1c} = i_1 = i_{1g}, \quad v_1 = v_{1g} + v_{1c}$$

$$i_{2c} = i_2 = i_{2g}, \quad v_2 = v_{2g} + v_{2c}$$


$$Z_c = \frac{1}{ac} \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}, \quad \det Z_c = 0$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_{1g} \\ V_{2g} \end{bmatrix} + \begin{bmatrix} V_{1c} \\ V_{2c} \end{bmatrix} = Z_{gm} \begin{bmatrix} I_{1g} \\ I_{2g} \end{bmatrix} + Z_c \begin{bmatrix} I_{1c} \\ I_{2c} \end{bmatrix} = (Z_{gm} + Z_c) \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Z = Z_{gm} + Z_c = \begin{bmatrix} 0 & r \\ -r & 0 \end{bmatrix} + \begin{bmatrix} \frac{1}{ac} & \frac{1}{ac} \\ \frac{1}{ac} & \frac{1}{ac} \end{bmatrix} = \begin{bmatrix} \frac{1}{ac} & r + \frac{1}{ac} \\ -r + \frac{1}{ac} & \frac{1}{ac} \end{bmatrix}$$

given any square matrix A
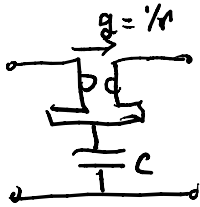
$$A = \frac{A + A^T}{2} + \frac{A - A^T}{2} = A_{\text{symmetric}} + A_{\text{skew}}$$



$$\Rightarrow Z = \begin{bmatrix} \frac{1}{ac} & r + \frac{1}{ac} \\ -r + \frac{1}{ac} & \frac{1}{ac} \end{bmatrix}; \quad \det Z = \left(\frac{1}{ac}\right)^2 - \left(r + \frac{1}{ac}\right)\left(-r + \frac{1}{ac}\right)$$


$$= \left(\frac{1}{ac}\right)^2 + r^2 - \frac{1}{ac^2} = r^2$$

$$Y = \frac{1}{r^2} \begin{bmatrix} \frac{1}{ac} & (r + \frac{1}{ac})(-1)^3 \\ (-r + \frac{1}{ac})(-1)^{2+1} & \frac{1}{ac} \end{bmatrix}$$


$$= g^2 \begin{bmatrix} \frac{1}{ac} & -r - \frac{1}{ac} \\ r - \frac{1}{ac} & \frac{1}{ac} \end{bmatrix}$$

$$= \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix} + \begin{bmatrix} \frac{1}{ar^2c} & -\frac{1}{ar^2c} \\ -\frac{1}{ar^2c} & \frac{1}{ar^2c} \end{bmatrix}$$

$$= Y_{gm} + Y_{ind}$$

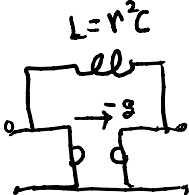

Let's load with a short

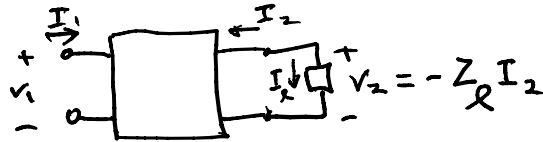

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = Z \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$= \begin{bmatrix} v_1 \\ -Z_L I_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$-Z_L I_2 = z_{21} I_1 + z_{22} I_2 \Rightarrow -(Z_L + z_{22}) I_2 = z_{21} I_1$$


$$I_2 = -(Z_L + z_{22})^{-1} z_{21} I_1 \quad \text{into 1st row}$$

$$v_1 = z_{11} I_1 + z_{12} I_2 = [z_{11} - z_{12} (Z_L + z_{22})^{-1} z_{21}] I_1$$

$$= Z_{in} \cdot I_1$$


here  $Z_{in} = \frac{z_{11} Z_L + z_{11} z_{22} - z_{12} z_{21}}{Z_L + z_{22}} = \frac{z_{11} Z_L + \det Z}{Z_L + z_{22}}$

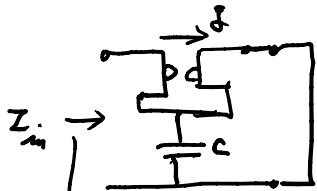for a short  $v=0$ ,  $i = \text{anything} \Rightarrow Z_L = 0$  if  $i$  is finite  
for our circuit,  $\det Z = \nu^2$





$$Z_{in} = \frac{\nu^2}{\frac{1}{sC}} = s \nu^2 C = s L_{eq}$$

corrected denominator

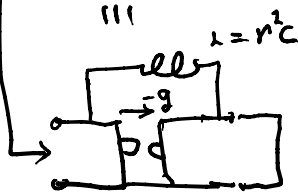
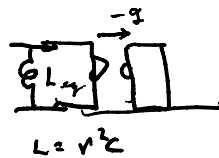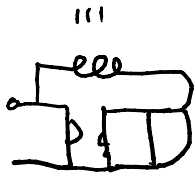
$$\equiv \left[ \right] \lambda = L_{eq} = \frac{C}{g^2}$$



$$\equiv \left[ \right] \lambda = \frac{C}{g^2}$$