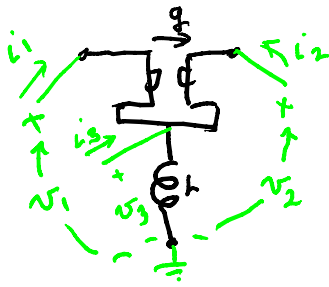


obtain a paper by next period

EE610  
09/08/09



⇒ nodal admittance

$$\underline{i}_{\text{node}} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}, \quad \underline{v}_{\text{node}} = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}, \quad \underline{i}_{\text{node}} = \underline{Y}_{\text{node}} \underline{v}_{\text{node}}$$

$$i_1 = g(v_1 - v_3)$$


$$i_2 = -g(v_1 - v_3)$$

$$i_3 = -(i_1 + i_2) + i_3 = -g(v_1 - v_3) - (-g)(v_1 - v_3) + \frac{1}{4L} v_3$$

↑  
KCL

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}_{\text{node}} = \begin{bmatrix} 0 & g & -g \\ -g & 0 & g \\ g & -g & \frac{1}{4L} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}_{\text{node}}; \quad \underline{Y}_{\text{node}} = \begin{bmatrix} 0 & g & -g \\ -g & 0 & g \\ g & -g & 1/4L \end{bmatrix}$$

For terminal (2-port) Y

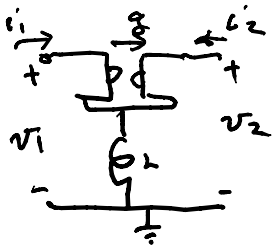

⇒ "eliminate" node 3

$$i_3_{\text{node}} = 0$$

$$\begin{bmatrix} i_1 \\ i_2 \\ 0 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$$0 = y_{21} v_1 + y_{22} v_3 = [g \quad -g] \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + [\frac{1}{4L}] v_3$$


$$v_3 = -y_{22}^{-1} y_{21} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = -4L [g \quad -g] \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ -g & -g \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} -g & g \\ \frac{1}{4L} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$


$$= \left\{ \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} + \begin{bmatrix} -g & g \\ g & -g \end{bmatrix} \right\} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} y_{11} - 4L g^2 & y_{12} - 4L g^2 \\ g & -g \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$Y_{\text{terminal}} = Y_{11} - Y_{12} Y_{22}^{-1} Y_{21}$$
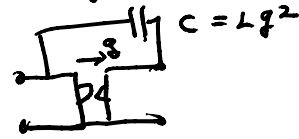
$$= \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} + \begin{bmatrix} 2Lg^2 & -2Lg^2 \\ -2Lg^2 & 2Lg^2 \end{bmatrix} = \begin{bmatrix} 2Lg^2 & g - 2Lg^2 \\ -g - 2Lg^2 & 2Lg^2 \end{bmatrix}$$



Indefinite  $Y = Y_{\text{ind}}$

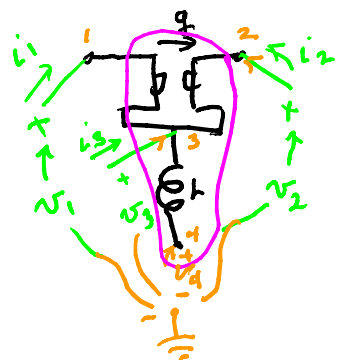

ground is outside the circuit  
now get a 4x4  $Y_{\text{ind}}$

$$i = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}, v = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} \text{ all w.r.t ground}$$

$$i_1 = g(v_2 - v_3), \quad i_2 = -g(v_1 - v_3), \quad i_3 = -(i_1 + i_2) + \frac{1}{2L}(v_3 - v_4)$$

$$i_4 = -i_3 \text{ of above} = +\frac{1}{2L}(v_4 - v_3)$$

$$i_1 \rightarrow Y_{\text{ind}} = \begin{bmatrix} 0 & g & -g & 0 \\ -g & 0 & g & 0 \\ g & -g & \frac{1}{2L} & -\frac{1}{2L} \\ 0 & 0 & -\frac{1}{2L} & \frac{1}{2L} \end{bmatrix}$$

node admittance of ground node 4  
here all entries in a row sum to zero  
" " " " a column sum to zero

this is singular. can make "definite" = a nodal admittance by putting a ground on the circuit i.e. force one voltage to zero

$$\text{if } v_4 = 0 \Rightarrow \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ 0 \end{bmatrix}$$

eliminate the current to the ground node (i.e. ignore)  
last column is multiplied by 0 so ignore

$\therefore Y_{\text{nodal}} = Y_{11}^{\text{ind}}$  if scratch out last row & column, i.e. ground last node


# Graph theory for finite circuits

set of points = nodes  
 & lines = branches

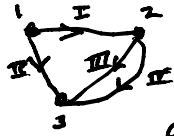
# of nodes =  $n$   
 # of branches =  $b$

oriented  
 put arrows  
 on branches

⇒ positive  
 direction of current  
 in a branch







$b=4$   
 $n=3$

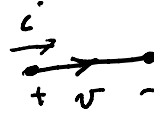



⇒ power in =  $v \cdot i$  for a  
 branch ⇒ arrow fixes  
 polarity for the voltage

Ex:

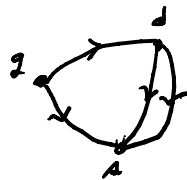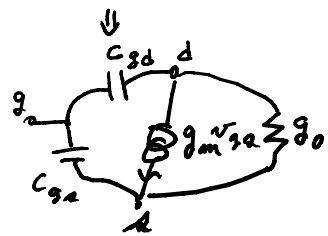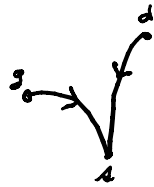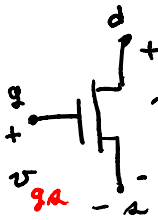

Laws of connection: KCL & KVL

Laws of elements: y's or z's, scattering

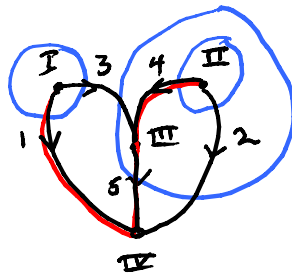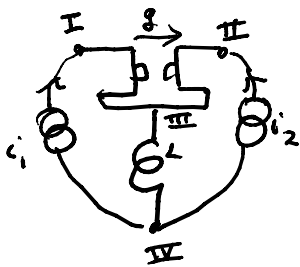

$b=5$   
 $m=4$   
 $t=3 = m-1$   
 $l=2 = b-t$   
 $= b-(m-1)$   
 $= b-m+1$

tree = set of branches connecting all nodes with <sup>out</sup> closed path, # of tree branches =  $t$

cotree = non-tree branches = leaves, # of leaves =  $l$

Cut set equations,  $C$  = cut set matrix, KCL on a sphere cutting only one tree branch

for branch 1:  $0 = i_1 + i_3$   
 4:  $0 = i_2 + i_4$   
 5:  $0 = i_2 - i_3$   $i_5$

