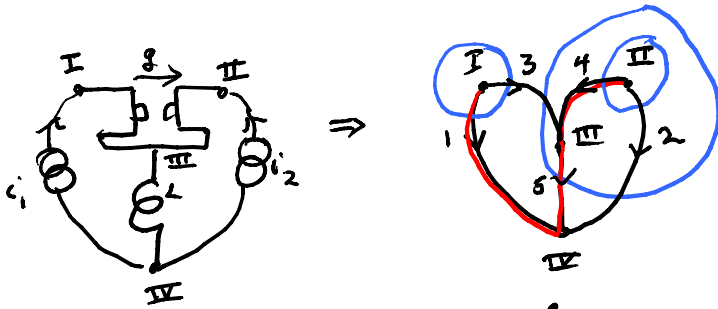


EE610
09/10/09



$b = 5$
 $m = 4$
 $t = 3$

— = tree

KCL $\Rightarrow C = \text{cut-set matrix}$
KVL $\Rightarrow J = \text{tie set matrix}$

KCL from 1) $0 = i_1 + i_3$
 " 4) $0 = +i_2 + i_4$
 " 5) $0 = +i_2 - i_3 + i_5$

KVL 2) $0 = +v_2 - v_4 - v_5$
 3) $0 = -v_1 + v_3 + v_5$

$$\Rightarrow \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}$$

$$C = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 & -1 & -1 \\ -1 & 0 & 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix}$$


$$J = \begin{bmatrix} 0 & 1 & 0 & -1 & -1 \\ -1 & 0 & 1 & 0 & 1 \end{bmatrix}$$

C is $t \times b$, J is $l \times b$

$b = t + l$

By renumbering we can make the last t columns of C to be the identity matrix, 1_t

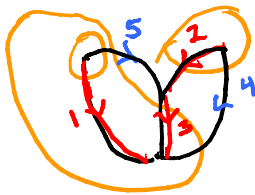then for this tree J has the last l columns to be 1_l



$$C = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 & -1 \end{bmatrix} = \begin{bmatrix} 1_3 & | & 0 & 1 \\ 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 0 & -1 \end{bmatrix} = \begin{bmatrix} 1_t & | & K_c \\ 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 0 & -1 \end{bmatrix}$$

$$J = \begin{bmatrix} 0 & -1 & -1 & 1 & 1 \\ -1 & 0 & 1 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 0 & -1 & -1 & 1 & 1 \\ -1 & 0 & 1 & 0 & 1 \end{bmatrix} = \begin{bmatrix} K_T & | & 1_l \\ -1 & 0 & 1 & 0 & 1 \end{bmatrix}$$

here $K_T = -K_C^T$ if true for all finite circuits then
 $KVL \Leftrightarrow KCL$; it is true

KCL $0_t = [1_t \mid K_c] \begin{bmatrix} i_t \\ i_l \end{bmatrix} = C i_b$ $i_b = \begin{bmatrix} i_t \\ i_l \end{bmatrix}$
 KVL $0_l = [K_T \mid 1_l] \begin{bmatrix} v_t \\ v_l \end{bmatrix} = J v_b$

$-i_t = K_c i_l$

$-v_l = K_T v_t$; $v_b = \begin{bmatrix} v_t \\ v_l \end{bmatrix} = \begin{bmatrix} 1_t \\ -K_T \end{bmatrix} v_t$

$i_b = \begin{bmatrix} i_t \\ i_l \end{bmatrix} = \begin{bmatrix} -K_c \\ 1_l \end{bmatrix} i_l$

for any circuit with graph this holds; choose one with arbitrary v_t
 here i_l can be arbitrary

$$e(Y_{b \times b} E - J) = [e Y_{b \times b} e^T] v_t$$

$$\Rightarrow v_t = [e Y_{b \times b} e^T]^{-1} \{e(Y_{b \times b} E - J)\}$$


$$\& v_b = e^T v_t$$

$$\hat{v}_b = v_b - E \Rightarrow \hat{i}_b = Y_{b \times b} \hat{v}_b$$

$$i_b = \hat{i}_b + J$$

\therefore know all voltages & currents if can invert $[e Y_{b \times b} e^T]$

Ex

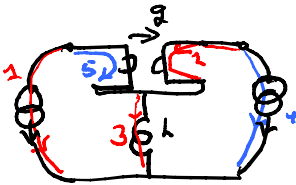

$$Y_{b \times b} = Y_{5 \times 5}$$

$$= \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & g \\ 0 & 0 & \frac{1}{g} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & -g & 0 & 0 & 0 \end{bmatrix}$$

$$J = \begin{bmatrix} J_1 \\ 0 \\ 0 \\ J_4 \\ 0 \end{bmatrix}, E = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$e = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 1 & 0 \\ 0 & 0 & 1 & 1 & -1 \end{bmatrix}$$