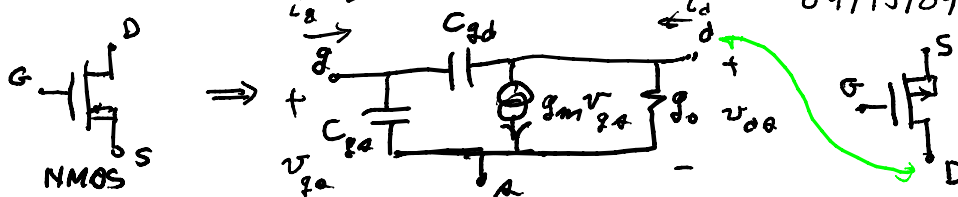


Homework due today now due Tn

EE610
09/15/09



$$\begin{bmatrix} i_g \\ i_d \end{bmatrix} = Y \begin{bmatrix} v_{gs} \\ v_{ds} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_{gs} \\ v_{ds} \end{bmatrix}$$


$$i_g = y_{11} v_{gs} + y_{12} v_{ds} \Rightarrow y_{11} = i_g / v_{gs} \Big|_{v_{ds}=0}$$



$$Y = \begin{bmatrix} sC_{gs} + sC_{gd} & -sC_{gd} \\ g_m - sC_{gd} & g_o + sC_{gd} \end{bmatrix}$$

$$y_{11} = (sC_{gs} + sC_{gd})$$


$$y_{12} = i_g / v_{ds} \Big|_{v_{gs}=0}$$

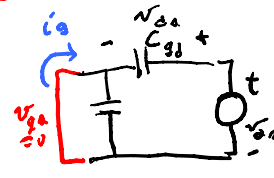

$$i_d = y_{21} v_{gs} + y_{22} v_{ds}$$


$$y_{21} = \frac{i_d}{v_{gs}} \Big|_{v_{ds}=0}$$

$$= g_m - sC_{gd}$$

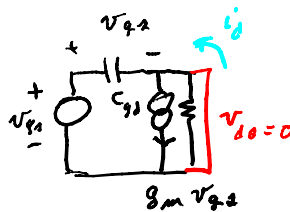


$$= -sC_{gd}$$

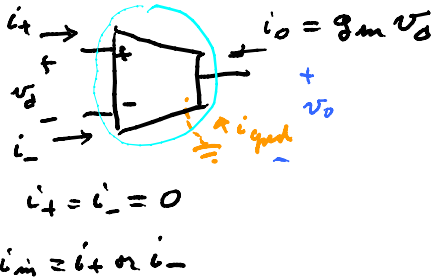OTA = operational transconductance amplifier



$$i_o + i_{+} + i_{-} = 0 \text{ by KCL}$$
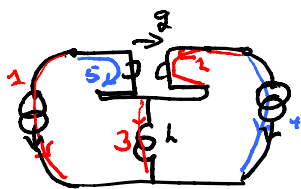
$$\begin{bmatrix} i_{in} \\ i_o \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} \begin{bmatrix} v_{ds} \\ v_o \end{bmatrix}$$



$$Y_{b \times b} = Y_{b \times n} Y_{n \times n}^{-1} Y_{n \times b}$$

$$= \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & g \\ 0 & 0 & \frac{1}{sL} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & -g & 0 & 0 & 0 \end{bmatrix}$$

$$J = \begin{bmatrix} s_1 \\ 0 \\ 0 \\ J_4 \\ 0 \end{bmatrix}, E = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$e = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 1 & 0 \\ 0 & 0 & 1 & 1 & -1 \end{bmatrix}$$

form

$$v_t = [e Y_{b \times b} e^T]^{-1} \{ e (Y_{b \times b} E - J) \}$$

$$-eJ = - \begin{bmatrix} 1 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & 1 & -1 \end{bmatrix} \begin{bmatrix} J_1 \\ J_4 \\ 0 \\ J_4 \\ 0 \end{bmatrix} = - \begin{bmatrix} J_1 \\ J_4 \\ J_4 \end{bmatrix}$$

$$eY_{\text{box}}e^T = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & 1 & -1 \end{bmatrix} \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & g \\ 0 & 0 & \frac{1}{2L} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & -g & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & 1 \\ 1 & 0 & -1 \end{bmatrix}$$

$$= \begin{bmatrix} 0 & -g & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & g \\ 0 & g & \frac{1}{2L} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & 1 \\ 1 & 0 & -1 \end{bmatrix} = \begin{bmatrix} 0 & -g & 0 \\ g & 0 & -g \\ 0 & g & \frac{1}{2L} \end{bmatrix}$$


$$v_t = \begin{bmatrix} 0 & -g & 0 \\ g & 0 & -g \\ 0 & g & \frac{1}{2L} \end{bmatrix}^{-1} \begin{bmatrix} -J_1 \\ -J_4 \\ -J_4 \end{bmatrix}; (eY_{\text{box}}e^T)^{-1}; \det(eY_{\text{box}}e^T) = -\frac{1}{2L}(-g^2) = \frac{g^2}{2L}$$

$$\text{Cofactors: } \Delta_{11} = g^2, \Delta_{21} = \left(-\frac{g}{2L}\right)(-1) = \frac{g}{2L}, \Delta_{31} = g^2(-1) = -g^2$$

$$\Delta_{12} = \frac{g}{2L}(-1) = -\frac{g}{2L}, \Delta_{22} = 0, \Delta_{32} = 0$$

$$\Delta_{13} = g^2, \Delta_{23} = 0, \Delta_{33} = g^2$$
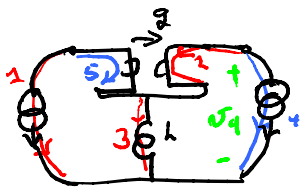
$$(eY_{\text{box}}e^T)^{-1} = \frac{2L}{g^2} \begin{bmatrix} g^2 & g/2L & -g^2 \\ -g/2L & 0 & 0 \\ g^2 & 0 & g^2 \end{bmatrix} = \begin{bmatrix} 2L & 1/g & -2L \\ -1/g & 0 & 0 \\ 2L & 0 & 2L \end{bmatrix}$$



$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 2L & 1/g & -2L \\ -1/g & 0 & 0 \\ 2L & 0 & 2L \end{bmatrix} \begin{bmatrix} -J_1 \\ -J_4 \\ -J_4 \end{bmatrix}$$

$$v_4 = v_2 + v_3 = \begin{bmatrix} -\frac{1}{g} + 2L & 0 & 2L \end{bmatrix} \begin{bmatrix} -J_1 \\ -J_4 \\ -J_4 \end{bmatrix} = \begin{bmatrix} -\frac{1}{g} + 2L & 2L \end{bmatrix} \begin{bmatrix} -J_1 \\ -J_4 \end{bmatrix}$$

$$v_1 = \begin{bmatrix} 2L & \frac{1}{g} + 2L \end{bmatrix} \begin{bmatrix} -J_1 \\ -J_4 \end{bmatrix}$$

$$2\text{-port description } v_{2\text{port}} = \begin{bmatrix} v_1 \\ v_4 \end{bmatrix}, i_{2\text{port}} = \begin{bmatrix} -J_1 \\ -J_4 \end{bmatrix}$$

$$\begin{bmatrix} v_{1, 2port} \\ v_{2, 2port} \end{bmatrix} = \begin{bmatrix} gL & \frac{1}{g} + gL \\ -\frac{1}{g} + gL & gL \end{bmatrix} \begin{bmatrix} i_{1, 2port} \\ i_{2, 2port} \end{bmatrix}; \quad Z_{2port} = \begin{bmatrix} gL & \frac{1}{g} + gL \\ -\frac{1}{g} + gL & gL \end{bmatrix}$$

$$Y = Z^{-1} = \frac{1}{\det \begin{bmatrix} \Delta_{11} & \Delta_{21} \\ \Delta_{12} & \Delta_{22} \end{bmatrix}} = \frac{1}{1/g^2} \begin{bmatrix} gL & -\frac{1}{g} - gL \\ \frac{1}{g} - gL & gL \end{bmatrix}$$

for the 2-port

Given a square matrix A , we can form its symmetric, A_{sy} , and skew symmetric, A_{sk} , parts to give $A = A_{sy} + A_{sk}$


$$A_{sy} = \frac{A + A^T}{2} = A_{sy}^T, \quad A_{sk} = \frac{A - A^T}{2} = -A_{sk}^T$$

$$Y_{sy} = \frac{1}{1/g^2} \begin{bmatrix} gL & -gL \\ -gL & gL \end{bmatrix}, \quad Y_{sk} = \frac{1}{1/g^2} \begin{bmatrix} 0 & -1/g \\ 1/g & 0 \end{bmatrix} = \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix}$$

$$C = g^2 L$$



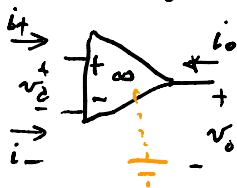What to do if no branch by branch $Y_{b \times b}$?



ideal op amp

$$v_d = 0; \quad i_{in} = i_+ \text{ or } i_- = 0$$

$$\begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} v_d \\ v_0 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_{in} \\ i_o \end{bmatrix}$$

Here $A v = B i$
 general linear
 description of
 circuit
 components

if Y exists $\Rightarrow i = Y v$
 then B^{-1} exists $\Rightarrow Y = B^{-1} A$

if Z exists $\Rightarrow v = Z i = A^{-1} B i$
 $Z = A^{-1} B$