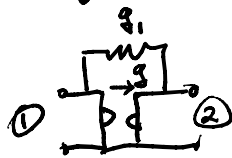



Necessary & sufficient

EE610
09/22/09



$$Y = \begin{bmatrix} g_1 & -g_1 \\ -g_1 & g_1 \end{bmatrix} + \begin{bmatrix} 0 & g_2 \\ -g_2 & 0 \end{bmatrix} = \begin{bmatrix} g_1 & g_2 - g_1 \\ -g_2 - g_1 & g_1 \end{bmatrix}$$

$$g_1 \geq 0, g_2 \text{ is real}$$

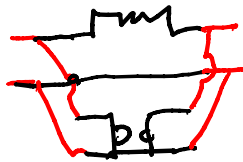

Given $Y(a) = \begin{bmatrix} y_{11}(a) & y_{12}(a) \\ y_{21}(a) & y_{22}(a) \end{bmatrix}$ when goes with the above circuit

necessarily $Y(a)$ is independent of a & all entries are real (not yet sufficient)

Rewrite $Y = Y_{sym} + Y_{as}$; $Y_{sym} = \frac{Y + Y^T}{2}$, $Y_{as} = \frac{Y - Y^T}{2}$

here necessarily Y_{sym} has rank 2 with $y_{11} = y_{22}$

$$Y_{sym} = \begin{bmatrix} y_{11} & y_{12} \\ y_{12} & y_{11} \end{bmatrix} \text{ as rank } Y_{sym} = 1, \det Y_{sym} = 0 = y_{11}^2 - y_{12}^2 = 0$$


$$\Rightarrow y_{12}^2 = y_{11}^2 \Rightarrow y_{12} = \pm \sqrt{y_{11}^2} = \pm y_{11}$$

we need $y_{11} = g \geq 0$ & then we need $y_{12} = -y_{11}$

\therefore necessarily, Y is real, independent of a ,

$$y_{11} = y_{22} = -y_{12} \geq 0$$

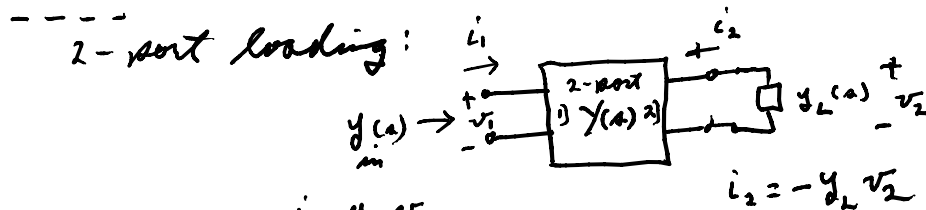these are also sufficient since given a $Y(a)$ satisfying these conditions we can make the circuit.



$$i_1 = y_{11} v_1$$

$$i_2 = -y_L v_2$$

$$\begin{bmatrix} i_1 \\ -y_L v_2 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

2nd eq: $-y_L v_2 = y_{21} v_1 + y_{22} v_2 \Rightarrow (-y_L - y_{22}) v_2 = y_{21} v_1$

$$v_2 = -(y_L + y_{22})^{-1} y_{21} v_1$$

1st eq: $i_1 = y_{11} v_1 + y_{12} v_2 = y_{11} v_1 - y_{12} (y_L + y_{22})^{-1} y_{21} v_1$

$$y_{in} = y_{11} - y_{12} (y_L + y_{22})^{-1} y_{21}$$

for a 2-port, $y_L + y_{22}$ in 1×1 so can divide


$$y_{in} = \frac{y_{11}(y_L + y_{22}) - y_{12} y_{21}}{y_L + y_{22}} = \frac{y_L y_{11} + \Delta y}{y_L + y_{22}}, \quad \Delta y = \det \text{ of } Y$$

Let's also find y_L as a function of y_{in}

$$y_{in} y_L + y_{in} y_{22} = y_L y_{11} + \Delta y$$

$$(y_{in} - y_{11}) y_L = -y_{in} y_{22} + \Delta y$$
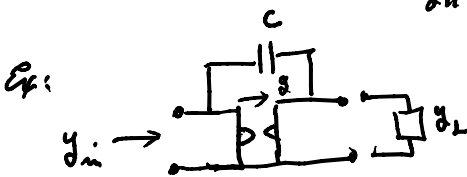
$$y_L = \frac{y_{in} y_{22} - \Delta y}{y_{11} - y_{in}}$$



$$Y = \begin{bmatrix} \kappa C & -\kappa C + g \\ -\kappa C - g & \kappa C \end{bmatrix}$$

$$\det Y = (\kappa C)^2 - (-\kappa C + g)(-\kappa C - g) \\ = (\kappa C)^2 - (\kappa C^2 + \kappa C g - \kappa C g - g^2) = g^2$$

$$y_L = \frac{y_{in} \kappa C - g^2}{\kappa C - y_{in}}$$

continue with a given $y_{in}(s) = \frac{\kappa}{s^2 + 2}$ is degree 2

the load to give this is

$$y_L(s) = \frac{\frac{\kappa}{s^2 + 2} \cdot \kappa C - g^2}{\kappa C - \frac{\kappa}{s^2 + 2}} = \frac{\kappa^2 C - g^2 s^2 - 2g^2}{\kappa^3 C + 2\kappa C - \kappa}$$

$$= \frac{(C - g^2) s^2 - 2g^2}{\kappa[\kappa^2 C + 2C - 1]} \quad \text{looks to be degree 3}$$


force a pole at $s=1$; $\kappa(\kappa^2 C + 2C - 1)|_{s=1} = 0 = (\kappa - 1)(\kappa^2 + \dots)$

$$1(C + 2C - 1) = 0 \Rightarrow C = 1/3$$

force a zero at $s=1$ $(1/3 - g^2) s^2 - 2g^2|_{s=1} = 0 \Rightarrow \frac{1}{3} - 3g^2 = 0$
 $\Rightarrow g = \pm 1/3$


$$y_{L(1)} = \frac{(\frac{1}{3} - \frac{1}{9})a^2 - \frac{2}{9}}{a(\frac{1}{3}a^2 + \frac{2}{3} - 1)} = \frac{\frac{2}{9}a^2 - \frac{2}{9}}{a(\frac{1}{3}a^2 - \frac{1}{3})} = \frac{\frac{2}{9}(a^2 - 1)}{\frac{1}{3}a(a^2 - 1)}$$

$$= \frac{2}{3a}$$

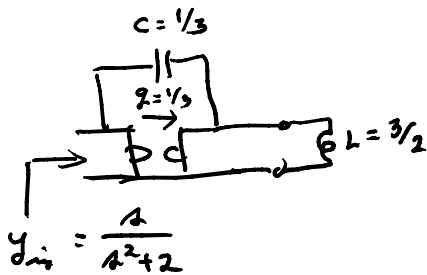

choose $C \& g$ to get y_L simpler than y_{in}


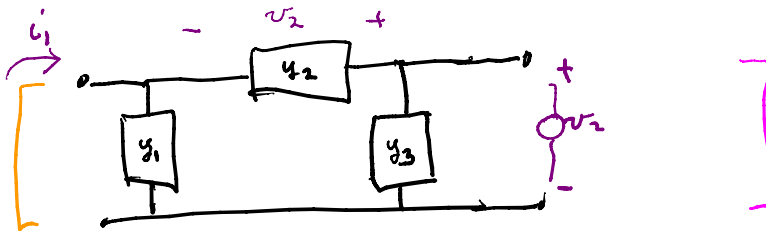
2-port Π equivalent: $y(a)$ $\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$




$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0} = y_1 + y_2, \quad y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0} = y_2 + y_3$$

$$y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -y_2 \Rightarrow y_{21} = -y_2 \text{ but needs } y_{12} \text{ possibly} \neq y_{21}$$

$$= \left. \frac{i_2}{v_1} \right|_{v_2=0}$$

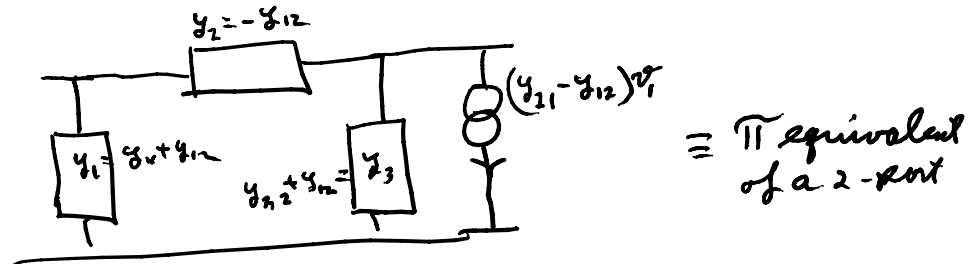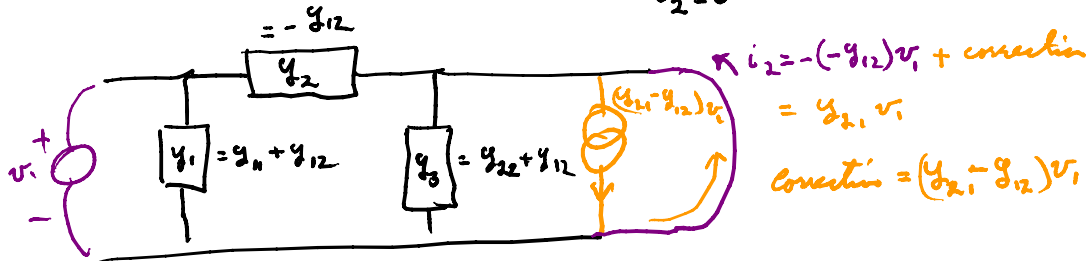

scattering matrix

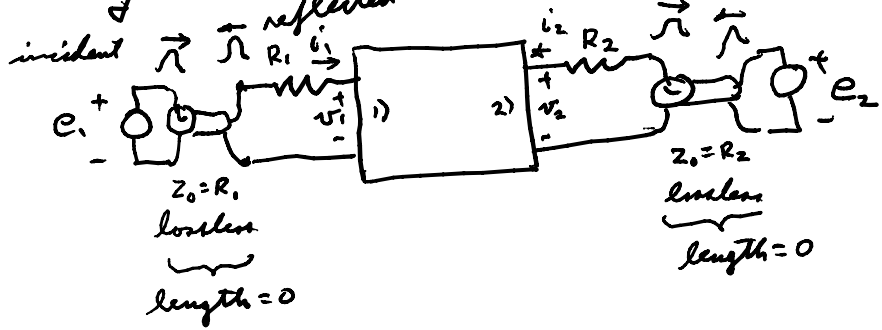

v^i = incident voltage (2-vector)

v^n = reflected voltage (2-vector)

S = scattering matrix $\Rightarrow v^n = S v^i$

$e_1 = v_1 + R_1 i_1$, $e_2 = v_2 + R_2 i_2$, $e = \begin{bmatrix} e_1 \\ e_2 \end{bmatrix}$; $R = \begin{bmatrix} R_1 & 0 \\ 0 & R_2 \end{bmatrix}$

$\frac{1}{2} e = v^i \Rightarrow \begin{cases} 2v^i = v + R i \\ 2v^n = v - R i \end{cases} \quad \left. \begin{aligned} 2v &= 2v^i + 2v^n \Rightarrow v = v^i + v^n \\ 2R i &= 2v^i - 2v^n \Rightarrow R i = v^i - v^n \end{aligned} \right\}$