


For  $V^T I^*$

$$(V^T I^*)^T = I^T V^* \neq I^{T*} V$$

EE 610  
10/01/09

Looking back

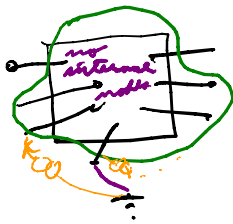- 1) pull out all nodes & make ground external
- 2) ground one node
- 3) port admittance



- ⇒ get the indefinite  $Y$
- ⇒ get the nodal admittance
- ⇒ use only some nodes externally (eliminate "internal" nodes by setting external currents to zero).

Examples of SCA


1)  $\frac{1}{s} C \Rightarrow y(s) = sC \Rightarrow$   
 $z(s) = \frac{1}{y(s)} = \frac{1}{sC}$

$S = \frac{1-y}{1+y} = \frac{1-sC}{1+sC}$ ; pole at  $s = -1/C$   
 necessarily  $C > 0$  if passive

$1 - S^*(j\omega) S(j\omega) \geq 0$  if passive  
 $= 1 - |S(j\omega)|^2 = 0$

$S(j\omega) = \frac{1 - j\omega C}{1 + j\omega C}$   
 $|S(j\omega)|^2 = \frac{1 + \omega^2 C^2}{1 + \omega^2 C^2} = 1$

here  $C$  is real  
 $\therefore C$  is passive if  $C \geq 0$

2)   $Z(s) = aL \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$ ;  $S = (Z + I_2)^{-1} (Z - I_2)$

$Z + I_2 = \begin{bmatrix} 1+aL & aL \\ aL & 1+aL \end{bmatrix} \Rightarrow \det(Z + I_2) = 1 + 2aL$

$S = \frac{1}{1+2aL} \begin{bmatrix} 1+aL & -aL \\ -aL & 1+aL \end{bmatrix} \begin{bmatrix} -1+aL & aL \\ aL & -1+aL \end{bmatrix} = \frac{1}{1+2aL} \begin{bmatrix} -1 & 2aL \\ 2aL & -1 \end{bmatrix}$

$(1+aL)(-1+aL) - (aL)^2 = -1 - aL + aL + (aL)^2 - (aL)^2 = -1$

$-aL(-1+aL) + ((1+aL)aL) = aL(1 - aL + 1 + aL) = 2aL$

$S(s) = \frac{1}{1+2aL} \begin{bmatrix} -1 & 2aL \\ 2aL & -1 \end{bmatrix}$  assume  $L \geq 0$   
 poles @  $s = -1/2L$

$$\begin{aligned} \mathbb{1}_2 - S^{T*}(j\omega)S(j\omega) &= \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \frac{1}{1+4\omega^2L^2} \begin{bmatrix} -1 & -2j\omega L \\ -2j\omega L & -1 \end{bmatrix} \begin{bmatrix} -1 & 2j\omega L \\ 2j\omega L & -1 \end{bmatrix} \\ &= \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \frac{1}{1+4\omega^2L^2} \begin{bmatrix} 1+4\omega^2L^2 & 0 \\ 0 & 1+4\omega^2L^2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \equiv \mathbb{O}_2 \end{aligned}$$

here  $\int_{\mathcal{L}_2}$  is passive as  $S$  is bounded real

In these cases we had lossless circuits

$$\mathcal{E}(t) = \int_{t \rightarrow \infty}^{\infty} v(t)^T i(t) dt = 0 \iff \text{definition of lossless}$$

$$\therefore \mathbb{1}_m - S^{T*}(j\omega)S(j\omega) = \mathbb{O}_m \Rightarrow \text{lossless if passive}$$

$\mathcal{L}$  in  $\mathcal{L}_2$ , Lebesgue integral; Ex of non- $\mathcal{L}_2$  function is the unit-step function

$$\int_{-\infty}^{\infty} 1(t)^2 dt = \int_0^{\infty} 1 dt = \infty$$


Ex of an  $\mathcal{L}_2$  function is  $f(t) = e^{-2t} 1(t)$ ;  $1(t) = \begin{cases} 1 & t > 0 \\ 0 & t < 0 \end{cases}$

$$\begin{aligned} \int_{-\infty}^{\infty} f^2(t) dt &= \int_{-\infty}^{\infty} e^{-4t} 1(t) dt = \int_0^{\infty} e^{-4t} dt = \frac{1}{-4} e^{-4t} \Big|_0^{\infty} \\ &= \frac{1}{4} e^{-0} = \frac{1}{4} < \infty \end{aligned}$$

For lossless  $\mathbb{1}_m - S^{T*}(j\omega)S(j\omega) = \mathbb{O}_m$  for all  $\omega$  if rational (passive)

$$S^*(s) = S(s^*) \text{ if real components}$$
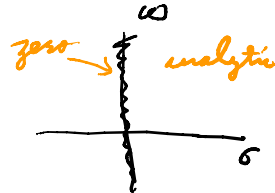
$$\Rightarrow \mathbb{1}_m - S^T(-j\omega)S(j\omega) = \mathbb{O}_m$$



analytically extend to  $s = \sigma + j\omega$  with  $\sigma > 0$

This means  $\mathbb{1}_m - S^T(-s)S(s) \equiv \mathbb{O}_m$  for all  $s$

$$\therefore \text{lossless condition is } \mathbb{1}_m = S^T(-s)S(s) \Rightarrow \underline{\underline{S^*(s) = S(-s)}}$$

$$\text{Ex: } S(s) = \frac{1-sC}{1+sC}; \quad S^*(s) = \frac{1+sC}{1-sC}$$

$$S(-s) = \frac{1-(-s)C}{1+(-s)C} = \frac{1+sC}{1-sC}$$

$\Leftarrow$  shows  $S(-s) = \frac{1}{S(s)}$  for the capacitor

Ex:

$$S(a) = \frac{1}{1+2aL} \begin{bmatrix} -1 & 2aL \\ 2aL & -1 \end{bmatrix}$$

$$S(-a) = \frac{1}{1-2aL} \begin{bmatrix} -1 & -2aL \\ -2aL & -1 \end{bmatrix} = S^T(-a)$$

$$\det = \frac{-1}{1+2aL} \times \frac{-1}{1-2aL} - \frac{2aL}{1+2aL} \cdot \frac{2aL}{1-2aL}$$

$$= \frac{1 - (2aL)^2}{(1+2aL)^2} = \frac{1-2aL}{1+2aL}$$

$$\rightarrow S(a) = \begin{bmatrix} \frac{-1}{1+2aL} & \frac{1+2aL}{1-2aL} \\ \frac{-2aL}{1+2aL} & \frac{1-2aL}{1+2aL} \end{bmatrix} = \begin{bmatrix} \frac{-1}{1-2aL} & \frac{-2aL}{1-2aL} \\ \frac{-2aL}{1-2aL} & \frac{-1}{1-2aL} \end{bmatrix}$$

here  $S^T(-a)$  is  $S^{-1}(a)$  implies  $\Sigma_L$  is lossless

We have  $S = (I_m + Y)^{-1} (I_m - Y)$ ; find conditions on  $Y$  to be lossless

$$\frac{1}{I_m} - \left( (I_m + Y(a))^{-1} (I_m - Y(a)) \right)^T \left( (I_m + Y(a))^{-1} (I_m - Y(a)) \right)$$

$$= I_m - \underbrace{(I_m - Y^T(-a)) (I_m + Y^T(-a))}_{(I_m + Y^T(-a))^{-1} (I_m - Y^T(-a))} \underbrace{(I_m + Y(a))^{-1} (I_m - Y(a))}_{(I_m - Y(a)) (I_m + Y(a))^{-1}}$$

$$= (I_m + Y^T(-a))^{-1} \left\{ (I_m + Y^T(-a)) (I_m + Y(a)) - (I_m - Y^T(-a)) (I_m - Y(a)) \right\} (I_m + Y(a))^{-1}$$

$$= (I_m + Y^T(-a))^{-1} \left\{ \begin{aligned} & I_m + Y^T(-a) + Y(a) + Y^T(-a) \cdot Y(a) \\ & - [I_m - Y(a) - Y^T(-a) + Y^T(-a) \cdot Y(a)] \end{aligned} \right\} (I_m + Y(a))^{-1}$$


$$= 2(I_m + Y^T(-a))^{-1} \{ Y(a) + Y^T(-a) \} (I_m + Y(a))^{-1} = O_m \text{ if lossless}$$

$$\Rightarrow Y(a) + Y^T(-a) = O_m$$

if  $m=1 \Rightarrow y(a) + y(-a) = 0 \Leftrightarrow E_2(y(a)) = 0$

$\Sigma_1$  rap.  $\begin{bmatrix} 1 \\ 1 \end{bmatrix} y = Ca \Rightarrow y(a) + y(-a) = C[a + (-a)] = 0$

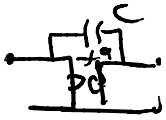and  $\begin{bmatrix} 1 \\ 1 \end{bmatrix} y = \frac{1}{L} a \Rightarrow \frac{1}{L} a + \frac{1}{L} (-a) = \frac{1}{L} (-a + a) = 0$



$$Y(s) = \begin{bmatrix} ca & -ca + g \\ -ca - g & ca \end{bmatrix}$$

$$Y^T(s) = \begin{bmatrix} -ca & ca + g \\ ca + g & -ca \end{bmatrix}$$

add:  $Y + Y^T = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}$

$\Rightarrow$  this is a lossless circuit  
(very useful for synthesis)