

EE610
10/06/09

Semistate equations:

$$E \dot{x} = A(x, t) + Bu$$

$$y = Cx$$

$u = \text{input} = u(t)$, an n -vector
 $y = \text{output} = y(t)$, an m -vector
 $x(t) = \text{semistate}$, a k -vector
 E, B, C are constant matrices
 E is $k \times k$, C is $m \times k$
 B is $k \times n$

$\dot{x} = \frac{dx}{dt}$; E may be singular
 (as we have resistors
 OTA's, etc.)

if linear & time-invariant

A is constant, $k \times k$

x can be $x = \begin{bmatrix} v_c \\ i_l \end{bmatrix}$ ← tree in which case $k = t + l = b = \# \text{ of branches}$
 ← link

Laplace transforming
 $\mathcal{L}[\cdot]$

$$E s \mathcal{L}[x] = A \mathcal{L}[x] + B \mathcal{L}[u]$$

$$\mathcal{L}[y] = C \mathcal{L}[x]$$

$(Es - A) \mathcal{L}[x] = B \mathcal{L}[u]$, if $(Es - A)^{-1}$ exists then

$$\mathcal{L}[x] = (Es - A)^{-1} B \mathcal{L}[u]$$

$$\rightarrow \mathcal{L}[y] = C (Es - A)^{-1} B \mathcal{L}[u] = T(s) \mathcal{L}[u]$$



$$T(s) = C (Es - A)^{-1} B = \text{transfer function}$$

$m \times n$ matrix

If E is the identity, $E = I_k$, then the semistate equations are state variable equations

(note if $E = I_k$, $T(\infty) = 0_{m \times n}$ & resistors by themselves can not be directly handled)

Ex:

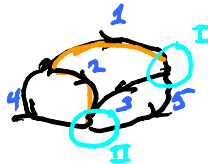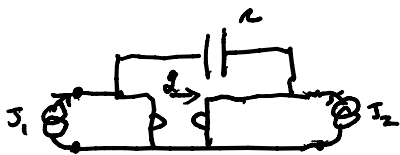

KCL: $\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & -1 & 0 & -1 \\ 0 & 1 & 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}$
 $= C i_b$

KVL: $\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & -1 & 1 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 \\ 1 & -1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix}$
 $= T v_b$

$u = \begin{bmatrix} J_1 \\ J_2 \end{bmatrix}$, $y = \begin{bmatrix} v_4 \\ v_5 \end{bmatrix}$

$e v_i = i_i$

$i_4 = 0 + (-J_1)$
 $i_5 = 0 + (-J_2)$

$$\begin{bmatrix} i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} \begin{bmatrix} v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -1 & -1 & -1 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_4 \\ i_5 \end{bmatrix}$$

$$= \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} \begin{bmatrix} 0 & 1 \\ -1 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$v_b = e^T v_t, \quad i_b = J^T i_x; \quad v_b = \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ -1 & -1 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} v_t, \quad i_b = \begin{bmatrix} 1 & 0 & 1 \\ -1 & -1 & -1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_3 \\ i_4 \\ i_5 \end{bmatrix}$$

$$C v_t = C v_b = i_b = i_3 + i_5$$

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 1 & 0 & 1 \\ -g & g & 1 & 1 & 1 \\ 0 & -g & -1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & 0 & 0 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \\ 0 & 0 \\ -1 & 0 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \end{bmatrix}$$

$$\Rightarrow E \dot{x} = Ax + B u$$

for the system:

$$\begin{bmatrix} \dot{v}_1 \\ \dot{v}_2 \\ \dot{i}_3 \\ \dot{i}_4 \\ \dot{i}_5 \end{bmatrix} = \begin{bmatrix} -g & g & 1 & 1 & 1 \\ 0 & -g & -1 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}$$

Two sources

$$i_{4b} = -J_1 \Rightarrow 0 = -1 \cdot i_{4b} - J_1$$

$$i_{5b} = -J_2 \Rightarrow 0 = -i_{5b} - J_2$$


output

$$y = \begin{bmatrix} v_4 \\ v_5 \end{bmatrix}_b = \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 & 0 & 0 \\ -1 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = C x$$

$$\text{Here } T(s) = C [sE - A]^{-1} B = Z(s)$$


as $v(s)$ = currents, $y(s)$ = outputs = voltages

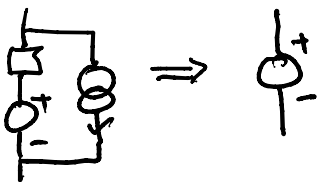But here had admittances in parallel with the input currents. If have voltage sources



so using admittances is not so convenient

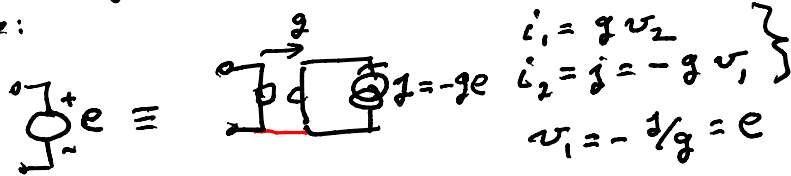
Still can always work with admittances in the linear case:





$$\left. \begin{aligned} i_1 &= g v_1 \\ i_2 &= -ge \\ v_1 &= -1/g = e \end{aligned} \right\}$$



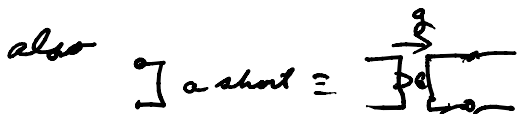⇒ can replace voltage sources by current sources without changing $T(s)$ [does add 2 more branches to the graph]




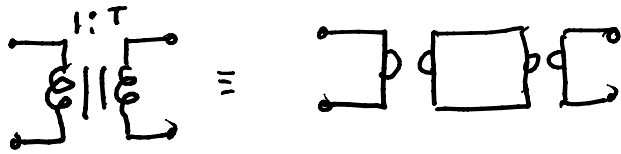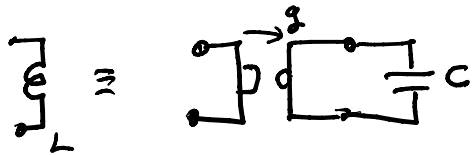

$$yf \equiv y \circ x$$

This means can assume a branch-by-branch admittance and derivatives only due to capacitors \Rightarrow gives semistate equations.

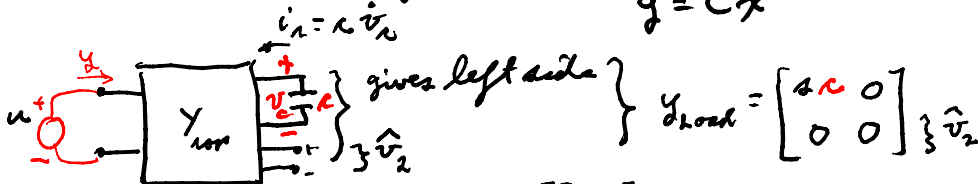To reverse: someone gives us $E\dot{x} = Ax + Bu$
 $y = Cx$



$$y_{in} = Tca; \quad Y_{comp} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v \\ v_c \\ \hat{v}_2 \end{bmatrix}$$

$$\text{output} \rightarrow \begin{bmatrix} i_{in} \\ i_c \\ 0 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v \\ v_c \\ \hat{v}_2 \end{bmatrix} = \begin{bmatrix} i_{in} \\ i_c \\ 0 \end{bmatrix} = \begin{bmatrix} Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v \\ v_c \\ \hat{v}_2 \end{bmatrix}$$

$$\text{derivative part of } E \rightarrow \begin{bmatrix} C\dot{v}_c \\ 0 \end{bmatrix} = \begin{bmatrix} Y_{21}v & Y_{22}v \\ Y_{21}v_c & Y_{22}v_c \end{bmatrix} \begin{bmatrix} v \\ v_c \\ \hat{v}_2 \end{bmatrix} \Big|_{3u}$$

implies can form Y_{comp} & make it by OTA's

\Rightarrow any linear circuit can be made with OTA's and capacitors