

$$R_y(s) = \frac{ky(s) - a y(s)}{ky(s) - a y(s)}$$

1st: $y(s), z(s) \rightarrow$ PR = positive real, rational
 $S(s) \rightarrow$ BR = bounded real, rational

all are analytic in $\sigma > 0$, no poles
 $y \& z \rightarrow$ no zero in $\sigma > 0$ at $\frac{1}{y} = z, \frac{1}{z} \text{ or } \frac{1}{2}$ is PR
 $S(s)$ can have zero in $\sigma > 0$ ($\Rightarrow \frac{1}{S}$ is not BR)
 (example: $y(s) = a$ is PR, $S(s) = \frac{1-y}{1+y} = \frac{1-a}{1+a}$ has a zero at $a=1$)

if PR & lossless then $y(s) = -y(-s)$ all poles & zeros are on $\sigma = j\omega$, alternate, simple & have positive residue
 here $\text{Ev } y(s) = 0$

if BR & lossless then $S(s)S(-s) = \frac{1}{m}$ if $m=1, S(-s) = \frac{1}{S(s)}$

$$\left. \begin{aligned} \text{Even } a(s) &= \frac{a(s) + a(-s)}{2} \\ \text{odd } a(s) &= \frac{a(s) - a(-s)}{2} \end{aligned} \right\} \text{add } a(s) = \text{Ev } a(s) + \text{Od } a(s)$$

$$\left. \begin{aligned} \text{Re } a(s) &= \frac{a(s) + a^*(s)}{2} \\ j \text{Im } a(s) &= \frac{a(s) - a^*(s)}{2} \end{aligned} \right\} \text{add } a(s) = \text{Re } a(s) + j \text{Im } a(s)$$




for $a = j\omega$ if rational with real coefficients
 $a^*(j\omega) = a(-j\omega) \Rightarrow \text{Re } a(j\omega) = \text{Ev } a(j\omega)$
 $\text{od } a(j\omega) = j \text{Od } a(j\omega)$

PR lossless: $y(s) = -y(-s) \Rightarrow \text{Ev } y(s) = 0 = \frac{y(s) + y(-s)}{2}$
 $\text{Ev } y(j\omega) = \text{Re } y(j\omega) = 0 \Rightarrow y(j\omega) = j \text{Im } y(j\omega)$
 $\Rightarrow y(s) = \text{odd}$

For lossless $\text{Ev } y(s) = 0$

OTA-C synthesis: OTA = operational transconductance amplifier
 = VCCS (op-amp id a VCVS)
 $v_{out} = \text{indeterminable}$
 $i_{out} = g_m(v_{in}), v_{in} = v_+ - v_-$
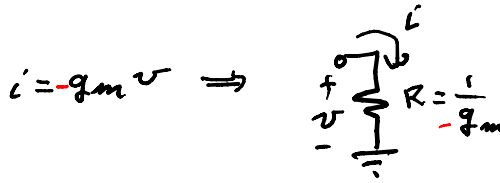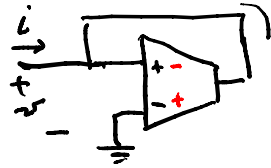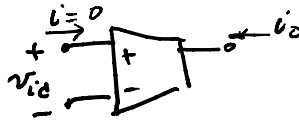
$$\begin{bmatrix} i_o \end{bmatrix} = \begin{bmatrix} g_m \end{bmatrix} \begin{bmatrix} v_{id} \end{bmatrix}$$



$$E \dot{x} = Ax + Bu$$

$$y = Cx$$

assume $u = v$, $y = i$

find a P & Q , nonsingular & transform the equation to make E diagonal: $x = Q \hat{x}$; P & Q constant

$$PEQ \hat{x} = PAQ \hat{x} + PBu$$

output $y = CQ \hat{x}$

$$Y(s) = CQ (sPEQ - PAQ)^{-1} PB \cdot U(s)$$

$$T(s) = CQ (sPEQ - PAQ)^{-1} PB$$

$$= CQ (P(sE - A)Q)^{-1} PB$$

$$= CQ Q^{-1} (sE - A)^{-1} P^{-1} PB$$

$$= C(sE - A)^{-1} B$$

choose P & Q to bring $\hat{E} = \begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} = PEQ$, $r = \text{rank of } E$

this gives $\hat{A} = PAQ$, $\hat{B} = PB$, $\hat{C} = CQ$

$$\hat{E} \hat{x} = \begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} \hat{x}_1 \\ \hat{x}_2 \end{bmatrix} = \begin{bmatrix} \hat{A} \\ \hat{C} \end{bmatrix} \hat{x} + \hat{B} u$$

$$y = \hat{C} \hat{x}$$

$\hat{x}_1 = r$ -vector

$\hat{x} = \begin{bmatrix} \hat{x}_1 \\ \hat{x}_2 \end{bmatrix} \begin{matrix} \} r \text{ rows} \\ \} n-r \text{ rows} \end{matrix}$

if x were a r -vector

current into capacitor & $n-r$ opens

$$\begin{bmatrix} -\hat{x}_1 \\ 0 \\ y \end{bmatrix}$$


$$\begin{bmatrix} \hat{E} \hat{x} \\ y \end{bmatrix}$$

$$= \begin{bmatrix} -\hat{A} & -\hat{B} \\ \hat{C} & 0 \end{bmatrix} \begin{bmatrix} \hat{x} \\ u \end{bmatrix}$$

$\}$ voltages $\}$ input voltage $\}$ m -vector

output current m -vector

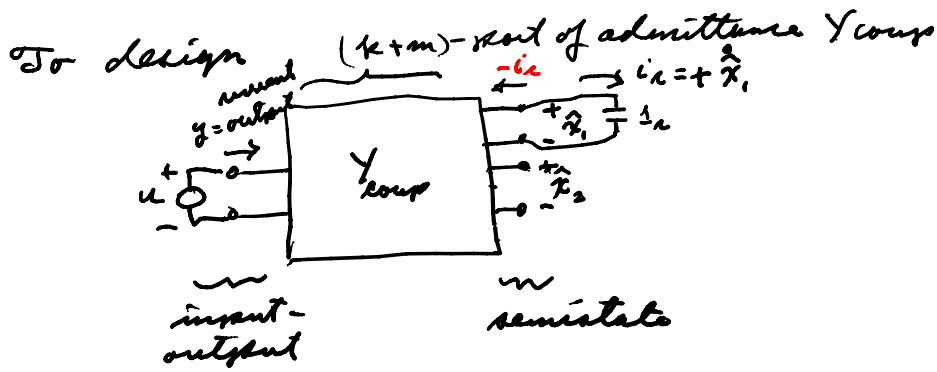an admittance matrix $Y_{comp} = \begin{bmatrix} -\hat{A} & -\hat{B} \\ \hat{C} & 0 \end{bmatrix} \begin{matrix} \} r \\ \} n \\ \text{num } r \\ \text{den } n \end{matrix}$



Ex: assume this is given


$$\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} a_1 & 0 \\ -1 & a_2 \end{bmatrix} x + \begin{bmatrix} 1 \\ -1 \end{bmatrix} v_i$$

$$a_1 < 0$$



$$a_2 > 0, k > 0$$

$$i_o = [3 \quad -5] x$$
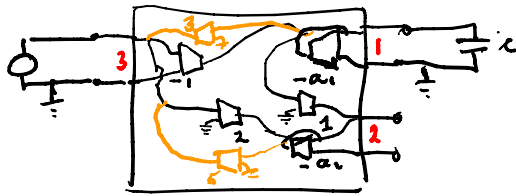
$$Y_{comp} = \begin{bmatrix} -a_1 & 0 & -1 \\ 1 & -a_2 & 2 \\ 3 & -5 & 0 \end{bmatrix}$$



OTA realization of Y_{comp}

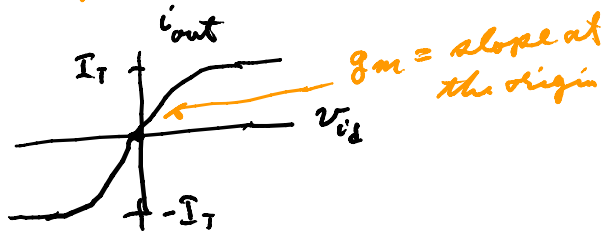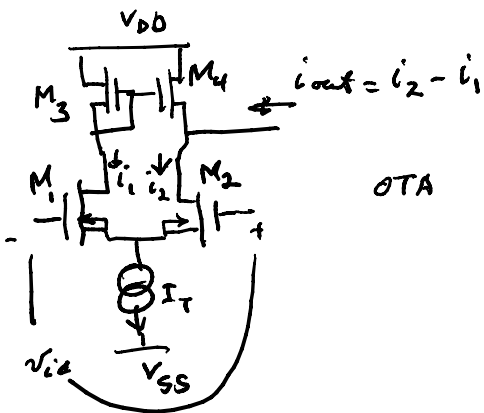

Back to Richards'

$$R_y(a) = \frac{k y(ka) - a y(a)}{k y(a) - a y(ka)}$$

if $y(ka) = -y(-ka)$ then

$$k y(ka) - (-ka) y(-ka) \quad @ a = -ka$$

$$= k y(ka) - ka y(ka) = 0 \text{ of num}$$

also $a = -ka$ is a zero of den.

then $s - (-1/s)$ cancels, already $s - 1/s$ cancelled

& the degree $\delta[R_y(s)] = \delta[y(s)] - 1$ \therefore if have real zeros
of the even part of $y(s)$
can repeat $\frac{1}{s}$ extraction

\therefore if y_L is lossless when y is
lossless this gives a 5th synthesis of lossless $y(s)$ until the $\delta[y_L] = 0$