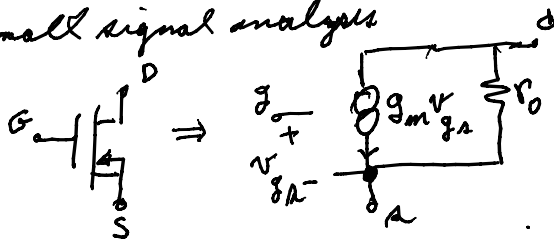


$V_{DS} = E = V_{GS}$
 $V_{DS} > V_{GS} - V_{TH}$
 if $E > V_{TH}$ > 0 for NMOS
 Inverse-mode
 mode
 transistor is
 in saturation

drain current at bias

$$= I_D = \beta (V_{GS} - V_{TH})^2 (1 + \delta V_{DS})$$

for small signal analysis



$$i_D = \beta (V_{GS} - V_{TH})^2 (1 + \delta V_{DS})$$




$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q = 2\beta (V_{GS} - V_{TH}) (1 + \delta V_{DS}) \Big|_Q$$

Q; $V_{GS} = E, V_{DS} = E$

$$g_m = 2 \frac{I_D}{V_{GS} - V_{TH}}$$

$$g_o = \frac{1}{r_o} = \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q = \beta (V_{GS} - V_{TH})^2 \delta \Big|_Q = \frac{I_D \cdot \delta}{1 + \delta V_{DS}}$$

small signal analysis

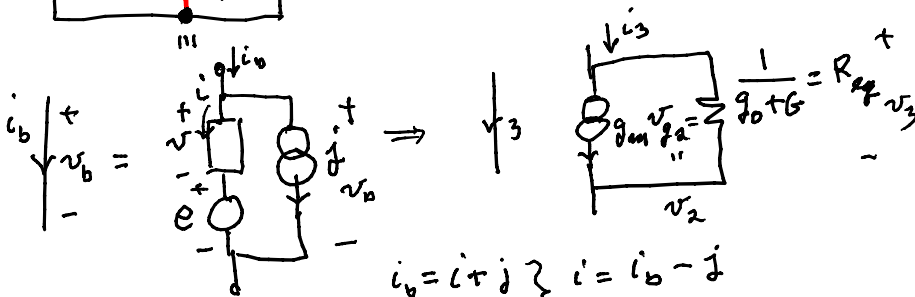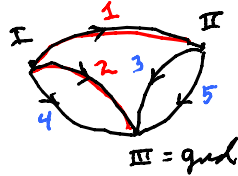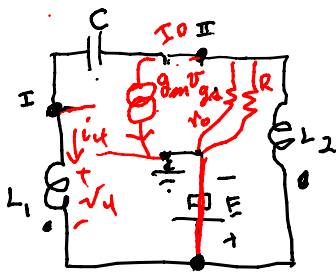

$$\left. \begin{aligned} i_b &= i + j \\ v_b &= v + e \end{aligned} \right\} \begin{aligned} i &= i_b - j \\ v &= v_b - e \end{aligned}$$

assume have linearized around the operating (= Q = bias) point; $\dot{x} = A x$

$$\begin{bmatrix} CA & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & g_m & g_b + g_c & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & L_1 & 0 \\ 0 & 0 & 0 & 0 & L_2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}$$

unconnected equations

$$\Rightarrow 0 = e i_b = \begin{bmatrix} 1_t & | & k \end{bmatrix} \begin{bmatrix} i_t \\ \vdots \\ i_r \end{bmatrix}; \quad 0 = \mathcal{O} v_b = \begin{bmatrix} -k^T & | & 1_r \end{bmatrix} \begin{bmatrix} v_t \\ \vdots \\ v_r \end{bmatrix}_b$$

$$\begin{bmatrix} v_t \\ \vdots \\ v_r \end{bmatrix} = \begin{bmatrix} 1_t & | & \vdots \\ \vdots & & \vdots \\ \vdots & & k^T \end{bmatrix} v_t \quad \begin{aligned} 0 &= -k^T v_t + v_r \\ \Rightarrow v_r &= k^T v_t \end{aligned}$$

$$\Rightarrow v_b = e^T v_t, \quad i_b = \mathcal{O}^T i_r$$

Note $v_b^T \cdot i_b = (e^T v_t)^T \cdot \mathcal{O}^T i_r = v_t^T \underbrace{[e \cdot \mathcal{O}^T]}_{\substack{\text{a row} \\ \text{vector}}} \underbrace{i_r}_{\substack{\text{column} \\ \text{a r-vector}}} = 0$

power in our circuit coming in from the outside $\equiv 0$

matrix

$$e \cdot \mathcal{O}^T = \begin{bmatrix} 1_t & | & k \end{bmatrix} \begin{bmatrix} -k \\ \vdots \\ 1_r \end{bmatrix} = -k + k = 0_{t \times r}$$

$$\begin{aligned} v &= v_b - e, \quad i = i_b - j \\ &= e^T v_t - e = \mathcal{O}^T i_r - j \end{aligned}$$


$$A(s)v = B(s)i$$

$$A(s)e^T v_t - A(s)e = B(s)\mathcal{O}^T i_r - B(s)j$$

$$A(s)e^T v_t - B(s)\mathcal{O}^T i_r = A(s)e - B(s)j$$

b-equation $\left\{ \begin{bmatrix} A(s)e^T & | & -B(s)\mathcal{O}^T \end{bmatrix} \begin{bmatrix} v_t \\ \vdots \\ i_r \end{bmatrix} = A(s)e - B(s)j \right.$

b-matrix

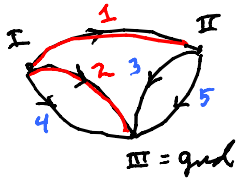

$$E = \begin{bmatrix} 1 & 0 & -1 & 0 & -1 \\ 0 & 1 & 1 & 1 & 1 \end{bmatrix} \quad ; \quad e = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad ; \quad d = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$J = \begin{bmatrix} 1 & -1 & 1 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 \\ 1 & -1 & 0 & 0 & 1 \end{bmatrix}$$

$$v = v_b = e^T v_t$$

$$i = i_b = J^T i_a$$

$$\underbrace{\begin{bmatrix} CA & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & g_m & g_t G & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix}}_{A(s)} \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & 1 \\ -1 & 1 \\ 0 & 1 \\ -1 & 1 \end{bmatrix}}_{B(s)} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$J_0 + G = G_0$$

$$= \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & L_1 & 0 \\ 0 & 0 & 0 & 0 & L_2 \end{bmatrix} \underbrace{\begin{bmatrix} 1 & 0 & 1 \\ -1 & -1 & -1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}}_{J^T} \begin{bmatrix} i_3 \\ i_4 \\ i_5 \end{bmatrix}$$

$$x = \begin{bmatrix} v_t \\ i_a \end{bmatrix}$$

$$\left[\begin{array}{cc|ccc} CA & 0 & -1 & 0 & -1 \\ 0 & 0 & 1 & 1 & 1 \\ -G_0 & g_m + G_0 & -1 & 0 & 0 \\ 0 & 1 & 0 & L_1 R & 0 \\ -1 & 1 & 0 & 0 & L_2 R \end{array} \right] x = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} C & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -L_1 & 0 \\ 0 & 0 & 0 & 0 & -L_2 \end{bmatrix} x = \begin{bmatrix} 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & -1 & -1 & -1 \\ G_0 - (g_m + G_0) & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 & 0 \end{bmatrix} x$$

take unilateral Laplace transform

$$sE \mathcal{L}[x] = A \mathcal{L}[x] + E x_0$$

↑ initial condition

$$\mathcal{L}[x] = [sE - A]^{-1} E x_0$$

here E is singular

so close to state variable equation

$$\frac{dx}{dt} = Ax$$