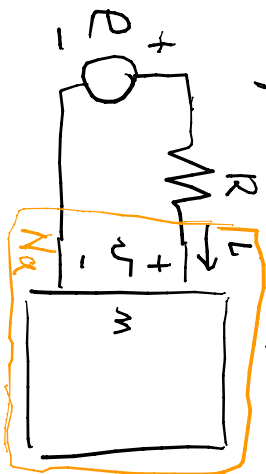


Consideration of results



$n$ -port  
or  $m$  terminal  
network

of linear

$$A(v) v = (B(s) G) R i$$

$$R = r 1_m, \quad G = R^{-1} = g 1_m, \quad g = 1/r$$

$$\left. \begin{aligned} e &= 2v^i = v + R i \\ 2v^n &= v - R i \end{aligned} \right\} \begin{aligned} v &= v^i + v^n \\ R i &= v^i - v^n \end{aligned} \Rightarrow (B G - A) v^i = (B G + A) v^n$$

$$R i = R Y_a e$$

$$v = (1_m - R Y_a) e$$

$$Z i = v, \quad Y v = i$$

$$\Rightarrow (1_m - 2R Y_a) v^i = 1_m v^n$$

$$v^n = S v^i \Rightarrow S = (B G - A)^{-1} (B G + A) = 1_m - 2R Y_a$$

$$= (1_m - R Y)^{-1} (1_m + R Y) = (G Z - 1_m)^{-1} (G Z + 1_m)$$

$$Y = G (1_m + S)^{-1} (1_m - S), \quad Z = (1_m - S)^{-1} (1_m + S) R = Y^{-1}$$

EE 610

10/05/10

$$A = R^{-1} Y_a$$

$$B G = 1_m - R Y_a$$


These  $(1_m + X)^{-1} (1_m - X) = (1_m - X) (1_m + X)^{-1}$  ( $(1_m + X)^{-1}$  &  $(1_m - X)$  commute)



$$Y_c = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix}; y_{in} = g_{11} - g_{12} (y_R + g_{22})^{-1} g_{21}$$

Other 2-port  $Y_c$ ;  $y_{in} = \frac{\Delta y + y_R y_{11}}{y_{22} + y_R}$ ;  $\Delta y = \text{determinant } Y_c = g_{11} g_{22} - g_{12} g_{21}$
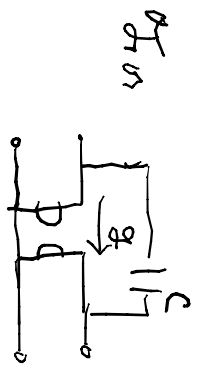
$$y_R = \frac{\Delta y - y_{22} y_{in}}{y_{in} - g_{11}}$$



$$Y_c = \begin{bmatrix} a_c & -a_c + g \\ -a_c - g & a_c \end{bmatrix}$$

$$y_R = \frac{g^2 - a_c y_{in}}{y_{in} - a_c} = \frac{(g^2/c) - a y_{in}(a)}{(1/c) y_{in}(a) - a}$$

$$= y(k\omega) \left[ \frac{k y(k\omega) - a y(a)}{k y(a) - a y(k\omega)} \right]$$

Identify with the Richards' function  $x y(k\omega)$

$g^2/c = k y(a)$   
 $k = 1/c$   
 $g^2 = y(k\omega)^2$

For a passive  $n$ -port  $Y(s)$  &  $Z(s)$  are positive-real  
 when they exist while  $S(s)$  (almost) always exists  
 and is bounded real. For finite circuits these  
 are rational (= ratio of 2 polynomials  $\Rightarrow$  all singularities  
 are poles) with real coefficients, i.e. PR for  $Y$  &  $Z$  and  
 BR for  $S$  [write PR or BR for scalars ( $m=1$ )]. And if  
 $Y(s)$  is PR so is the Richards' function.


$S(s)$  has no poles on  $s = j\omega$  while  $Z$  &  $Y$  have at  
 most simple poles on  $s = j\omega$ . One lower  $*$  for  
 $s \rightarrow -s$ . Then for lossless circuits,  $D_m = n \times n$  zero matrix

$$Y + Y_* = D_m, \quad Z + Z_* = 0_m, \quad \mathbf{1}_m = S_* S \Rightarrow S^{-1} = S_*$$

---

Transformers, gyrator equivalents, lossless synthesis, RC synthesis

1-port transformer

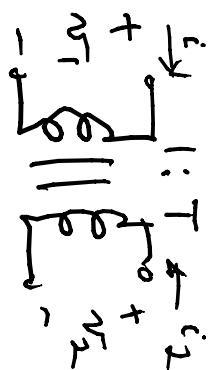

$$v_2 = T v_1$$

$$P_{in}(t) \equiv 0$$

$$P_{in} = v_1 i_1 + v_2 i_2 = 0$$

$$= v_1 i_1 + T v_1 i_2 = v_1 (i_1 + T i_2) = 0$$

for any  $v_1$

$$\Rightarrow i_1 = -T i_2$$

$$A v = B i$$

$$\begin{bmatrix} 0 & 0 \\ -T & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 1 & T \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$Z = A^{-1} B, \quad Y = B A^{-1} \quad \text{but no inverse for } A \text{ or } B$$

$$\text{assume } G = I_2 \quad S = (B + A)^{-1} (B - A)$$

$$= \begin{bmatrix} 1 & T \\ -T & 1 \end{bmatrix}^{-1} \begin{bmatrix} 1 & T \\ T & -1 \end{bmatrix} = \frac{1}{1+T^2} \begin{bmatrix} 1 & -T \\ T & 1 \end{bmatrix} \begin{bmatrix} 1 & T \\ T & -1 \end{bmatrix}$$


$$= \frac{1}{1+T^2} \begin{bmatrix} 1-T^2 & 2T \\ 2T & -1+T^2 \end{bmatrix}$$

$$I_2 - S^T S \Rightarrow S^2 = S^T S = \frac{1}{(1+T^2)^2} \begin{bmatrix} 1-T^2 & 2T \\ 2T & -1+T^2 \end{bmatrix} \begin{bmatrix} 1-T^2 & 2T \\ 2T & -1+T^2 \end{bmatrix}$$

$$= \frac{1}{(1+T^2)^2} \begin{bmatrix} (1-T^2)^2 + 4T^2 & 0 \\ 0 & 4T^2 + (-1+T^2)^2 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \text{ check lossless condition}$$

look at

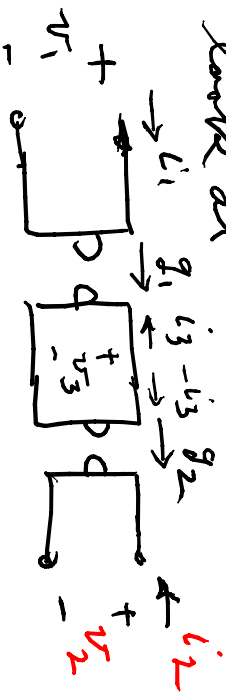

$$1: T = g_1/g_2$$

$$i_1 = g_1 v_3 \quad -i_3 = g_2 v_2$$

$$i_3 = -g_1 v_1 \quad i_2 = -g_2 v_3$$

$$i_1' = g_1 \left( -\frac{i_2}{g_2} \right) \Rightarrow i_1' = -\frac{g_1}{g_2} i_2 \Rightarrow i_1' + \frac{g_1}{g_2} i_2$$

$$v_2 = -\frac{i_3}{g_2} = +\frac{g_1}{g_2} v_1 \Rightarrow v_2 = \frac{g_1}{g_2} v_1$$

for odd  $n$  there is  $m=1$


$$g(a) + g(-a) = y + g_* = 2 \text{Er } g$$

$$y - g_* = 2 \text{Od } g$$

$$y = \text{Er } g + \text{Od } g$$

$$\text{Er } g \equiv 0$$
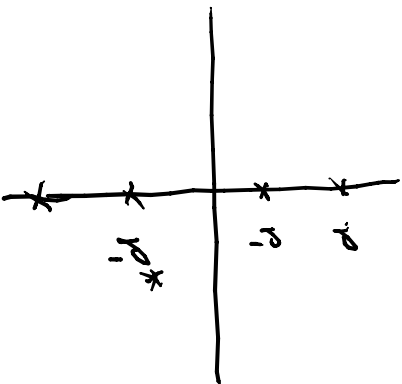
$$g(a) = a \left( \frac{\pi a^2 + \omega_i^2}{\pi a^2 + \omega_i'^2} \right)$$



$$y = \frac{R_{00}}{a} + R_{00} a + \sum_{i=1}^{m_1} \frac{2R_i a}{a^2 + \omega_i'^2}$$

Pr

$$z = \frac{R_{00}'}{a} + R_{00}' a + \sum_{i=1}^{m_1'} \frac{2R_i' a}{a^2 + \omega_i'^2}$$

also Pr

If no pole at  $a=0$  in  $g$  there is one in  $z$

$$\left( y - \frac{R_{00}}{a} \right)^{-1} = \frac{R_{00}'}{a} + \dots$$

same at  $a = \infty$

Ex:

$$f = \frac{(a^2+1)(a^2+5)}{a(a^2+4)} \text{ has a pole at } a = \infty$$

$$= \frac{a^4 + 6a^2 + 5}{a^3 + 4a}$$

$$\frac{a^3 + 4a}{a^4 + 6a^2 + 5} \left| \frac{1}{2} a \right.$$

$$\frac{2a^2 + 5}{a^3 + 4a} + \frac{5}{2}$$

$$\frac{3}{2} a \left| \frac{4}{3} a \right.$$


$$\frac{2}{2} a^2 + 5 \left| \frac{3}{10} a \right.$$

$$\frac{5}{5} \left| \frac{3}{2} a \right.$$

$$\frac{3}{2} a$$

$$g = a + \frac{1}{\frac{1}{2} a + \frac{1}{\frac{4}{3} a + \frac{1}{\frac{3}{10} a + 0}}}$$

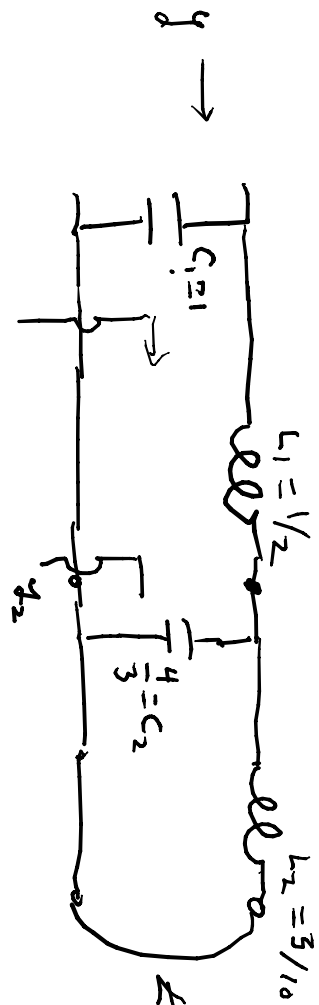= continued fraction expansion about  $a = \infty$



$$Z = \frac{1}{2}s + \frac{1}{\frac{4}{3}s + \frac{1}{\frac{3}{10}s + 1}}$$

$$y_2 = \frac{\frac{4}{3}s + \frac{1}{10}}{\frac{3}{10}s + 1}$$

$Z = 0$   
 = 1st corner  
 asymptotic  
 removed poles  
 at  $s = \infty$

gives zeros of  
 transmission  
 at  $s = \infty$   
 $\Rightarrow$  low pass filter

2nd corner = remove poles at  $s = 0$

$$y = \frac{s^4 + 6s^2 + 5}{s^3 + 4s} = \frac{5 + 6s^2 + s^4}{4s + s^3}$$




$$\frac{4R + R^3}{5/4R} \left( \frac{5 + 6R^2 + R^4}{5 + 5R^2} \right)$$

$$\frac{16}{19R} \left( \frac{4R + R^3}{4R} \right)$$

$$\frac{19R^2}{12R} \left( \frac{3R^3}{19} \right)$$
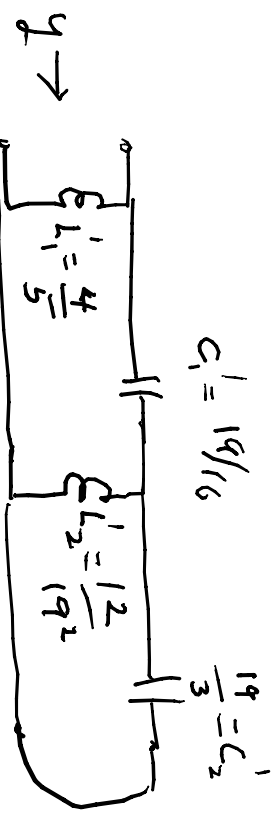
$$\frac{19R^2}{4} \left( \frac{3}{19} \right)$$




2nd Cover

(gives zeros of transmission at  $a = 0$  if attach output leads)  $\Rightarrow$  high pass filter

see chapters 8

LC
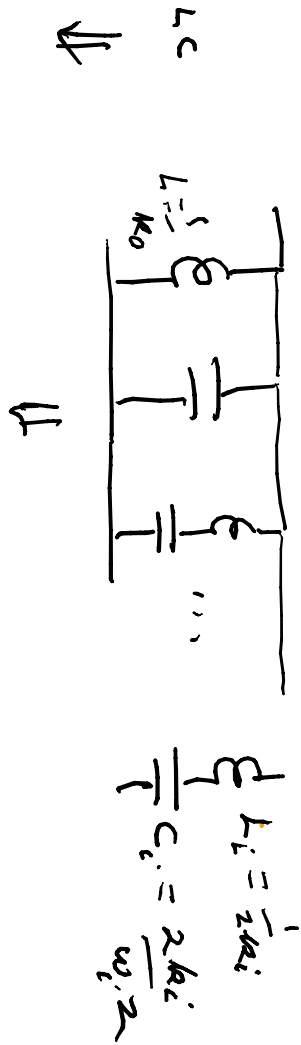
$$y_{LC}(s) = \frac{k_0}{s} + k_{\infty} s + \left( \sum_{i=1}^{M_1} \frac{2k_i s}{s^2 + \omega_i^2} = \sum_{i=1}^{M_1} \frac{1}{\frac{s}{\omega_i} + \frac{\omega_i}{s}} \right)$$



RC

$$y_{RC} = k_0 + k_{\infty} s + \left( \sum_{i=1}^{M_1} \frac{1}{\frac{1}{2k_i} + \frac{\omega_i}{2R_i \cdot s}} = \sum_{i=1}^{M_1} \frac{2k_i \cdot s}{s + \omega_i} \right)$$

$R_i = \frac{1}{2k_i}$   
 $C_i = \frac{2k_i}{\omega_i}$

