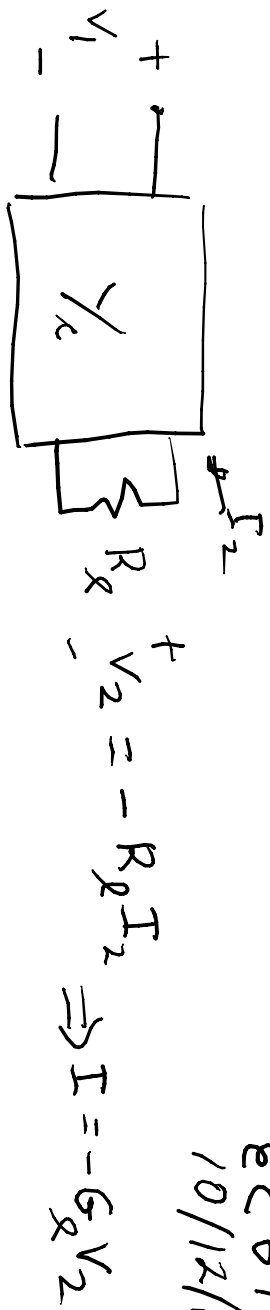


EE 610  
10/12/10




$$\Rightarrow I = -G_R V_2$$

$$I_1 = g_{11} V_1 + g_{12} V_2$$

$$I_2 = g_{21} V_1 + g_{22} V_2 = -G_R V_2$$
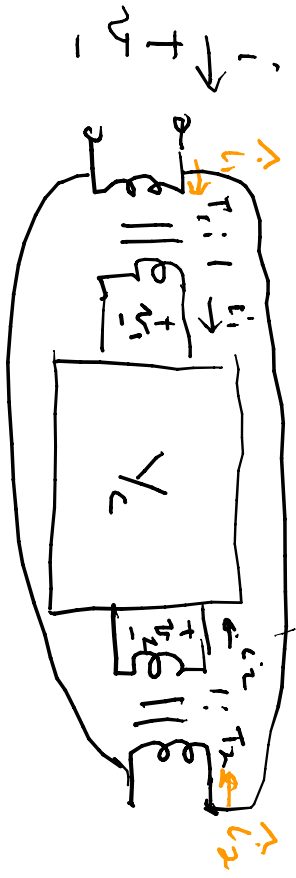
$$\frac{V_2}{V_1} = \frac{g_{21}}{-(G_R + g_{22})} = \frac{-g_{21}}{G_R + g_{22}} = \frac{-y_{21}/G_R}{1 + y_{22}/G_R}$$



$$L' = y_{in} v \quad ; \quad v = T_1 v_1 = T_2 v_2 \Rightarrow v_1 = v/T_1$$

$$v_2 = v/T_2$$

$$= L_1' + L_2' \quad ; \quad L_1' = T_1 L_1$$

$$L_2' = T_2 L_2$$

$$= T_1 (y_{11} v_1 + y_{12} v_2) + T_2 (y_{21} v_1 + y_{22} v_2)$$

$$= \left\{ T_1 \left( \frac{y_{11}}{T_1} + \frac{y_{12}}{T_2} \right) + T_2 \left( \frac{y_{21}}{T_1} + \frac{y_{22}}{T_2} \right) \right\} v$$

$$= y_{in} v \Rightarrow y_{in} = y_{11} + y_{22} + \frac{T_1}{T_2} y_{12} + \frac{T_2}{T_1} y_{21}$$

if  $y_{12} = y_{21}$  then  $y_{in} = y_{11} + y_{22} + \left( \frac{T_1}{T_2} + \frac{T_2}{T_1} \right) y_{21}$

$$= y_{11} + y_{22} + \left( \frac{T_1^2 + T_2^2}{T_2 T_1} \right) y_{21}$$

Choose  $T_1 T_2 = \pm 1$  & look at a pole on jw axis

$y_m$  is PR if  $y$  is PR

$$8 \quad y_m | z \quad \frac{2k_1 a}{a^2 + \omega_0^2} + \frac{2k_2 a}{a^2 + \omega_0^2} + \frac{2k_{x1} a}{a^2 + \omega_0^2} \quad ; \quad \begin{matrix} 2k_1 \text{ depends} \\ \text{on } T_1^2 + T_2^2 \\ T_1 T_2 \end{matrix}$$

means  
a pole  
on jw axis

if pole for  $y_{x1}$  is not present in  $y_{11} \& y_{22}$

i.e.  $k_1 = k_2 = 0$   $y_m | z$  (any sign on  $k_{x1}$  by  
choice of  $T_1 T_2$ )  
means  $a = j\omega_0$

$\Rightarrow$  can not be PR as can get a negative residue  
( $2k_{x1}$ ) for a jw axis pole.

If there is a common pole the residue

$$k_1 + k_2 + k_{z_1} \geq 0$$

$\therefore$  any pole on the jw axis in  $g_{z_1}$  is also in  $g_{v_1}$   
(and  $g_{z_2}$ )

$$\frac{V_2}{V_1} = \frac{-g_{z_1}}{1 + g_{z_2}}$$

for a lossless coupling circuit  
then  $g_{z_2}(s) = \frac{N_{z_2}(s)}{D_{z_2}(s)}$ ,  $g_{z_1} = \frac{N_{z_1}}{D_{z_1}}$

NZD polynomial

$$= \frac{-N_{z_1} D_{z_2}}{D_{z_1} (D_{z_2} + N_{z_2})}$$

$$= \frac{-N_{z_1} \hat{D}_{z_2}}{D_{z_2} + N_{z_2}}$$

$g_{z_2} =$  realizable function

an even + an odd

As if given  $V_2 = \frac{N(s)}{D(s)}$  ;

$D(s)$  has no zeros in  $\sigma > 0$  as passive loaded in a transfer = a Hurwitz polynomial



As  $\rightarrow Z_{in} = R + \frac{N_{LC}}{D_{LC}} = \frac{1}{g_m} \Rightarrow g_m = \frac{D_{LC}}{R D_{LC} + N_{LC}}$

$R = 1$  has no pole in  $\sigma > 0$  as  $N$  & with loss  $= \frac{D_{LC}}{D_{LC} + N_{LC}}$

$\therefore$  the denominator + numerator of a reactance function is a Hurwitz polynomial

$\therefore$  synthesize  $g_{dr}$  to get the zeros of  $g_{r1}$  (easy if zeros of  $v_2/v_1$  are at  $a=0$  or  $a=\infty$ )


$$\frac{V_2}{V_1} = \frac{N}{D} ; \quad y_{22} = \frac{\partial^2 D}{\partial V_2^2} \text{ or vice versa}$$

$$\text{Ex: } \frac{V_2}{V_1} = \frac{R}{R^2 + 10R + 5}$$

$$D(R) = (R^2 + 5) + (10R)$$

$$\frac{\partial^2 D}{\partial V_2^2} = \frac{10R}{R^2 + 5}$$

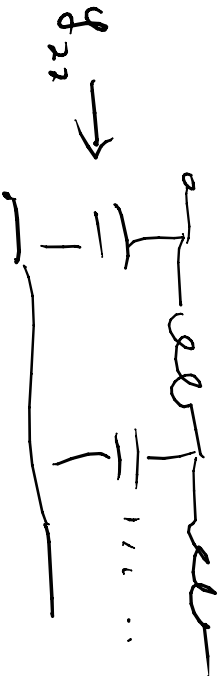
$$y_{22} = \frac{10R}{R^2 + 5} ; \quad y_{21} = \frac{-R}{R^2 + 5} ; \quad R \text{ results from the synthesis}$$




gives zero of transmission  
at  $R = \infty$  (where series  
arms open & shunt arms  
short)  $\Rightarrow$  1st zero synthesis  
of  $y_{22}$

$$y_{22} = \frac{1}{y_{22}} = \frac{8+5}{10A} = \frac{1}{10}A + \frac{5}{10A} = \frac{1}{10}A + \frac{1}{2A}$$

$C=2 \quad L=1/10$

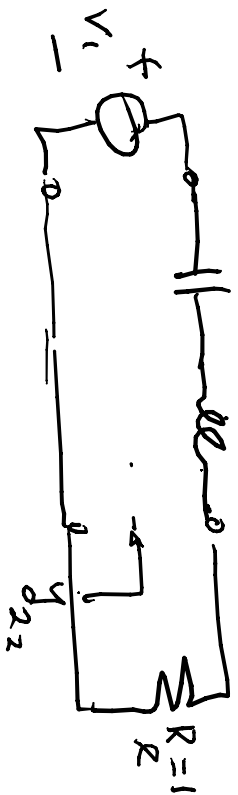


$$y_{21} = \frac{I_2}{V_1} \quad | \quad V_2=0$$

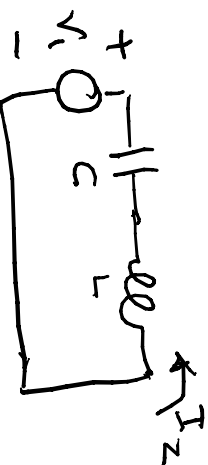

$$y_{21} = \frac{-CA}{LC\theta^2 + 1} = \frac{-\frac{1}{10}A}{8 + \frac{1}{LC}} = \frac{80A}{8^2 + 5}$$

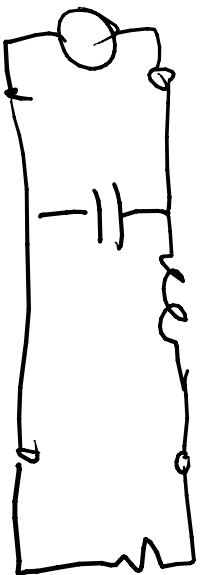
$$I_2 = -Y_2 \cdot V_1 = \frac{-1}{LC\theta^2 + 1} V_1$$



doesn't give  $g_{21}$

$$\text{look at } y_{22} = \frac{2V}{2A} = \frac{2^2+5}{10A} = \frac{1}{10}A + \frac{1}{2A}$$

$$y_{21} = -\frac{1}{2A}$$

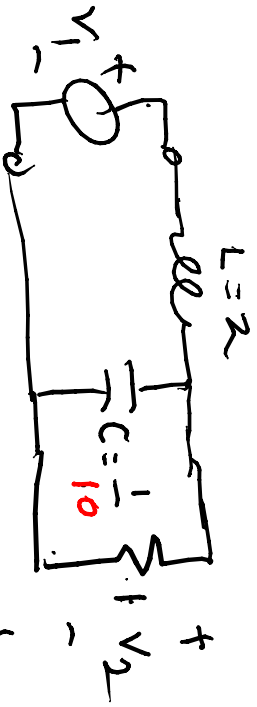


$$\frac{V_2}{V_1} = \frac{3z_{C1}}{z_L + 3z_{C1}} = \frac{1+4C}{A_L + \frac{1}{1+4C}} = \frac{1}{A_L^2 C + A_L + 1} = \frac{1/LC}{A^2 + \frac{2}{C} + \frac{1}{LC}}$$

$$\frac{V_2}{V_1} = \frac{5}{A^2 + 10A + 5} = \frac{R_2}{A^2 + 10A + 5}, \quad R_2 = 5$$



For RC systems  $\frac{V_2}{V_1} = \frac{-g_{21}}{g_{22}}$  all poles are on the  $-s$  axis


$$g(s) = \frac{-g_{21}}{1 + g_{22}}$$

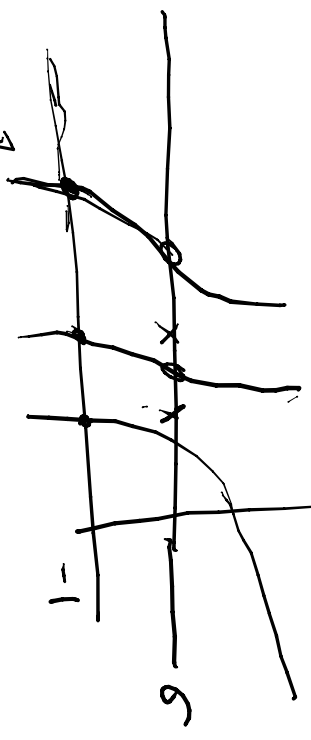


Zeros of the even part of an RC circuit are all real

$$g_{RC} + g_{RC}^*$$

if terminated in  $R_2 = 1$

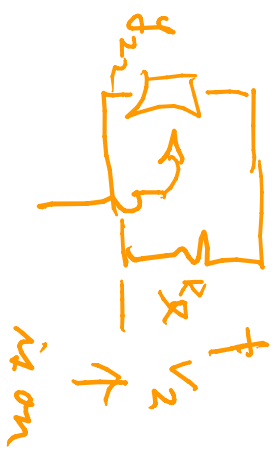

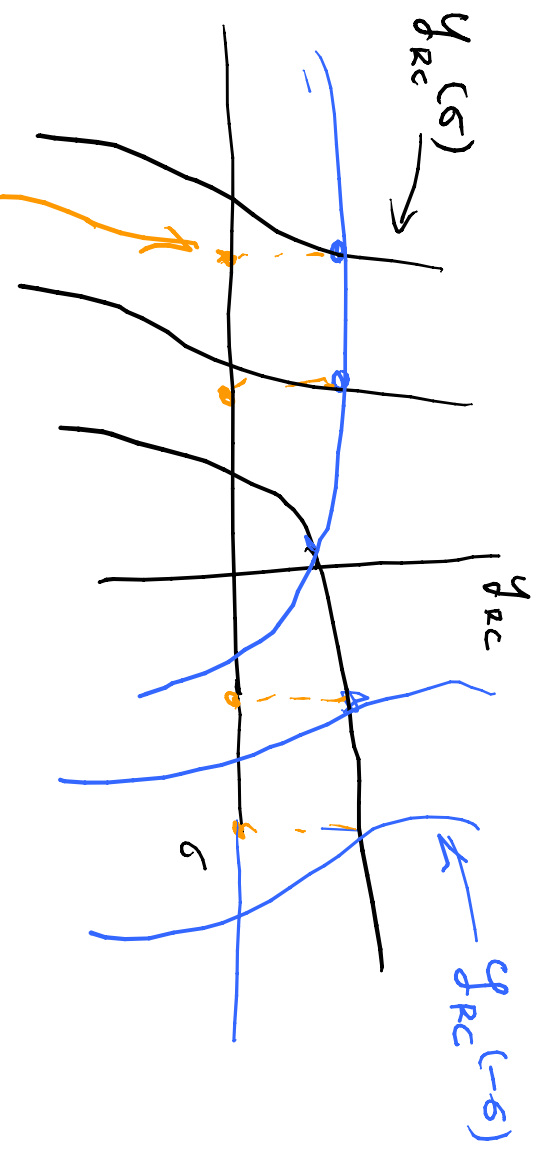parallel combination of  $R_2$  &  $g_{22}$



zeros of the even part of  $y_{RC}$

allows to use real  $\sigma$  in Richards' functions for  $y_{RC}(\sigma)$