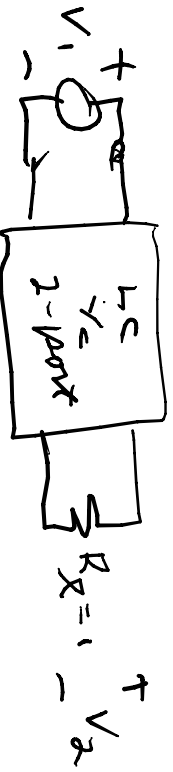


EE610  
10/14/10



passive

passive  
rational  
with real  
coefficients

$$\frac{V_2}{V_1} = \frac{-y_{21}}{1 + y_{22}} = \frac{N(\omega)}{D(\omega)}$$

$D = \text{Hurwitz}$

$y_{12} = y_{21}$   
reciprocal 2-port  
 $Y_c = Y_c^T$   $V^T = \text{transposes}$

$$y_{21} = R_{210} + \frac{R_{210}}{A} + \sum_{i=1}^{m_{x1}} \frac{2R_{i21}A}{A^2 + \omega_i^2} = \text{odd in } \omega = \frac{N_{21}}{D_{21}}$$

if  $N_{21}$  is odd,  $D_{21}$  is even  
" is even " is odd

$$y_{22} = \frac{\epsilon_r D}{\partial d D} \text{ or } \frac{\partial d D}{\epsilon_r D}$$

$$\frac{V_2}{V_1} = \frac{N}{D} = \frac{N}{\epsilon_r D + \partial d D}$$

$\left\{ \begin{array}{l} \frac{N/\epsilon_r D}{1 + \frac{\partial d D}{\epsilon_r D}} \text{ or } \frac{N/\partial d D}{1 + \frac{\epsilon_r D}{\partial d D}} \end{array} \right.$   
choice fixed by  $N$  odd or even

$$\frac{V_2}{V_1} = \frac{R}{A^3 + 1A^2 + 3R + 4} = \frac{N}{D} \quad N = R = a \text{ constant even}$$

$$= \frac{R}{(A^3 + 3A) + (2A^2 + 4)} = \frac{R/(A^3 + 3A)}{1 + \left(\frac{2A^2 + 4}{A^3 + 3A}\right)}$$

$$y_{21} = \frac{R}{A(A^2 + 3)} \quad (odd)$$

$$y_{22} = \frac{2A^2 + 4}{A(A^2 + 3)} \quad (even/odd)$$

$$= \frac{R}{A} + \frac{-\frac{R}{3}A}{A^2 + 3} = -R \left\{ \frac{\frac{1}{3}(A^2 + 3) - \frac{1}{3}A^2}{A(A^2 + 3)} \right\} = \frac{-R}{A(A^2 + 3)}$$


synthesis  $y_{22}$  to give  $y_{12}$ ; all zeros of  $y_{12}$  are at  $\infty$   
 $\Rightarrow$  let  $\text{zeros } y_{12}$  be at  $\infty$

$$y_{22} = \frac{2A^2 + 4}{A^3 + 3A}$$

no poles at  $\infty$ , but one in in  $\frac{1}{y_{22}} = \frac{A^3 + 3A}{2A^2 + 4}$

$$\sum \frac{1}{y_{22}} = \frac{1}{y_{22}} \Rightarrow \frac{2A^2 + 4}{A^3 + 3A} \left( \frac{1}{2} \right) \frac{1}{A} \left( \frac{2A}{A^3 + 3A} \right) \left( \frac{1}{A} \right) \left( \frac{2A}{2A^2 + 4} \right) \left( \frac{1}{4} \right) \left( \frac{1}{A} \right)$$

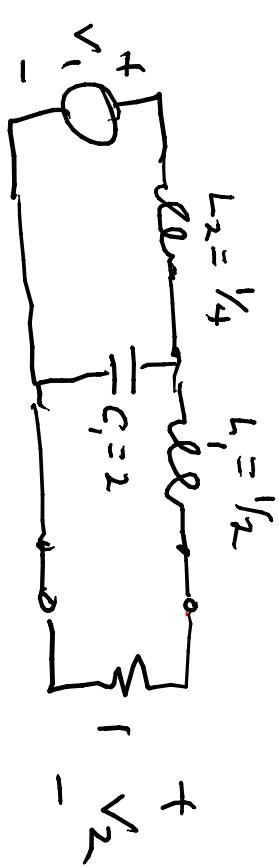to find the  $R$  in  $y_{21}$ ; let  $\sigma = 1$ ,



$LA = LG = L$   
 resistor value  $a$   
 resistor  $R \geq L$   
 $CA = CG \Rightarrow G = C$

Q 5=1 the circuit is



$$\frac{V_2}{V_1} = \frac{-y_{21}(1)}{1 + y_{22}(1)}$$

$$\frac{V_2}{V_1} = \frac{k}{R^3 + 2R^2 + 3R + 4} \Big|_{S=1} = \frac{k}{1 + 2 + 3 + 4} = \frac{k}{10}$$

here  $k=4$  as  $\frac{V_2}{V_1} = \frac{1}{5/2} = \frac{k}{10}$

to get state variables for a given

transfer function

$$\frac{Y(s)}{U(s)} = T(s) = \frac{N_1s + M_2}{A^2 + d_1s + d_0} \Rightarrow \dot{x} = Ax + Bu$$

$$\text{here } D=0 \quad y = Cx + Du$$

look at

$$\begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -d_0 & -d_1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} b_1 \\ b_2 \end{bmatrix} u$$

$$y = [c_1 \quad c_2] \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

to get  $T(A), k=2$

$$A I_k X = AX + BV \quad X = (A I_k - A)^{-1} B U$$

$$Y = C X + D U \quad Y = \{C(A I_k - A)^{-1} B + D\} U$$

$$T(A) = D + C(A I_k - A)^{-1} B \quad D = T(\infty)$$

need  $(A I_2 - I)^{-1} = \begin{bmatrix} A & -1 \\ d_0 & A + d_1 \end{bmatrix}$ ;  $\det(A I_2 - A) = A^2 + d_1 A + d_0$

$$(A I_2 - A)^{-1} = \frac{1}{A^2 + d_1 A + d_0} \begin{bmatrix} A + d_1 & +1 \\ -d_0 & A \end{bmatrix}$$

$$\begin{aligned}
 (A^2 + d_1 A + d_0) [C(AI_2 - A)^{-1} B] &= [c_1 \quad c_2] \begin{bmatrix} A + d_1 & 1 \\ -d_0 & A \end{bmatrix} \begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = M_1 A + M_0 \\
 &= [c_1 A + c_1 d_1 - c_2 d_0, \quad c_1 + c_2 A] \begin{bmatrix} b_1 \\ b_2 \end{bmatrix}
 \end{aligned}$$


choose  $b_1 = 0, b_2 = 1$

Then

$$= c_1 + c_2 A = M_0 + M_1 A$$

$$\dot{x} = \begin{bmatrix} 0 & 1 \\ -d_0 & -d_1 \end{bmatrix} x + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u$$

$$y = [m_0 \quad m_1] x + d u$$

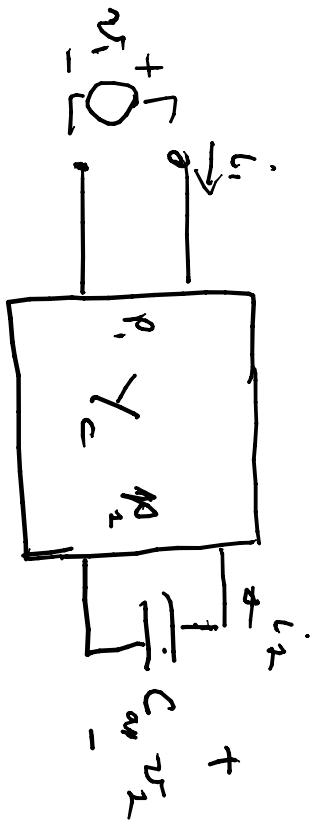

$$T(s) = \frac{I_2}{V_1}$$

$$\dot{I}_2 = -C_{eq} \dot{V}_2 = -C_{eq} X$$

$$y = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$y_{11}$  is  $P_1 \times P_1$   
 $y_{12}$  is  $P_2 \times P_1$   
 $P_1 = \#$  of input ports  
 $P_2 = \#$  of output ports

$$-C_{eq} \dot{x} = y_{22} x + y_{21} u =$$

$$y = y_{12} x + y_{11} u = Cx + Du$$

$$\dot{x} = -C_{eq}^{-1} y_{22} x - C_{eq}^{-1} y_{21} u = Ax + Bu$$

$$Y_c = \begin{bmatrix} D & C \\ -C_B & -C_{ap}A \end{bmatrix}$$